

Analogna i mješovita obrada signala

Predavanja – I. Ciklus

Hvala Darioli na bilježnici
Uploaded by milan89
Scanned by Dado G.

AMOS

MI 60

$$ZI \quad 40 = P + U = 20 + 20$$

- ↓
- 1 → 0
 - 2 → 5
 - 3 → 10
 - 4 → 15
 - 5 → 20

$$DZ \quad 80 = 10Z + 2DZ = 10 + 10$$

PRAG

MI + ZIp

50% 30

ZI 9

DZ

50% 10

ROK

P 60

U 20


DZ 20

Literatura

S. Franco - Designing operational amplifiers and analog integrated circuits
 Mijat - El. filtri - 2001. skripta

Lin, nelin izodličenja

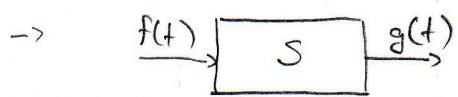
SUSTAV → skup reduseno povezanih komp. kog je zajedno obavljaju određenu funkciju



$f(t)$, $g(t)$ - mogu biti i vekt. funkcije - više ulaza i izlaza organizovano se na $f(t)$; $g(t)$ - skalarni (1 ulaz, 1 izlaz)
→ Operator logički deluje na $f(t)$ dajući $g(t)$


$$g(t) = S[f(t)]$$

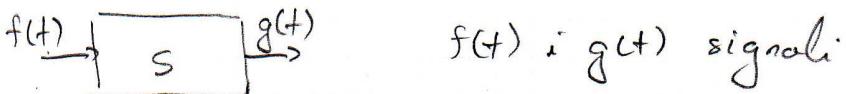SIGNAL → proužajiva varanska veličina $x(t)$



→ interesantni oblik signala: $u(t)$, $i(t)$, $(P(t), \dots)$

- valni oblik signala $x(t)$

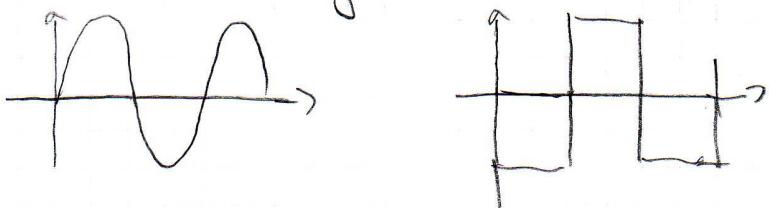

OBRADA SIGNALA

→ analogni obrada signala - bez pretvorbe

→ dig. obrada signala → nakon A/D pretvorbe


→ mješovita obrada signala - i A; D obrada signala.

- primjeri: audio/video sustavi, modem, med. uređaji


- konstenje A; D obrade zahfjeva pretvorbu između različitih reprezentacija signala.

Dva moguća scenario:

a)


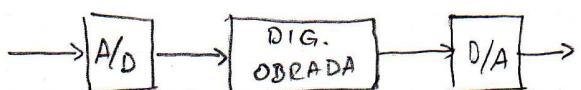


2)

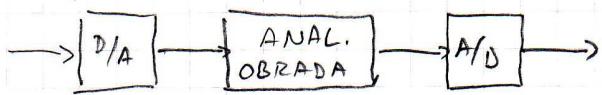

FUNKCIJE (OPERACIJE)

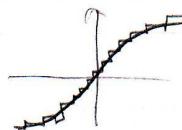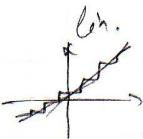- pojačavanje
- filtriranje (smetnji, ...)
- modulacija i demodulacija (za prenos i obrade)
- prilagodba razina
- prilagodba impedancija
- U/I i I/U pretvorba
- linearizacija
- zbrajanje i oduzimanje
- decimacija i integracija
- AC/DC pretvorba
- detekcija razine
- ograničavanje razine (limitiranje)
- A/D ili D/A pretvorba
- otiskovanje (uzimaće uzorak)
- kvantiziranje
- ⋮




SIGNALI I NJIHOVI SPEKTARI

- valni oblik signala nam često ne daje dovoljno inf. o signalu
- svaki signal je sastavljen od određenog broja frekv. kompon.
- skup svih frekv. kompon. signala je SPEKTAR.
- periodični signali - mogu se prikazati Fourierovim redom - diskretan spektar
- neperiodični signali - prikazuju se Fourierovom transf. - kont. spektar
- vremenska domena - valni oblik
- frekv. domena - spektar signala


VALNI OBLIK, FAZORSKI PRIKAZ, SPEKTAR

$$x(t) = A \cos(\omega t + \varphi)$$
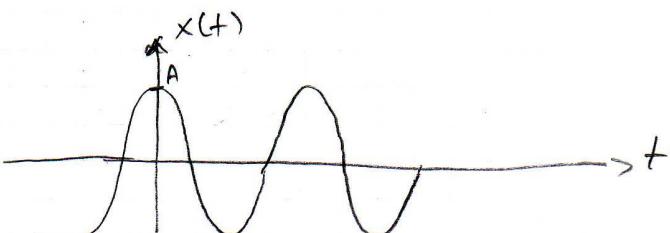
$$x(t) = A \operatorname{Re} \{ e^{i(\omega t + \varphi)} \}$$




Fazorski prikaz

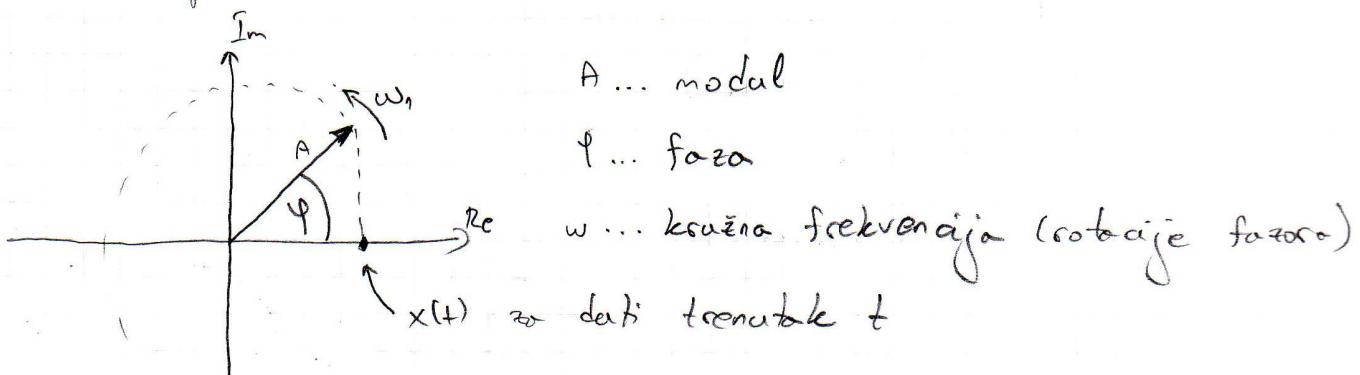


Jednostavni linijski spektar

amplitudi:

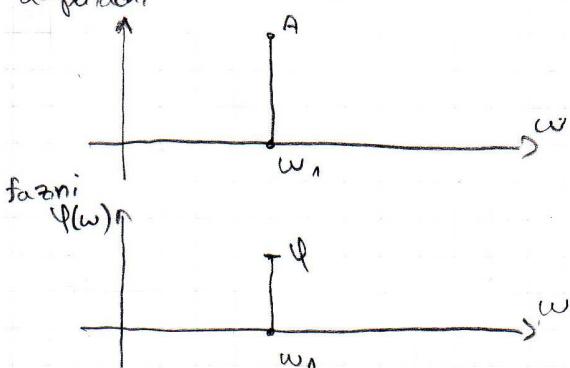

fazni


$\varphi(\omega)$

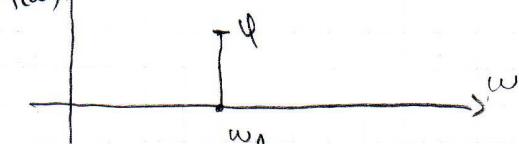

Istih signal


$$x(t) = \frac{1}{2} A e^{j(\omega_1 t + \phi)} + \frac{1}{2} A e^{-j(\omega_1 t + \phi)} = A \cos(\omega_1 t + \phi)$$

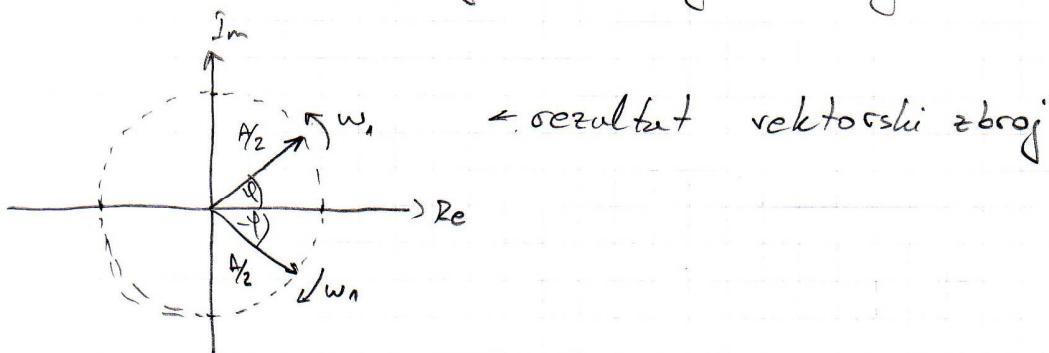dva fazora istih amplituda koji rotiraju u suprotnim smjerovima




Dvostrani linjski spektar

AMP

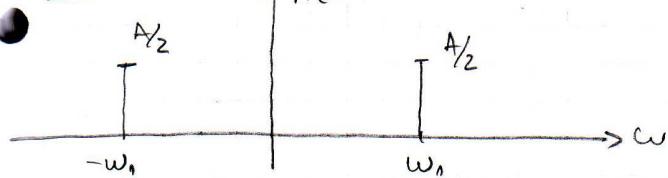


fazni:

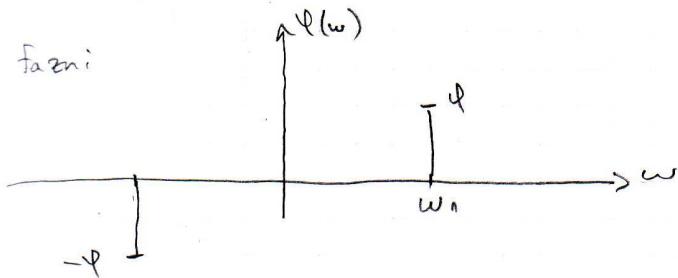

Priječ


$$x(t) = 2 + 6 \cos(2\pi 10t + \frac{\pi}{6}) + 3 \sin(2\pi 30t) - 4 \cos(2\pi 35t)$$

Jednostrani linjski spektar

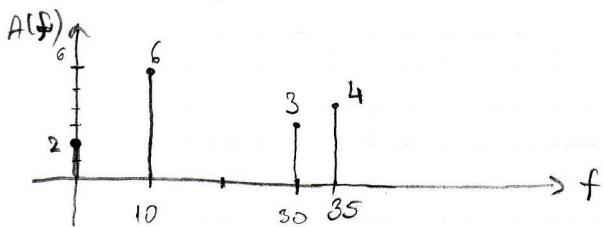

← amplitude su uvijek pozitivne

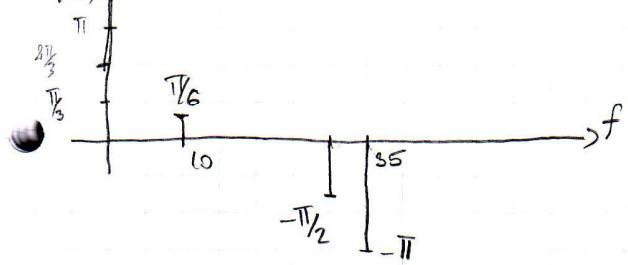
$$3 \sin(2\pi 30t) = 3 \cos(2\pi 30t - \frac{\pi}{2})$$




-uzinano $-\pi$ zbog realnih sustava
koji uvijek imaju kašnjenje.
faza uvijek pada s rastom frekv.

$$-4 \cos(2\pi 35t) = 4 \cos(2\pi 35t - \pi)$$

Dvostrukost

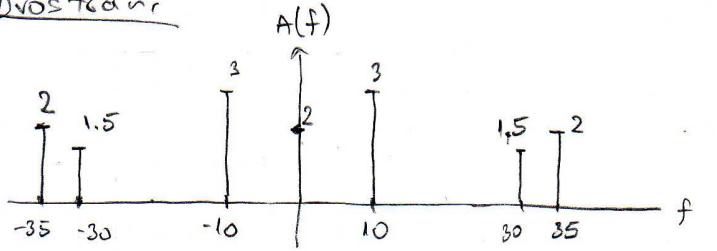

parna funkcija

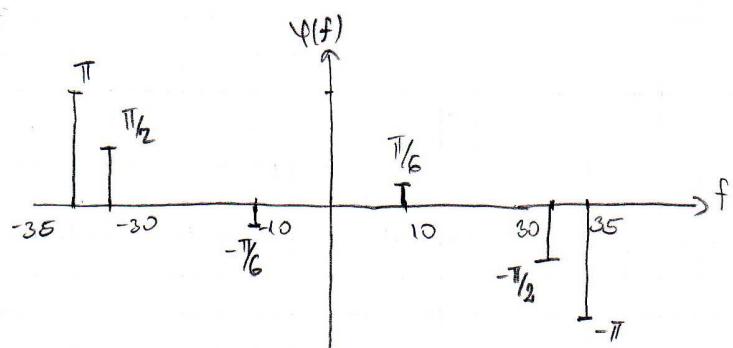

neparna funkcija

FOURIEROV RED

$$f(t) = \sum_{n=-\infty}^{+\infty} F_n \cdot e^{jn\omega_0 t}$$

za periodične signale \rightarrow spektar diskretan
 $, n = 0, \pm 1, \pm 2, \dots$

$$F_n = \frac{1}{T_0} \int_{-\frac{T_0}{2}}^{\frac{T_0}{2}} f(t) \cdot e^{-jn\omega_0 t} dt$$

$$F_n = |F_n| e^{j\phi_n}$$

amplitud \uparrow faze


FOURIEROVA TRANSFORMACIJA

za ne periodične signale \rightarrow spektar kontinuiran.

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) \cdot e^{j\omega t} d\omega \quad \leftarrow \text{inverzna F. transf.} \quad \leftarrow \text{ujek } +j$$

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad \leftarrow \text{ujek ina } -j$$

Princip

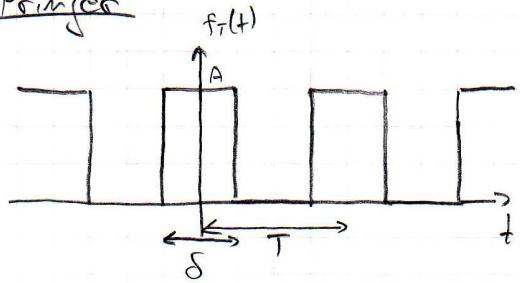


analytická zápis jednoho perioda

$$f_T(t) = \begin{cases} A, & -\delta/2 < t < \delta/2 \\ 0, & \delta/2 < t < T - \delta/2 \end{cases}$$

$$f_T(t) = \sum_{n=-\infty}^{+\infty} F_n e^{j\omega_0 t}$$

$$F_n = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f_T(t) e^{-j\omega_0 n t} dt = \frac{1}{T} \int_{-\frac{\delta}{2}}^{\frac{\delta}{2}} A e^{-j\omega_0 n t} dt = \frac{1}{T} \frac{A}{j\omega_0 n} e^{-j\omega_0 n t} \Big|_{-\frac{\delta}{2}}^{\frac{\delta}{2}} = \frac{A\delta}{T} \frac{\sin(n\omega_0 \frac{\delta}{2})}{n\omega_0 \frac{\delta}{2}}$$

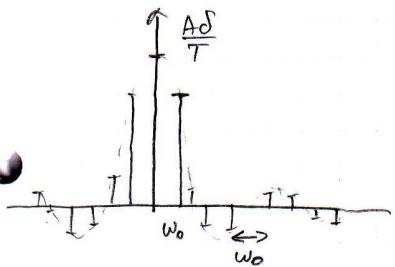

$$\omega_0 = \frac{B\pi}{T}$$

kad $T \rightarrow \infty \Rightarrow \omega_0 \rightarrow 0$

↳ neperiodický signál → kont. spektrum

odlaci F. integrála

$$F(\omega) = \int_{-\infty}^{+\infty} f(t) e^{-j\omega t} dt$$

modul i faza
↓ ↘

$$F(\omega) \text{ komplexna} \Rightarrow F(\omega) = F_{Re}(\omega) + j F_{Im}(\omega) = |F(\omega)| e^{j\varphi(\omega)}$$

$$F(\omega) = \int_{-\infty}^{+\infty} f(t) e^{-j\omega t} dt = \int_{-\infty}^{+\infty} f(t) [\cos(\omega t) - j \sin(\omega t)] dt =$$

$$= \int_{-\infty}^{+\infty} f(t) \cos(\omega t) dt - j \int_{-\infty}^{+\infty} f(t) \sin(\omega t) dt = F_{Re}(\omega) + j F_{Im}(\omega)$$

$$F_{Re}(\omega) = |F(\omega)| \cos(\varphi(\omega))$$

$$F_{Im}(\omega) = |F(\omega)| \sin(\varphi(\omega))$$

1. $f(t)$ komplexní:

$$f(t) = f_{Re}(t) + j f_{Im}(t)$$

$$F(\omega) = \int_{-\infty}^{+\infty} [f_{Re}(t) + j f_{Im}(t)] [\cos(\omega t) - j \sin(\omega t)] dt =$$

$$= \underbrace{\int_{-\infty}^{+\infty} [f_{Re} \cos(\omega t) + f_{Im} \sin(\omega t)] dt}_{F_{Re}(\omega)} - j \underbrace{\int_{-\infty}^{+\infty} [f_{Re} \sin(\omega t) - f_{Im} \cos(\omega t)] dt}_{j F_{Im}(\omega)}$$

$$f_R = \frac{1}{2\pi} \int_{-\infty}^{+\infty} [F_R(\omega) \cos(\omega t) - F_i(\omega) \sin(\omega t)] d\omega$$

$$f_I(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} [F_R(\omega) \sin(\omega t) + F_i(\omega) \cos(\omega t)] d\omega$$

Specijalni slučajevi

a) $f(t)$ realna

$$f(t) = f_R(t), \quad f_i(t) = 0$$

$$F_R(\omega) = \int_{-\infty}^{+\infty} f(t) \cos(\omega t) dt, \quad F_i(\omega) = - \int_{-\infty}^{+\infty} f(t) \sin(\omega t) dt$$

$$F_R(-\omega) = F_R(\omega), \quad F_i(-\omega) = -F_i(\omega)$$

$$F(-\omega) = *F(\omega)$$

Inverzna transf.

$$f_i(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} \underbrace{[F_R(\omega) \sin(\omega t)]}_{\text{NEPARNA}} + \underbrace{[F_i(\omega) \cos(\omega t)]}_{\text{NEPARNA}} d\omega = 0$$

integral neparne funkcije po simetričnom intervalu jednak je 0
zbog jednakih površina na obe strane

$$f_R(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} \underbrace{[F_R(\omega) \cos(\omega t)]}_{\text{PARNA}} - \underbrace{[F_i(\omega) \sin(\omega t)]}_{\text{PARNA}} d\omega = \frac{1}{\pi} \int_0^{+\infty} [F_R(\omega) \cos(\omega t) - F_i(\omega) \sin(\omega t)] d\omega$$

b) $f(t)$ imaginarno

$$f(t) = j f_i(t), \quad f_R(t) = 0$$

$$F_R(\omega) = \int_{-\infty}^{+\infty} f_i(t) \sin(\omega t) dt$$

$$F_R(\omega) = \int_{-\infty}^{+\infty} f_i(t) \cos(\omega t) dt$$

$$F_R(-\omega) = -F_R(\omega)$$

$$F_i(-\omega) = F_i(\omega)$$

$$F(-\omega) = -*F(\omega)$$

c) $f(t)$ parna

$$f_p(-t) = f_p(t)$$

$$F_R(\omega) = \int_{-\infty}^{+\infty} f_p(t) \cos(\omega t) dt = 2 \int_0^{+\infty} f_p(t) \cos(\omega t) dt$$

$$F_i(\omega) = - \int_{-\infty}^{+\infty} f_p(t) \sin(\omega t) dt = 0$$

Inverzna

$$f_p(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} F_r(\omega) \cos(\omega t) d\omega = \frac{1}{\pi} \int_0^{+\infty} F_r(\omega) \cos(\omega t) d\omega$$

PARNA

d) $f(t)$ neparna

$$f_N(-t) = -f_N(t)$$

$$F_r(\omega) = \int_{-\infty}^{+\infty} f_N(t) \cos(\omega t) dt = 0$$

$$F_i(\omega) = - \int_{-\infty}^{+\infty} f_N(t) \sin(\omega t) dt = -2 \int_0^{+\infty} f_N(t) \sin(\omega t) dt$$

c) $f(t)$ realna funkcija kao suma parne i neparne


$$f(t) = f_p(t) + f_N(t)$$

$$f(-t) = f_p(-t) + f_N(-t) = f_p(t) - f_N(t)$$

$$\Rightarrow f_p(t) = \frac{f(t) + f(-t)}{2}, \quad f_N(t) = \frac{f(t) - f(-t)}{2}$$

Prijer

$$f(t) = e^{-t} \sin t$$

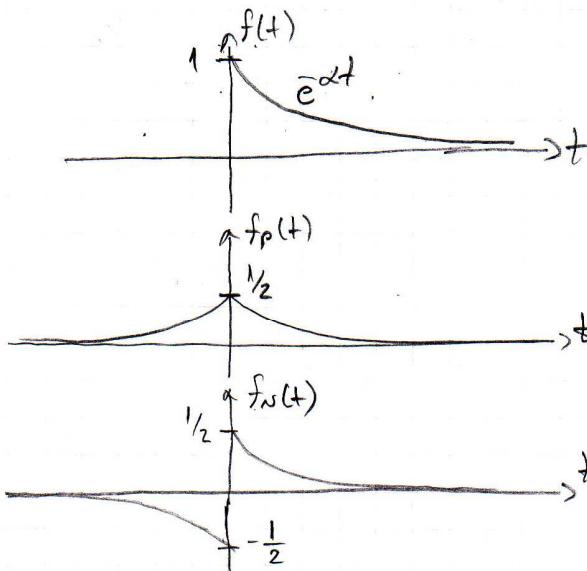

$$f(t) = 2f_p(t), \quad t > 0$$

$$f(t) = 2f_N(t), \quad t > 0$$

$$f(t) \rightarrow F_r(\omega) + jF_i(\omega)$$

$$f_p(t) \rightarrow F_r(\omega)$$

$$f_N(t) \rightarrow jF_i(\omega)$$

$$F_r(\omega) = \frac{1}{2} \int_0^{+\infty} f_p(t) \cos(\omega t) dt$$

$$F_i(\omega) = -\frac{1}{2} \int_0^{+\infty} f_N(t) \sin(\omega t) dt$$

$$f_p(t) = \frac{1}{\pi} \int_0^{+\infty} F_r(\omega) \cos(\omega t) d\omega$$

$$f_N(t) = -\frac{1}{\pi} \int_0^{+\infty} F_i(\omega) \sin(\omega t) d\omega$$


KAUZALNOST

f) $f(t)$ kauzalan

$$f(t) = 0 \quad , t < 0$$

onda vrijedi

$$f(-t) = 0 \quad , t > 0$$

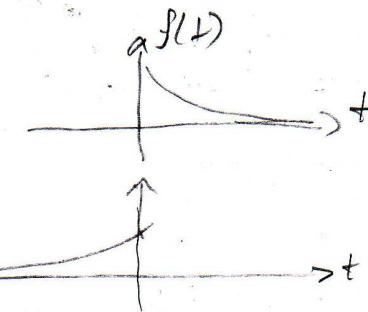

$$f(t) = 2f_p(t) \quad , t > 0$$

$$f(t) = 2f_n(t) \quad , t > 0$$

$$f(t) = \frac{2}{\pi} \int_0^{\infty} F_R(\omega) \cos(\omega t) d\omega = -\frac{2}{\pi} \int_0^{\infty} F_i(\omega) \sin(\omega t) d\omega$$

$$F_i(\omega) = -\int_{-\infty}^{+\infty} f(t) \sin(\omega t) dt = -\int_0^{+\infty} f(t) \sin(\omega t) dt$$

zalog / kauzalnost

$$F_R(\omega) = -\frac{2}{\pi} \int_0^{+\infty} F_i(y) \cos y + \sin y dt$$

$$F_R(\omega) = -\frac{2}{\pi} \int_0^{+\infty} F_i(y) \sin y t \cos \omega t dy$$

računajući Im spektra preko Re.

SVOJSTVA FOURIEROVIH TRANSFORMACIJA

$$\mathcal{F}[a_1 f_1(t) + a_2 f_2(t)] = a_1 F_1(\omega) + a_2 F_2(\omega)$$

simetrična

$$\mathcal{F}[f(t)] = F(t) \Rightarrow \mathcal{F}[f(-t)] = 2\pi f(-\omega)$$

$$\mathcal{F}[f(at)] = \frac{1}{a} F\left(\frac{\omega}{a}\right)$$

Dokaz

$$\mathcal{F}[f(t-t_0)] = F(\omega) e^{-j\omega t_0}$$

$$\mathcal{F}[f(t) e^{j\omega_0 t}] = F(\omega - \omega_0)$$

$$\mathcal{F}\left[\frac{df(t)}{dt}\right] = j\omega F(\omega) - f(0)$$

$$\mathcal{F}\left[\frac{d^n f(t)}{dt^n}\right] = (j\omega)^n F(\omega) - (j\omega)^{n-1} f(0) - (j\omega)^{n-2} f'(0) \dots$$

$$\mathcal{F}\left[\int_{-\infty}^t f(t) dt\right] = \frac{F(\omega)}{j\omega}$$

$$\mathcal{F}\left[\frac{d^n F(\omega)}{d\omega^n}\right] = (jt)^n f(t)$$

$$\mathcal{F} \{ f(t) * g(t) \} = F(\omega) \cdot G(\omega)$$

$$f(t) * g(t) = \int_{-\infty}^{+\infty} f(\tau) g(t - \tau) d\tau$$


$$\mathcal{F} [f(t) \cdot g(t)] = \frac{1}{2\pi} F(\omega) * G(\omega)$$

singulare Funktionen


$$\int_{-\infty}^{+\infty} \delta(t) dt = 1$$

$$\int_{-\infty}^{+\infty} \delta(t) \phi(t) dt = \phi(0)$$


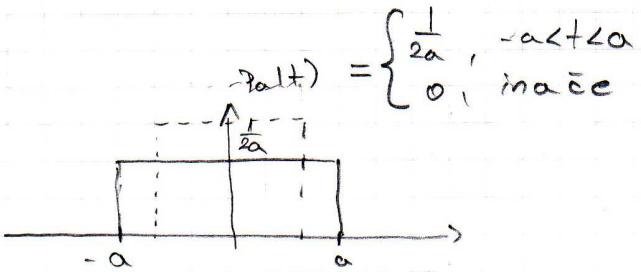
$$\int_{-\infty}^{+\infty} \delta(t-t_0) \phi(t) dt = \phi(t_0)$$






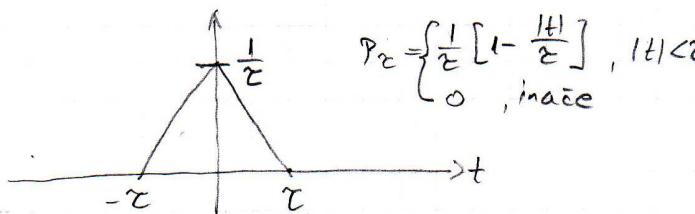
$$\delta(t) = \lim_{a \rightarrow 0} p_a(t) = \lim_{a \rightarrow 0} \frac{1}{2a} [S(t+a) - S(t-a)]$$


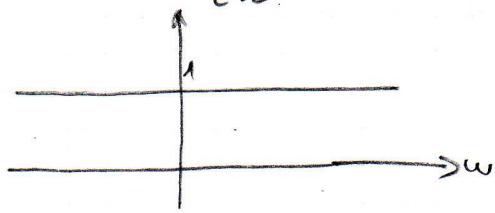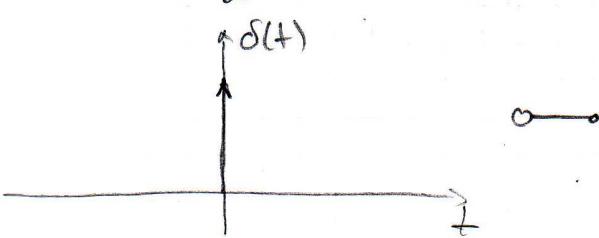
$$\mathcal{F} [\delta(t)] = \int_{-\infty}^{+\infty} \delta(t) e^{-j\omega t} dt = 1$$




$$\mathcal{F} [k\delta(t)] = k$$

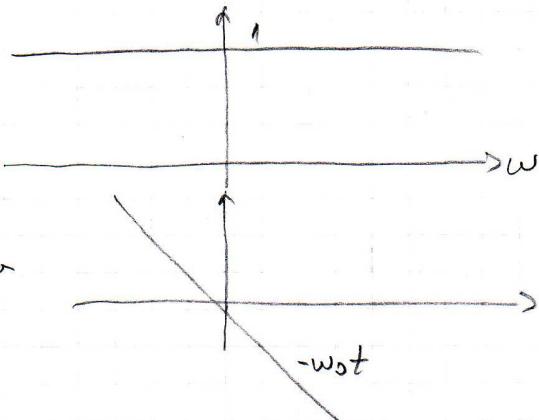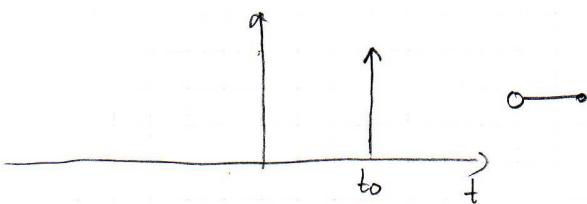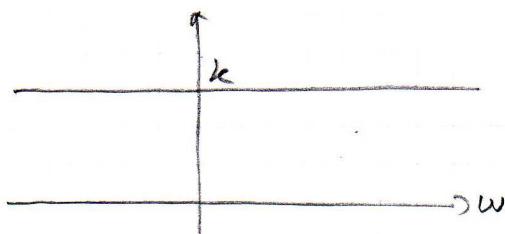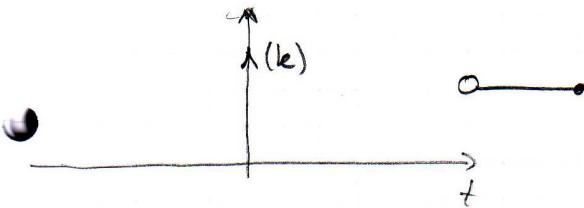

pomak u vrijeme i fazu samo pomak fazu.


-w_0 t

$$f(t) = k$$

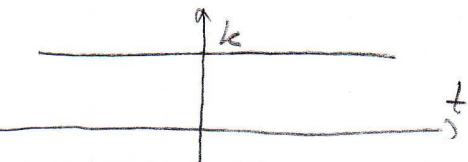

teogen
duamost
G


$$F(\omega) = 2\pi k \delta(\omega)$$

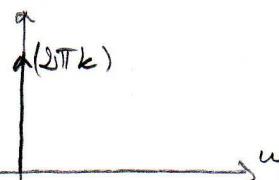

$$f(t) = k e^{j\omega_0 t}$$

$$F(\omega) = 2\pi k \delta(\omega - \omega_0)$$


o

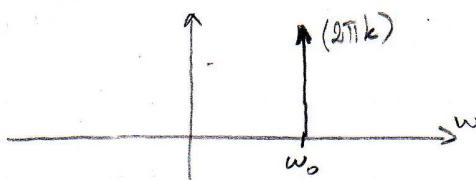

$$f(t) = \cos(\omega_0 t)$$

$$\rightarrow F(\omega) = \pi \delta(\omega + \omega_0) + \pi \delta(\omega - \omega_0)$$

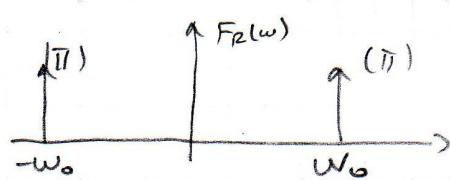
$$\cos(\omega t) = \frac{1}{2} (e^{j\omega t} + e^{-j\omega t})$$




$$f(t) = \sin(\omega_0 t)$$

$$\rightarrow F(\omega) = [\pi \delta(\omega - \omega_0) - \pi \delta(\omega + \omega_0)]$$
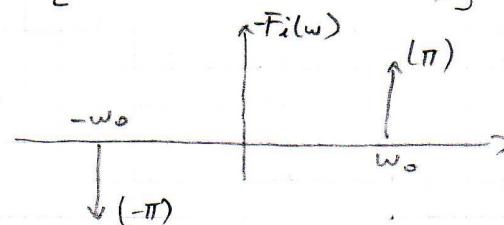
$$\sin(\omega_0 t) = \frac{1}{j2} (e^{j\omega_0 t} - e^{-j\omega_0 t})$$


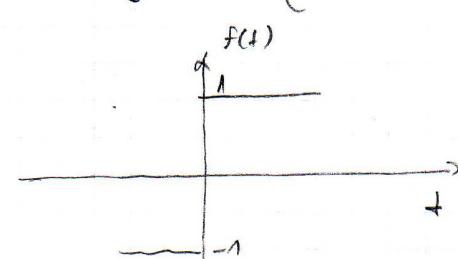
$$f(t) = \text{sgn}(t) = \begin{cases} 1, & t > 0 \\ -1, & t < 0 \end{cases}$$



$$\rightarrow \mathcal{F}[f(+)] = \frac{2}{j\omega} = j \frac{2}{\omega}$$


provjeravamo paroci inverzne

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} F(\omega) e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\infty}^{+\infty} \frac{2}{j\omega} e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\infty}^{+\infty} \frac{2}{j\omega} [\cos(\omega t) + j\sin(\omega t)] d\omega =$$

NEP

PARNA

$$= \frac{2}{\pi} \int_0^{+\infty} \frac{\sin \omega t}{\omega} d\omega = \left| \int_0^{\infty} \frac{\sin \omega t}{\omega} d\omega \right|_{\text{NEP.}} = \begin{cases} 1, & t > 0 \\ -1, & t < 0 \end{cases}$$

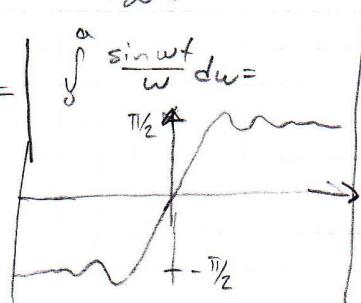


Heaviside step funkcija

$$s(t) = \begin{cases} 1 & , t > 0 \\ 0 & , t < 0 \end{cases}$$



$$s(t) = \frac{1}{2} + \frac{1}{2} \operatorname{sgn}(t)$$
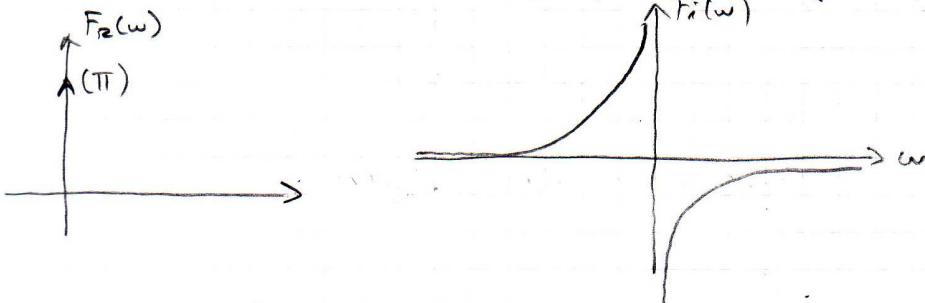
$$\mathcal{F}\{s(t)\} = \frac{1}{2} \cdot 2\pi \delta(\omega) + \frac{1}{2} \cdot \frac{1}{j\omega} = \pi \delta(\omega) + \frac{1}{j\omega} = \pi \delta(\omega) - j \frac{1}{\omega} = F_R(\omega) + j F_I(\omega)$$



fekv. karakter. i odziv sustava

$$H(\omega) = H_R(\omega) + j H_I(\omega) = |H(\omega)| e^{j\varphi(\omega)} = A(\omega) e^{j\varphi(\omega)} \rightarrow \boxed{H(\omega)}$$

$$\text{atenuacija } \alpha(\omega) = -\ln A(\omega)$$

$$\text{fazno kusnjenje } \theta(\omega) = -\varphi(\omega)$$

$$H(\omega) = e^{-\alpha(\omega)} e^{-j\theta(\omega)}$$

Impulsni odziv

$$f(t) = \delta(t)$$

$$g(t) = f(t) * h(t) = \int_{-\infty}^{\infty} f(\tau) h(t - \tau) d\tau \rightarrow G(\omega) = H(\omega) \cdot F(\omega) = 1 \cdot H(\omega)$$

$$\mathcal{F}[G(\omega)] = g(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} H(\omega) e^{j\omega t} d\omega = h(t) \leftarrow \text{impulsni odziv}$$

$$h(t) = h_r(t) + j h_i(t)$$

Skokoviti odziv

$$f(t) = s(t)$$

$$G(\omega) = (\pi \delta(\omega) - \frac{j}{\omega}) H(\omega)$$

$$g(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} (\pi \delta(\omega) - j \frac{1}{\omega}) H(\omega) e^{j\omega t} d\omega$$

približno određivanje odziva

$$g(t) = \int_{-\infty}^{+\infty} f(t-\tau) h(\tau) d\tau$$

$$f(t-\tau) \approx f(t)$$


za uski vremenski interval

$$g(t) \approx \int_{-\infty}^{+\infty} f(t) h(\tau) d\tau = f(t) \int_{-\infty}^{+\infty} h(\tau) d\tau = f(t) \int_{-\infty}^{+\infty} h(\tau) e^{j\omega t} d\tau = f(t) \cdot H(0)$$

$$h(t-\tau) = h(t) \quad \text{na kraćkom intervalu}$$

$$g(t) = \int_{-\infty}^{+\infty} f(\tau) h(t-\tau) d\tau = \int_{-\infty}^{+\infty} f(\tau) h(t) d\tau = h(t) \int_{-\infty}^{+\infty} f(\tau) d\tau = h(t) \cdot \int_{-\infty}^{+\infty} f(\tau) d\tau$$

Idealizirani sustavi

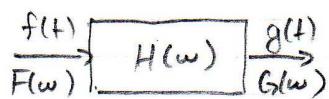


$$f(t) = g(t) \Rightarrow F(\omega) = G(\omega)$$

$$H(\omega) = 1, A(\omega) = 1, \Theta(\omega) = 0$$

↳ ne unosi kašnjenje signala

$$G(j\omega) = F(j\omega) \cdot H(j\omega) = A \cdot F(j\omega)$$

idealni NP filter

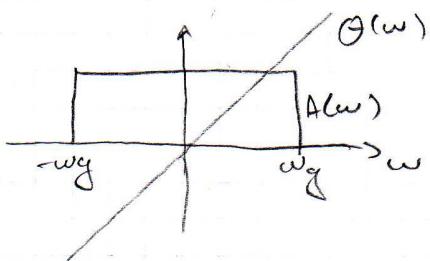

Sustav bez izobljeđenja



- ima linearne fazne karakteristike.

$$H(j\omega) = A(\omega) e^{j\varphi(\omega)}$$

$A(\omega) = k_0$ - konstanta

$$\varphi(\omega) = -t_d \cdot \omega$$
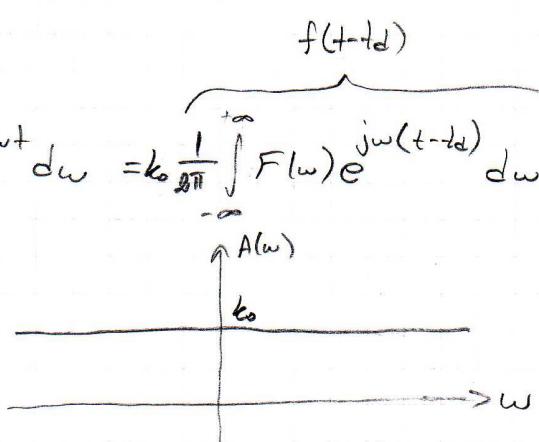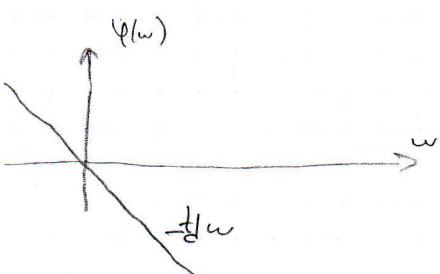
$$g(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} A(\omega) e^{j\varphi(\omega)} \cdot F(\omega) e^{j\omega t} d\omega = k_0 \frac{1}{2\pi} \int_{-\infty}^{+\infty} F(\omega) e^{j\omega(t-t_d)} d\omega = k_0 \cdot f(t-t_d)$$




Amplitudno skalar
i ponaknuto u
vremenu

- linearne izobličenja nastaju kad karakter. odstupaju od prethodne.


- ne nastaju novi harmonici, nastaju samo amplitudna i faza izobličenja.

Nelinearna izobličenja

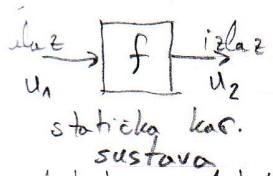

(amplitudno-amplitudna)
nelinearna

$$u_2 = f(u_1)$$

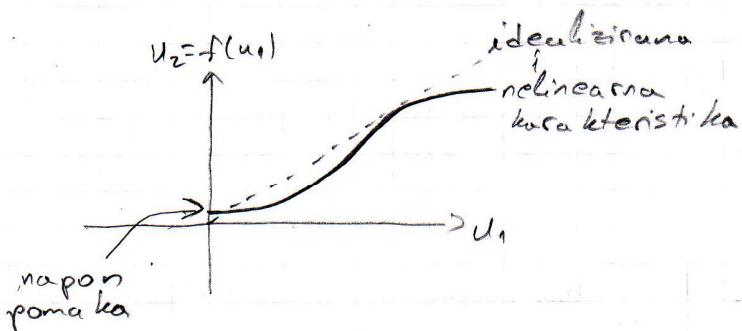

Primer:

$$u_2 = a_0 + a_1 u_1 + a_2 u_1^2 + a_3 u_1^3$$

Ako je $u_1 = U_1 \sin(\omega t)$

$$\begin{aligned} u_2 &= a_0 + a_1 U_1 \sin(\omega t) + a_2 U_1^2 \sin^2(\omega t) + a_3 U_1^3 \sin^3(\omega t) = \\ &= a_0 + a_1 U_1 \sin(\omega t) + \frac{a_2}{2} U_1^2 - \frac{1}{2} a_2 U_1^2 \cos(2\omega t) + \frac{3}{4} a_3 U_1^3 \sin(\omega t) - \frac{a_3}{4} U_1^3 \sin(3\omega t) = \\ &= a_0 + \frac{1}{2} U_2 U_1^2 + (a_1 U_1 + \frac{3}{4} a_3 U_1^3) \sin(\omega t) - \frac{a_2}{2} U_1^2 \cos(2\omega t) - \frac{a_3}{4} U_1^3 \sin(3\omega t) \end{aligned}$$

novi harmonici

Ako je $u_1 = U_1 \sin(\omega_1 t) + U_2 \sin(\omega_2 t)$

$$u_2 = a_0 + a_1 U_1 + a_2 U_1^2$$

↓

$$\begin{aligned} u_2 &= a_0 + a_1 U_1 \sin(\omega_1 t) + a_1 U_2 \sin(\omega_2 t) + \frac{a_2}{2} U_1^2 + \frac{a_2}{2} U_2^2 - \frac{a_2}{2} U_1^2 \cos(2\omega_1 t) - \frac{a_2}{2} U_2^2 \cos(2\omega_2 t) + \\ &\quad + \frac{a_2}{2} U_1 U_2 \cos(\omega_1 - \omega_2)t + \frac{a_2}{2} U_1 U_2 \cos(\omega_1 + \omega_2)t \end{aligned}$$


Uz ω_1 i ω_2 imamo još: DC, $2\omega_1$, $2\omega_2$, $\omega_1 - \omega_2$, $\omega_1 + \omega_2$

Faktor nelinearnog izobličenja - total harmonic distortion - THD

THD (D)

$$\text{THD} = \sqrt{\frac{A_2^2 + A_3^2 + \dots + A_n^2}{A_1^2}} \leftarrow \begin{array}{l} \text{amplitude ostalih harmonika} \\ \text{amplitude osnovnog harmonika} \end{array}$$

IDEALNI NP FILTAR

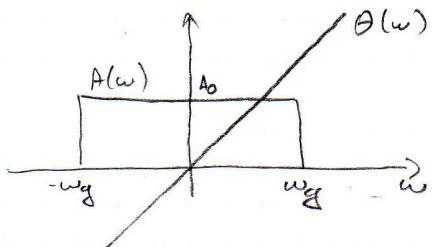

$$A(\omega) = \begin{cases} A_0, & -\omega_g < \omega < \omega_g \\ 0, & \text{inace} \end{cases}$$

$$\Theta(\omega) = \omega \cdot t_0$$

$$H(\omega) = A_0 \cdot e^{j\omega t_0} \cdot p_{wg}(\omega)$$


↑ proces na intervalu $[\omega_g]$

impulsni odziv

$$h(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} H(\omega) e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\omega_g}^{\omega_g} A_0 e^{j\omega t_0} e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\omega_g}^{\omega_g} A_0 e^{j\omega(t-t_0)} d\omega = \frac{A_0}{\pi} \int_0^{\omega_g} e^{j\omega(t-t_0)} d\omega =$$


$$= \frac{A_0}{\pi} \int_0^{\omega_g} (\cos(\omega(t-t_0)) + j \sin(\omega(t-t_0))) d\omega = \frac{A_0}{\pi} \int_0^{\omega_g} \underbrace{\cos(\omega(t-t_0))}_{\text{neparno komponente}} d\omega = \frac{A_0}{\pi} \omega_g \frac{\sin \omega_g(t-t_0)}{\omega_g(t-t_0)}$$

IMPULSNI ODZIV
IDEALNOG NP FILTRA

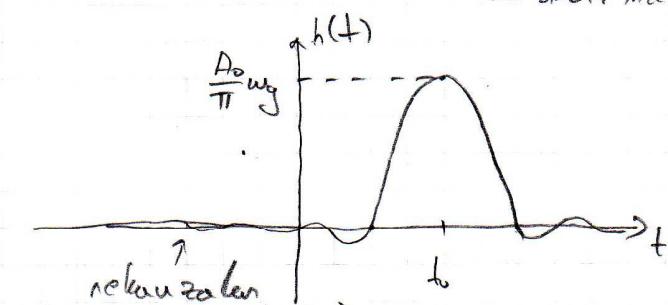

rekursivni
(odziv nije poduce)
nemoguce realizacije

VP filter

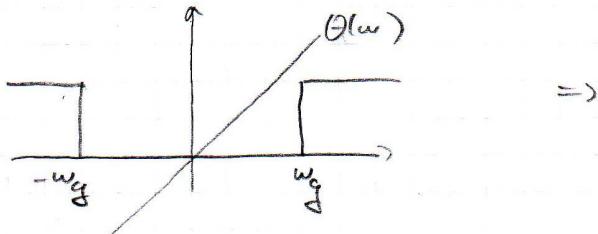

=>

$$\Psi(\omega) = -\Theta(\omega)$$




f_{02} f_{02}
fazni koefficijenti

HILBERTOVA TRANSFORMACIJA

$$H(\omega) = H_r(\omega) + j H_i(\omega)$$

$$H_i(\omega) = -\frac{1}{\pi} \int_{-\infty}^{+\infty} \frac{H_r(y)}{\omega - y} dy, \quad H_r = \frac{1}{\pi} \int_{-\infty}^{+\infty} \frac{H_i(y)}{\omega - y} dy$$

kauzalna funkcija

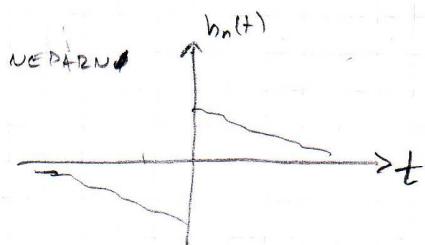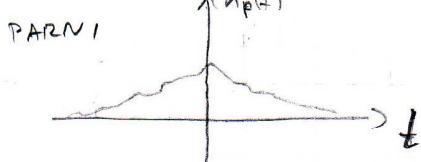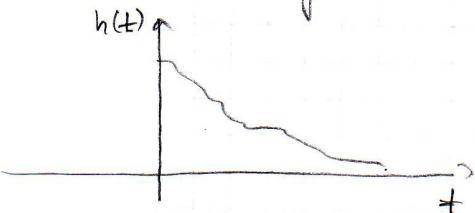

impulzni odziv nekog kauzalog sustava

$$\begin{aligned} h_p(t) &= h_n(t), \quad t > 0 \\ h_p(t) &= -h_n(t), \quad t < 0 \end{aligned} \quad \left. \right\} \Rightarrow \begin{aligned} h_p(t) &= h_n(t) \cdot \text{sig}(t) \\ h_n(t) &= h_p(t) \cdot \text{sig}(t) \end{aligned}$$

$h_p(t) \rightarrow H_r(\omega)$
$h_n(t) \rightarrow j H_i(\omega)$

$$f(t) \cdot g(t) \xrightarrow{\text{FT}} \frac{1}{2\pi} F(\omega)^* G(\omega) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} F(y) G(\omega - y) dy$$




$$\text{sgn}(t) \rightarrow \frac{2}{j\omega}$$

$$j H_i(\omega) = \frac{1}{2\pi} \cdot H_r(\omega) * \frac{2}{j\omega} = \frac{1}{j\pi} \int_{-\infty}^{+\infty} H_r(y) \frac{1}{\omega - y} dy = -j \frac{1}{\pi} \int_{-\infty}^{+\infty} \frac{H_r(y)}{\omega - y} dy$$


$$\Rightarrow H_i(\omega) = -\frac{1}{\pi} \int_{-\infty}^{+\infty} \frac{H_r(y)}{\omega - y} dy$$

VEZA između A i f karakteristike

- općenito nije jednoznačna

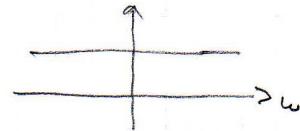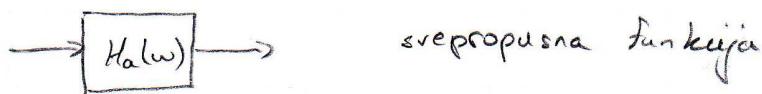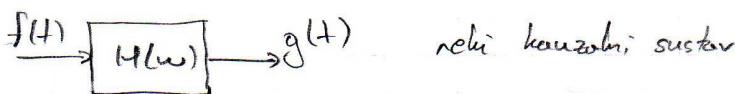

- formirano kaskader

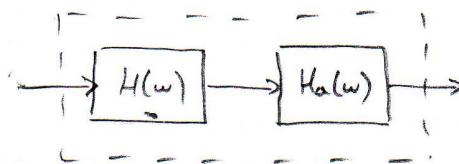

$$H_u(w) = H(w) \cdot H_a(w)$$

$$\hookrightarrow |H(w)| e^{j\varphi(w)}$$

$$\hookrightarrow |H_a(w)| e^{j\varphi_a(w)}$$

$$\Rightarrow H_u(w) = |H(w)| e^{j(\varphi(w) + \varphi_a(w))} = |H(w)| e^{j\varphi_u(w)}$$



sustavi s minimumom faze

- za njih se može odrediti jednoznačna veza A if karakteristike.

- oni koji se nemogu rastaviti na produkt $H(jw)$: propusne funkcije

- kako utvrditi da se radi o sustavu s minimumom faze?

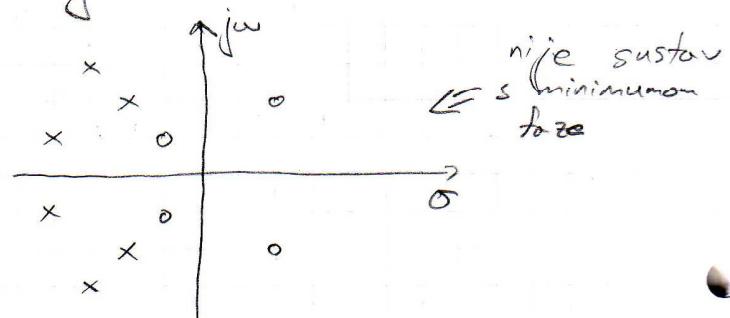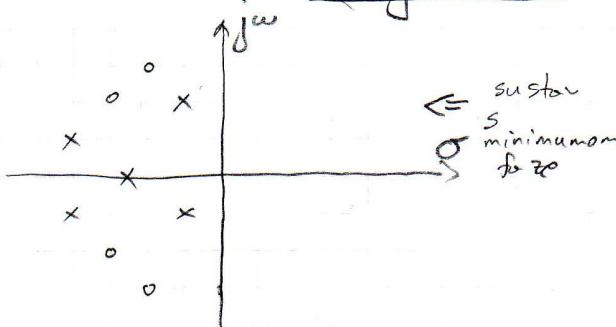- ti sustavi renaju nula u desnoj ravnini



$$H(w) = \frac{-\alpha(w) - j\Theta(w)}{|H(w)|}$$

$\alpha(w)$ - log. mješač amp. karakter.

veza između $\alpha(w)$ i $\Theta(w)$:

$$\Theta(w) = \frac{w}{\pi} \int_{-\infty}^{+\infty} \frac{\alpha(y)}{y^2 - w^2} dy$$

$$\alpha(w) = \alpha(0) - \frac{w^2}{\pi} \int_{-\infty}^{+\infty} \frac{\Theta(y)}{y(y^2 - w^2)} dy$$


DEFINICIJA

- za danu amp. karakter. može se tijekom realizirati forme karakter. s mini. faze, tj. ne može se očekivati mješač faza koštanjegje od ovog, koje radi sustav s minimumom faze.

- Možuće su i druge faz. karakter. uz zadane amp. karakter. no ova dva imaju već deblju težnju nad ostalim s min. faze.

Izračunati gusgeye $\angle(\omega)$ filtra s prijen. funkc. minim. baze, i AF kvalit.

$$\Theta(\omega) = \begin{cases} \text{to } \omega, & |\omega| < \omega_c \\ \text{to } \omega_c, & \omega > \omega_c \end{cases}$$

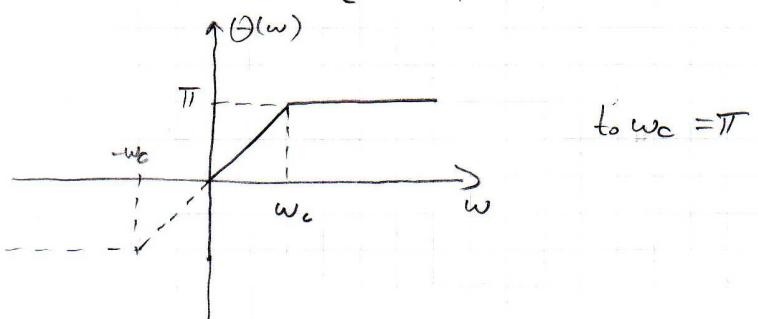

rijedi Hilbertova transf.


$$\angle(\omega) = \angle(0) - \frac{\omega^2}{\pi} \int_{-\infty}^{+\infty} \frac{\Theta(y)}{y(y^2 - \omega^2)} dy =$$

$$= \angle(0) - \frac{\omega^2}{\pi} \int_{-\infty}^{\omega_c} \frac{-\text{to } \omega_c}{y(y^2 - \omega^2)} dy - \frac{\omega^2}{\pi} \int_{-\omega_c}^{\omega_c} \frac{\text{to } y}{y(y^2 - \omega^2)} dy - \frac{\omega^2}{\pi} \int_{\omega_c}^{+\infty} \frac{\text{to } \omega_c}{y(y^2 - \omega^2)} dy =$$


$$\left\{ \begin{array}{l} \int \frac{dy}{y(y^2 - \omega^2)} = \frac{1}{2\omega^2} \ln \left| 1 - \frac{\omega^2}{y^2} \right| \\ \int \frac{dy}{y^2 - \omega^2} = \frac{1}{2\omega} \ln \left| \frac{y - \omega}{y + \omega} \right| \end{array} \right\}$$

$$= \angle(0) + \frac{\text{to } \omega_c}{\pi} \left[\left(1 + \frac{\omega}{\omega_c} \right) \ln \left| 1 + \frac{\omega}{\omega_c} \right| + \left(1 - \frac{\omega}{\omega_c} \right) \ln \left| 1 - \frac{\omega}{\omega_c} \right| \right]$$

$$A(\omega) = e^{-\angle(\omega)}$$

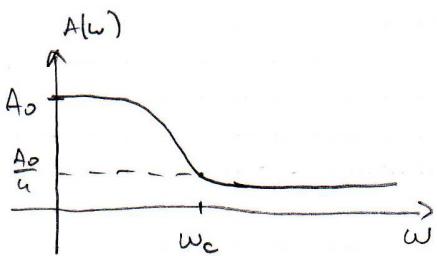

Primeros 2

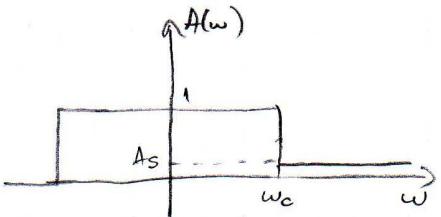


$$A(\omega) = \begin{cases} 1 & |\omega| \leq \omega_c \\ A_s & |\omega| > \omega_c \end{cases}$$


$$\Theta(\omega) = ?$$

$$H(\omega) = e^{-\alpha(\omega) - j\theta(\omega)} = A(\omega) e^{j\theta(\omega)} \quad A(\omega) = e^{-\alpha(\omega)} \Rightarrow \alpha(\omega) = \ln \frac{1}{A(\omega)}$$

$$\Theta(\omega) = \frac{\omega}{\pi} \int_{-\infty}^{+\infty} \frac{\alpha(y)}{y^2 - \omega^2} dy = \frac{\omega}{\pi} \int_{-\infty}^{+\infty} \frac{-\ln A(y)}{y^2 - \omega^2} dy = -\frac{\omega}{\pi} \int_{-\infty}^{-\omega_c} \frac{\ln A_s}{y^2 - \omega^2} dy - \frac{\omega}{\pi} \int_{-\omega_c}^{\omega_c} \frac{\ln 1}{y^2 - \omega^2} dy - \frac{\omega}{\pi} \int_{\omega_c}^{+\infty} \frac{\ln A_s}{y^2 - \omega^2} dy = \dots = -\frac{\ln A_s}{\pi} \ln \left| \frac{\omega - \omega_c}{\omega + \omega_c} \right|$$

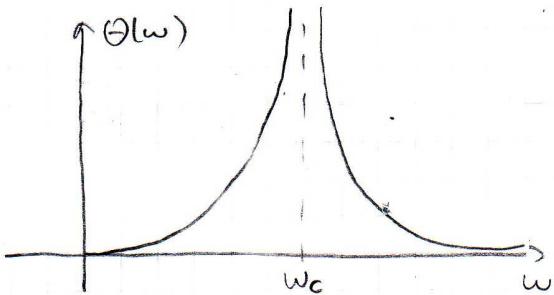

1.

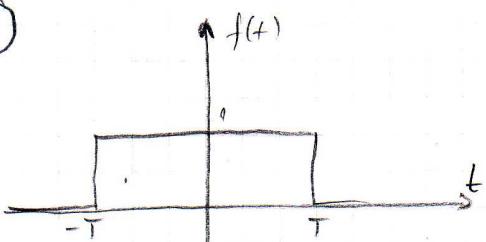


$$F(\omega) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} f(t) e^{j\omega t} dt$$

$$f(t) \text{ parcia } \Rightarrow F(\omega) = F_p(\omega) = \int_{-\infty}^{+\infty} f_p(t) \cos(\omega t) dt$$

$$= 2 \int_0^{\infty} f_p(t) \cos(\omega t) dt = 2 \frac{\sin(\omega T)}{\omega} \Big|_0^T = 2 \frac{\sin(\omega T)}{\omega T}$$


2.

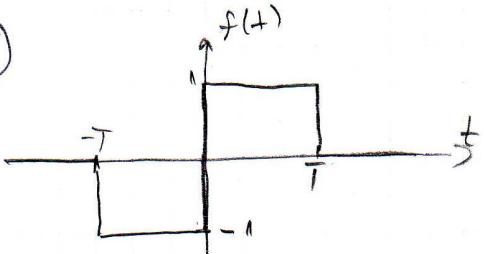

$$F(\omega) = -j F_i(\omega)$$

$$F_i(\omega) = - \int_{-\infty}^{+\infty} f_i(t) \sin \omega t dt = -2 \int_0^T \sin \omega t dt = -\frac{2}{\omega} (\cos \omega - 1)$$

3.

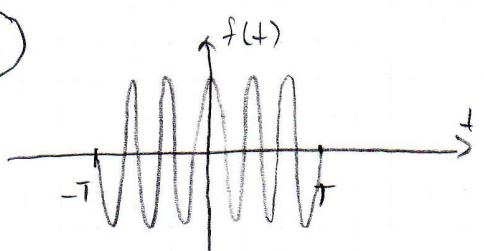


$$f(t) = f_0(t) \cos(\omega_0 t)$$

$$F(\omega) = \int_{-\infty}^{+\infty} f(t) \cos \omega t e^{-j\omega t} dt = \int_{-T}^T \cos(\omega_0 t) e^{-j\omega t} dt = \int_{-T}^T \frac{1}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t}) e^{-j\omega t} dt = \frac{1}{2}$$


$$= \frac{1}{2} \int_{-T}^{+T} e^{j(\omega - \omega_0)t} + e^{-j(\omega + \omega_0)t} dt =$$
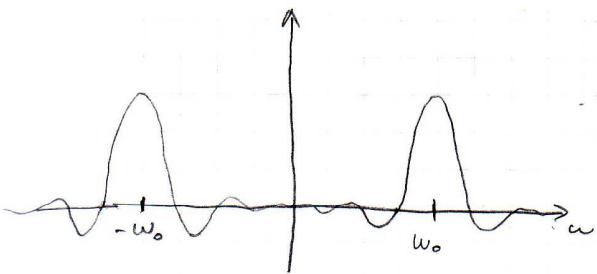
$$F(\omega) = \frac{e^{-j(\omega - \omega_0)T}}{2j(\omega - \omega_0)} - \frac{e^{-j(\omega + \omega_0)T}}{2j(\omega + \omega_0)} = \frac{\sin(\omega - \omega_0)T}{\omega - \omega_0} + \frac{\sin(\omega + \omega_0)T}{\omega + \omega_0}$$



ZADATAK

odrediti $\mathcal{F}\{f(t)\}$

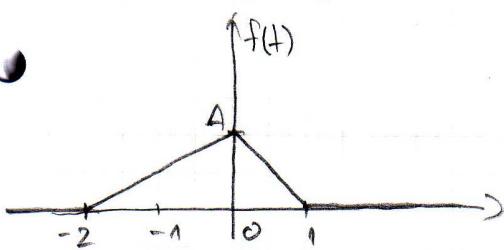

$$F(\omega) = ?$$

$$F_r(\omega) = ?$$

$$F_i(\omega) = ?$$

$$f(t) = \begin{cases} \frac{A}{2}t + A, & -2 \leq t \leq 0 \\ -A - \frac{A}{2}t, & 0 < t \leq 1 \end{cases}$$

$$\begin{aligned} F(\omega) &= \int_{-\infty}^{+\infty} f(t) e^{-j\omega t} dt = \int_{-2}^0 \left(\frac{A}{2}t + A \right) e^{-j\omega t} dt + \int_0^1 \left(-A - \frac{A}{2}t \right) e^{-j\omega t} dt = \\ &= \frac{A}{2} \int_{-2}^0 t e^{-j\omega t} dt - \frac{A}{j\omega} \int_{-2}^0 e^{-j\omega t} dt - \frac{A}{j\omega} \int_0^1 e^{-j\omega t} dt - A \int_0^1 t e^{-j\omega t} dt = \\ &= \frac{A}{2} \left[\frac{-j\omega t}{(j\omega)^2} (-j\omega t - 1) \right]_{-2}^0 + j \frac{A}{\omega} (1 - e^{j2\omega}) - A \left[\frac{e^{-j\omega t}}{(j\omega)^2} (-j\omega t - 1) \right]_0^1 + \\ &+ j \frac{A}{\omega} [e^{j\omega} - 1] = \end{aligned}$$

$$= \frac{A}{2} \left[\frac{1}{-\omega^2} (-1) - \frac{e^{j2\omega}}{-\omega^2} (2j\omega - 1) \right] + j \frac{A}{\omega} (e^{j\omega} - e^{j2\omega}) - A \left[\frac{e^{-j\omega}}{-\omega^2} (-j\omega - 1) + \frac{1}{\omega^2} \right] =$$


$$= \frac{A}{2\omega^2} + \cancel{\frac{A}{\omega^2} e^{j2\omega}} - \cancel{\frac{A}{\omega^2} e^{j4\omega}} - \frac{A}{2} \frac{e^{j\omega}}{\omega^2} + j \frac{A}{\omega} e^{j\omega} - \cancel{j\frac{A}{\omega} e^{j2\omega}} - \cancel{A \frac{e^{j\omega}}{\omega^2} j\omega} - A \frac{e^{j\omega}}{\omega^2} + \frac{A}{\omega^2} =$$

$$= \frac{3A}{2\omega^2} - \frac{A}{2\omega^2} [\cos 2\omega + j \sin 2\omega] - \frac{A}{\omega^2} (\cos \omega - j \sin \omega) =$$


$$= \frac{3A}{2\omega^2} - \frac{A}{2\omega^2} \cos 2\omega - \frac{A}{\omega^2} \cos \omega - j \frac{A}{2\omega^2} \sin 2\omega + j \frac{A}{\omega^2} \sin \omega =$$

$$= \underbrace{\frac{A}{2\omega^2} (3 - \cos 2\omega - 2 \cos \omega)}_{F_r(\omega)} + j \underbrace{\frac{A}{2\omega^2} (-\sin 2\omega + 2 \sin \omega)}_{F_i(\omega)}$$

2. NAČIN

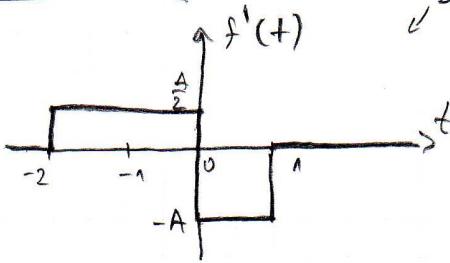

Derivacija

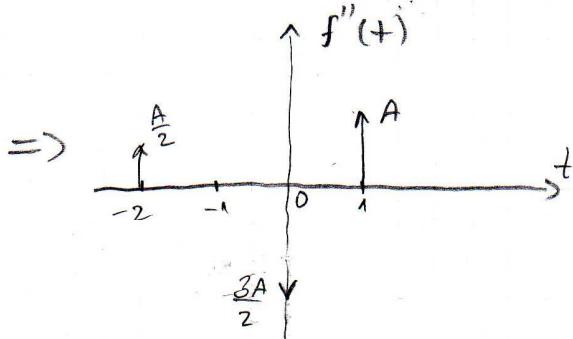

$$\frac{d^{(n)} f(t)}{dt^n} \longrightarrow (j\omega)^n \cdot F(\omega)$$

$$\delta(t-t_0) \longrightarrow e^{-j\omega t_0} \cdot 1$$

$$f''(t) \longrightarrow (j\omega)^2 \cdot F(\omega) = -\omega^2 F(\omega)$$


$$f''(t) = \frac{A}{2} \delta(t+2) - \frac{3A}{2} \delta(t) + A \delta(t-1)$$

$$-\omega^2 F(\omega) = \frac{A}{2} e^{j2\omega} - \frac{3A}{2} + A e^{j\omega}$$

$$\Rightarrow F(\omega) = \frac{3A}{2\omega^2} - \frac{A}{2\omega^2} e^{j2\omega} \rightarrow \frac{A}{\omega^2} e^{-j\omega} = \underbrace{\frac{A}{2\omega^2} (3 - \cos 2\omega - 2\cos \omega)}_{F_c(\omega)} + j \underbrace{\frac{A}{2\omega^2} (\sin 2\omega + \sin \omega)}_{F_i(\omega)}$$

POJASALA

Naponsko pojačalo

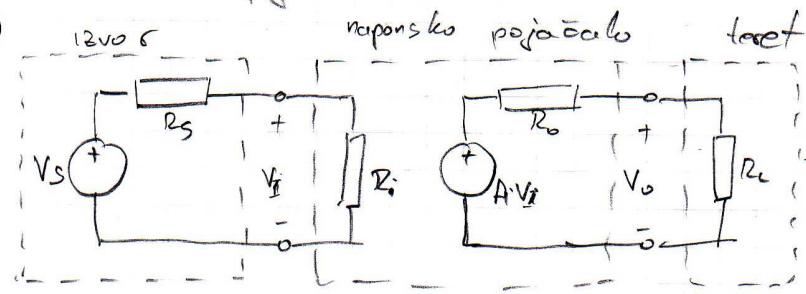

$$V_I = \frac{R_i}{R_s + R_i} V_S$$

$$V_o = A_{oc} \cdot V_I \cdot \frac{R_L}{R_o + R_L}$$

$$\frac{V_o}{V_S} = \frac{R_i}{R_s + R_i} A_{oc} \frac{R_L}{R_o + R_L}$$

↑ ↑


FAKTORI OPTEREDENJA
ULAZNOG I IZLAZNOG STUPNJA

A_{oc} - amplificatio in open circuit
(pojačanje pri otvorenom kolu)

$$R_i \gg R_s \Rightarrow V_I \approx V_S$$

$$R_o \rightarrow 0 \Rightarrow V_o \approx A_{oc} V_I$$

Stotino pojačalo

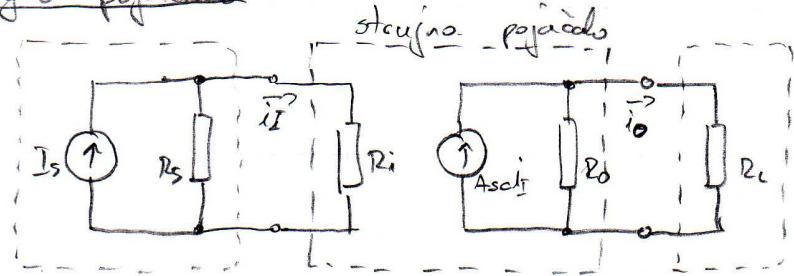

$$\frac{i_O}{i_S} = \frac{R_L}{R_s + R_i} A_{oc} \frac{R_o}{R_o + R_L}$$

A_{sc} - short-circuit current gain



$$R_i \rightarrow 0 \Rightarrow i_S \approx i_I$$

$$R_o \rightarrow \infty \Rightarrow i_O \approx A_{sc} i_I$$


input + output +

V_I	V_o	naponsko stotino
i_I	i_o	
V_I	i_o	naponsko stotino
i_I	V_o	

Operacijsko pojačalo

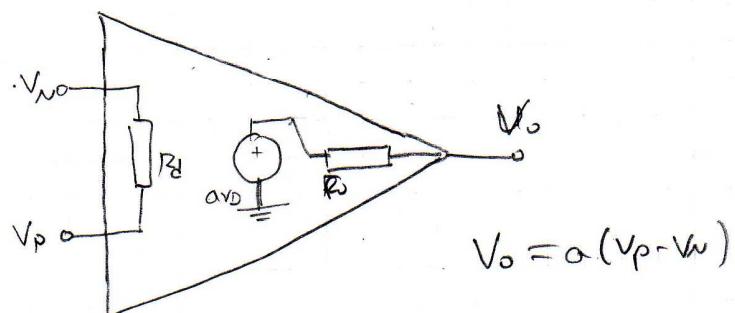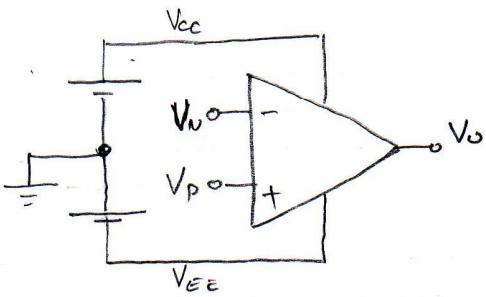

idealno

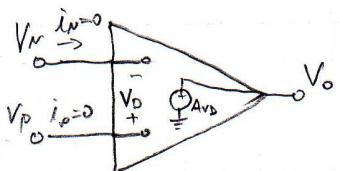

$$\alpha \rightarrow \infty$$

$$r_d = \infty$$



$$g_o = 0$$

$$i_p = i_n = 0$$

$$\frac{V_o}{\alpha} = V_p - V_N \Rightarrow V_p = V_N$$

OSNOVNE KONFIGURACIJE

Neinvertirajuće pojačalo

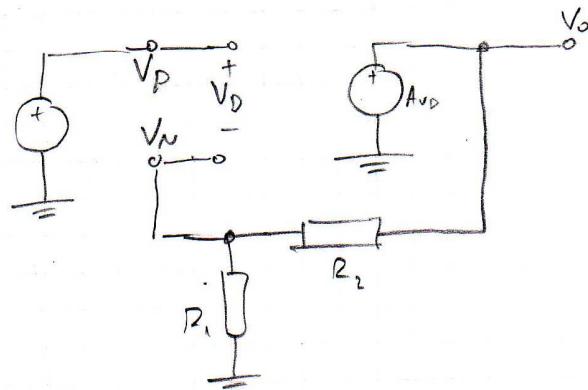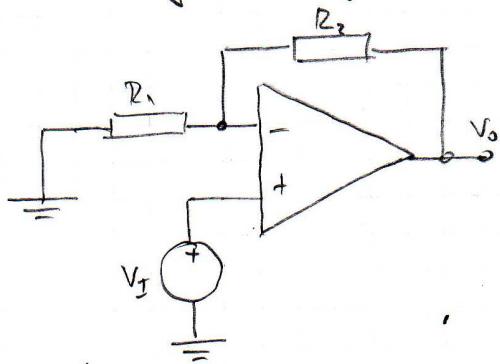

$$V_p = V_I$$

$$V_N = \frac{R_1}{R_1 + R_2} \cdot V_o$$

$$V_o = a(V_p - V_N) = a(V_I - V_o \frac{R_1}{R_1 + R_2}) \Rightarrow \frac{V_o}{V_I} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{1 + \frac{R_2/R_1}{a}}$$

a je konstanan

$$A_{IDEALNO} \Rightarrow \lim_{a \rightarrow \infty} \frac{V_o}{V_I} = 1 + \frac{R_2}{R_1}$$

$$R_i = \infty, R_o = 0$$

Primer

$$V_I = 1V$$


$$R_1 = 2k\Omega$$

$$R_2 = 18k\Omega$$

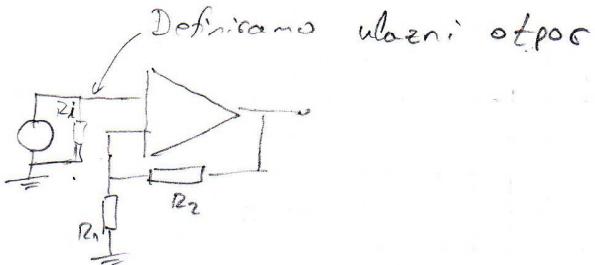
- a) $\alpha = 10^2 [V/V]$
 b) $\alpha = 10^4$
 c) $\alpha = 10^6$
-

$V_o = ?$

$$R_i = \frac{V_i}{I_p} = \infty \quad , \quad R_o = R_{out} = 0$$



Invertirajuće pojačalo

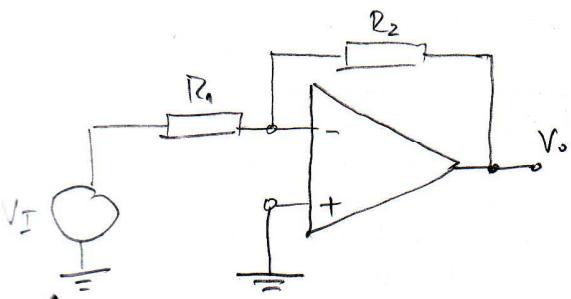

$$R_i = R_1$$

$$R_o = 0$$

$$V_p = 0$$


$$V_N = \frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_o$$

$$V_o = \alpha(V_p - V_N) = \alpha \left(-\frac{R_2}{R_1 + R_2} V_i - \frac{R_1}{R_1 + R_2} V_o \right)$$

$$A = \frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{R_1/R_2}{\alpha}}$$


$$A_{IDEAL} = \lim_{\alpha \rightarrow \infty} A = -\frac{R_2}{R_1}$$

Sumirajuće pojačalo

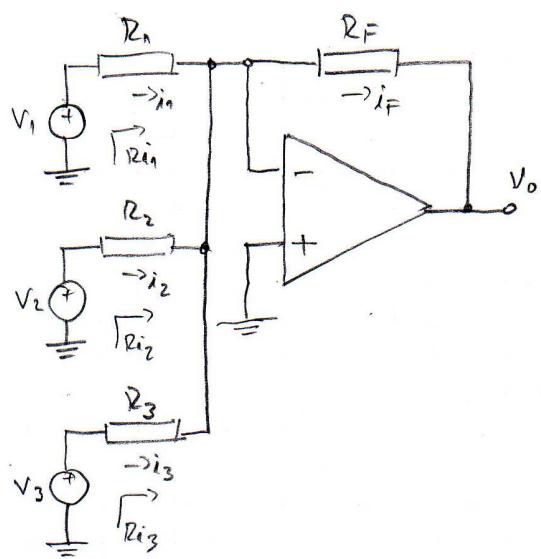

$$i_F = i_1 + i_2 + i_3$$

Diferencijsko pojačalo

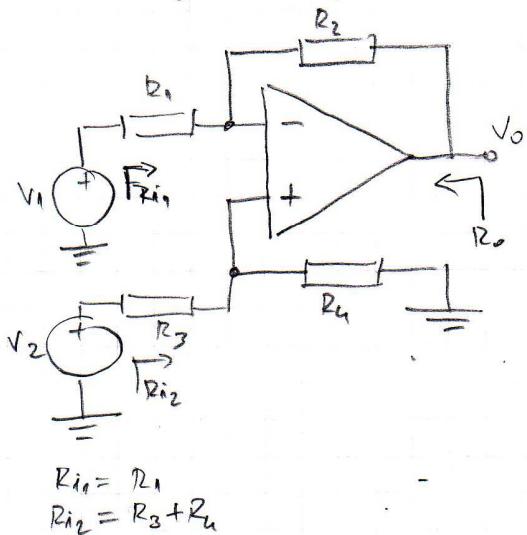

$$R_{i1} = R_1$$

$$R_{i2} = R_2 + R_u$$


$$V_0 = V_{01} + V_{02}$$

$$V_0 = \frac{R_2}{R_1} \left(\frac{1 + \frac{R_0}{R_2}}{1 + \frac{R_3}{R_4}} V_2 - V_1 \right)$$


$$\frac{R_3}{R_4} = \frac{R_1}{R_2} \Rightarrow V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

$\frac{R_2}{R_1} \leftarrow$ Diferencijsko
pojačanje
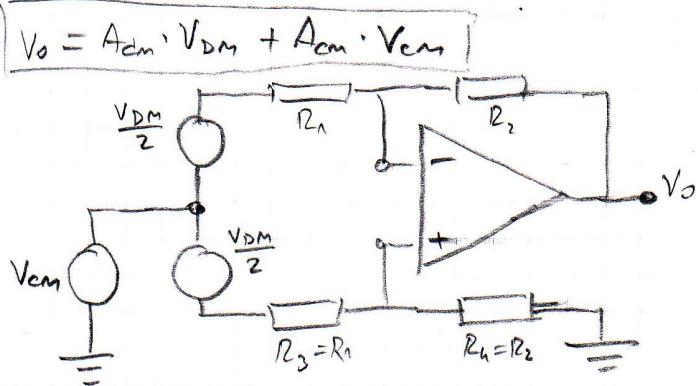
$$\left. \begin{array}{l} V_{DM} = V_2 - V_1 \\ V_{CM} = \frac{V_1 + V_2}{2} \end{array} \right\} \Rightarrow \begin{array}{l} V_1 = V_{CM} - \frac{V_{DM}}{2} \\ V_2 = V_{CM} + \frac{V_{DM}}{2} \end{array}$$



Razgođeni kruž

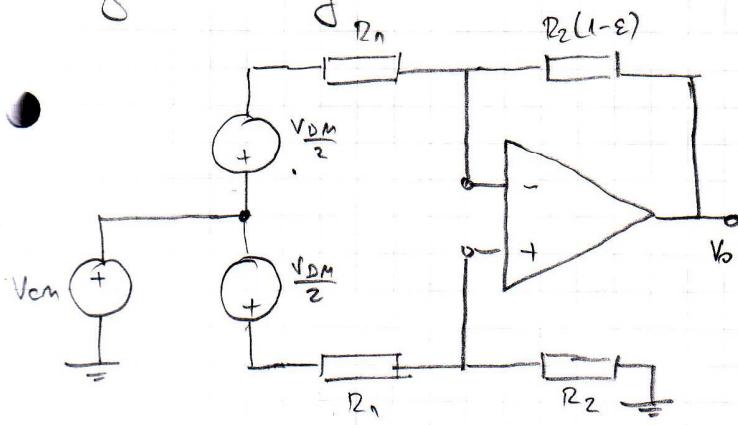

$$A_{dm} = \frac{R_2}{R_1} \left(1 - \frac{R_1 + 2R_2}{R_1 + R_2} \cdot \frac{\epsilon}{2} \right)$$

$$A_{cm} = \frac{R_2}{R_1 + R_2} \cdot \epsilon$$

↑ unosi nam istočarne komponente (neželjena)

$$CMRR_{dB} = 20 \log \left| \frac{A_{dm}}{A_{cm}} \right|$$

$$\text{za } \epsilon \rightarrow 0 \Rightarrow A_{dm} = \frac{R_2}{R_1}$$


$$A_{cm} = 0$$

$$R_{id} = 2R_1$$

$$R_{ic} = \frac{R_1 + R_2}{2}$$

ULAZNI OTPORI


T mreža u posrednoj verziji

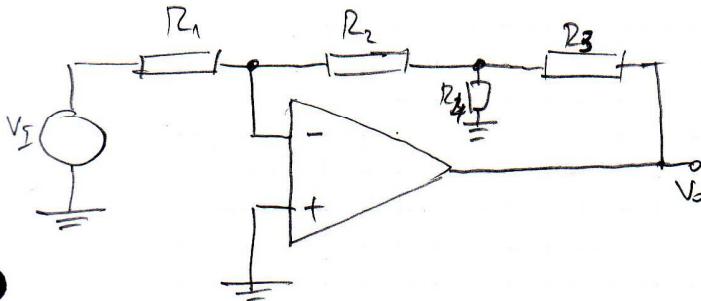

$$A = \frac{V_o}{V_\Sigma} = -\frac{R_2 + R_3 + R_2 \frac{R_3}{R_4}}{R_1}$$

zbog nepohrpetljivih izlaza
otpada konstrukcije T mreža

Priimek 1

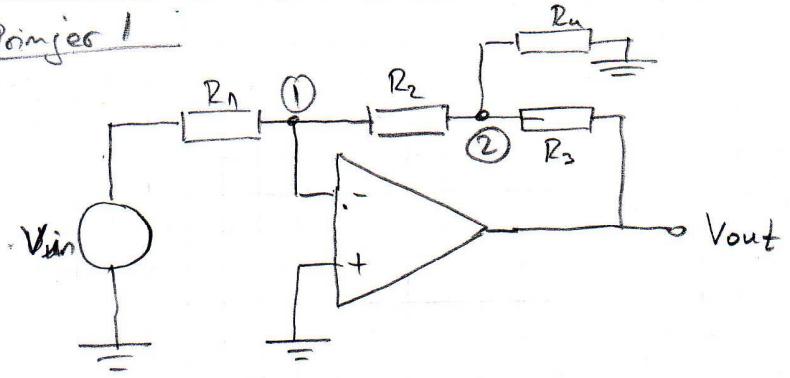

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \frac{1}{R_2} = \frac{V_{in}}{R_1}$$

$$-V_1 \frac{1}{R_2} + V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_L} \right) = \frac{V_{out}}{R_3}$$

$V_1 = 0$ (virtualni KS)

$$V_2 = -\frac{R_2}{R_1} V_{in}$$

$$-V_{in} \frac{R_2}{R_1} \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_L} \right) = \frac{V_{out}}{R_3}$$

$$\Rightarrow V_{out} = -V_{in} \frac{\frac{R_2 R_3}{R_2 + R_3 + R_L}}{R_1}$$

$$R_{ul} = R_1$$

$$A = -\frac{R_2 + R_3 + \frac{R_2 R_3}{R_L}}{R_1}$$

ZAHTEV

$R_{ul} = 100 k\Omega$
$A = -100$


\Rightarrow za klasična povratna vezu (samo R_2) otpor bi morao iznositi $10 M\Omega$ što je previše

Za T mrežu

$$R_1 = 100 k\Omega$$


$$R_2 = R_3 = 100 k\Omega$$

$$R_L = 1 k\Omega \Rightarrow A = -\frac{100 + 100 + \frac{100 \cdot 100}{1}}{100} = -102 \approx -100$$

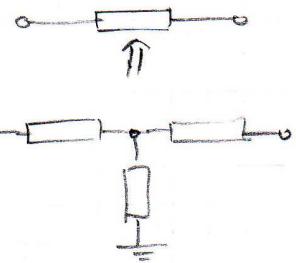

Primer 2

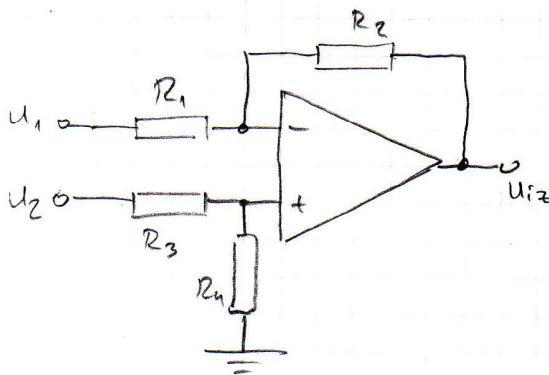- Na crtežu shemice dif. pos. je operac. pojač. i odrediti iznos otpora, naminalno pojačanje 10. Na raspolaganju su dve otpornice toles. $\pm 1\%$ nagubice i iznosa otpora 100kΩ slučaju.
- Kolika je pojačanje istosmjernog i; diferencijalnog u njenopogodnjem slučaju.



$$U_{iz} = -\frac{R_2}{R_1} U_1 + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) U_2$$

$$U_d = U_2 - U_1, \quad U_i = \frac{U_1 + U_2}{2}$$

$$U_1 = U_2 - \frac{U_d}{2}, \quad U_2 = U_2 + \frac{U_d}{2}$$

IDEALNO

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} \Rightarrow U_{iz} = \frac{R_2}{R_1} (U_2 - U_1)$$

$$A_D = 10 = \frac{R_2}{R_1} \quad R_2 = 100 \text{ k}\Omega \Rightarrow R_1 = 10 \text{ k}\Omega$$

$$\begin{aligned} R_1 &= R_3 = 10 \text{ k}\Omega \\ R_2 &= R_4 = 100 \text{ k}\Omega \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} A_N = 10$$

$$\rho = \pm 1\%$$

Najnepovoljniji slučaj:

$$\left(\frac{R_2}{R_1}\right)_{\min} \quad \left(\frac{R_4}{R_3}\right)_{\max}$$

$$\Downarrow$$

$$\Downarrow$$

$$\frac{R_2(1-\rho)}{R_1(1+\rho)}$$

$$\frac{R_4(1+\rho)}{R_3(1-\rho)}$$

$$U_{iz} = -\frac{R_2}{R_1} \left(U_i - \frac{U_d}{2}\right) + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) \left(U_i + \frac{U_d}{2}\right)$$

$$U_{iz} = U_i \underbrace{\frac{1}{2} \left[\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) \right]}_{A_d} + U_i \underbrace{\left[-\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) \right]}_{A_i}$$

Najgoriči slučaj:
 $R_1' = 10,1 \text{ k}\Omega$
 $R_2' = 99 \text{ k}\Omega$
 $R_3' = 9,9 \text{ k}\Omega$
 $R_4' = 101 \text{ k}\Omega$

$$\text{za } p = 1\%$$

$$\frac{R_2}{R_1} = 9,80198$$


$$\frac{R_L}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) = 0,91073 \cdot 10,80198 = 9,83769$$

$$A_d = 9,82 \approx 10$$

$$A_i = 0,0357 \approx 0$$

$$F = 20 \log \frac{A_d}{A_i} = 48,8 \text{ dB}$$

Sustav s negativnom povratnom vezom

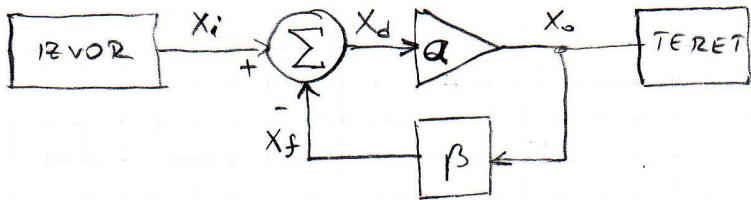

$$x_o = \alpha x_d$$

$$x_d = x_i - x_f$$

$$x_f = x_o \beta$$

$$x_o = \alpha(x_i - x_f) = \alpha(x_i - \beta x_o)$$

$$\Rightarrow x_o = \frac{\alpha}{1 + \alpha \beta} x_i \Rightarrow A = \frac{x_o}{x_i} = \frac{\alpha}{1 + \alpha \beta}$$

$\alpha \beta = T$ ← pojačanje petlje


$$\lim_{\alpha \rightarrow \infty} A = \lim_{\alpha \rightarrow \infty} \frac{\alpha}{1 + \alpha \beta} = \lim_{\alpha \rightarrow \infty} \frac{1}{\frac{1}{\alpha} + \beta} = \frac{1}{\beta} = A_{\text{ideal}}$$

↑ za beskonačno pojačanje

$$A = A_{\text{IDEAL}} \cdot \frac{1}{1 + \frac{1}{\alpha \beta}}$$

- utjecaj ulaznog i izlaznog otpora OP

- neinvertirajuće

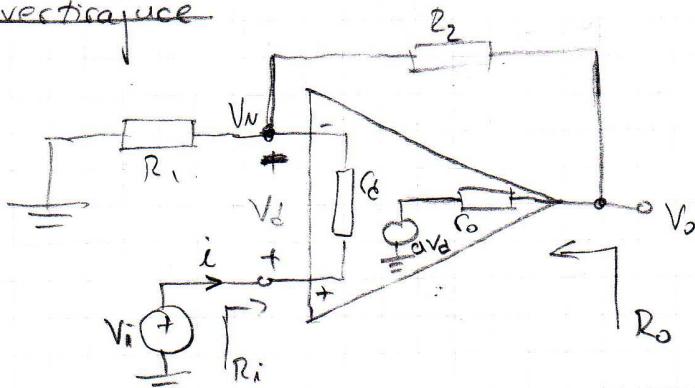

$$\frac{V_i - V_N}{R_1} - \frac{V_N}{R_1} + \frac{V_O - V_N}{R_2} = 0$$

$$\frac{V_N - V_O}{R_2} + \frac{\alpha(V_i - V_N) - V_O}{R_2} = 0$$

$$A = \frac{V_o}{V_i} = ? \quad R_i = ? , R_o = ?$$

$$A = \frac{V_o}{V_i} = \frac{\left(1 + \frac{R_2}{R_1}\right)\alpha + \frac{r_o}{r_d}}{1 + \alpha + \frac{R_2}{R_1} + \frac{R_2 + r_o}{r_d} + \frac{r_o}{R_1}}$$

(1)

$$r_o \approx 30\Omega$$

$$r_d \approx 500k - 1M\Omega$$

$$\frac{r_o}{r_d} \ll \text{za dobro dizajnirano}$$

$$\frac{R_2 + r_o}{r_d} \ll$$

$$\frac{r_o}{R_1} \ll$$

$$\Rightarrow A = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \frac{1}{T}} \quad , \quad T = \alpha \beta , \quad \beta = \frac{R_1}{R_1 + R_2}$$

$$R_i = \frac{V_i}{i}$$

$$\frac{V_i - V_N}{r_d} - \frac{V_N}{R_1} + \frac{\alpha(V_i - V_N) - V_N}{R_2 + r_o} = 0$$

$$V_N = V_i - V_d = V_i - i \cdot r_d$$


$$R_i = \underbrace{\left(1 + \frac{\alpha}{1 + \frac{R_2 + r_o}{R_1}}\right)}_{I} \underbrace{(r_d + R_1) \parallel (R_2 + r_o)}_{II}$$

$$\Rightarrow R_i = r_d (1 + \alpha \beta) = r_d (1 + T)$$

$$r_o \ll R_2$$

$$I \gg II \quad \text{za dobar dizajn}$$

Izlazni otpor

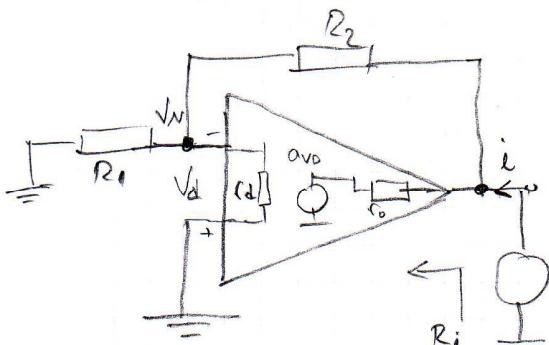

$$V_N = \frac{R_1 \parallel r_d}{(R_1 \parallel r_d) + R_2} \cdot V$$

$$i + \frac{V_N - V}{R_2} + \frac{-\alpha V_N - V}{r_o} = 0$$

$$R_o = \frac{V}{i} = \frac{r_o}{1 + \frac{\alpha + \frac{r_o}{R_1} + \frac{r_o}{r_d}}{1 + \frac{R_2}{R_1} + \frac{R_2}{r_d}}}$$

$$\frac{r_o}{R_1}, \frac{r_o}{r_d}, \frac{R_2}{r_d} \ll$$

$$\Rightarrow R_o = r_o \cdot \frac{1}{1 + T}$$

poratno vezu smanjuje izlazni otpor

Prijev Neinvertirajuća konfiguracija

741 pojačalo
 $A = \frac{250V/mV}{2mV} = 2 \cdot 10^5$
 $R_2 = 2M\Omega$
 $R_o = 75\Omega$

a) $R_1 = 1k\Omega$
 $R_2 = 999k\Omega$

b) sljedilo ($R_1 = \infty$, $R_2 = 0$)

a) $A_{IDEALUO} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} = 1000 ; A = 995,022$

$T = 200$
 $A = 995,024$ ← nakon pojednostavljenog
zanemarenja
(formula s T) (2)

egzaktni rezultat
(velika formula) (1)

$R_{egzaktno} = 401,97M\Omega$, $R_i = 402M\Omega$

$R_{o,IDEAL} = 0$, $R_o = 373,32m\Omega$, $R_o = 373,13m\Omega$
↑
egzaktni ; ↑
aprosks .


b) $T = 200,000$

$A_{IDE} = 1$, $A_T = 0,999995$

$R_{IDE} = \infty$, $R_{iT} = 400G\Omega$

$R_{o,IDE} = 0$, $R_{oT} = 375\mu\Omega$

INVERTIRAJUĆE POJAČALO

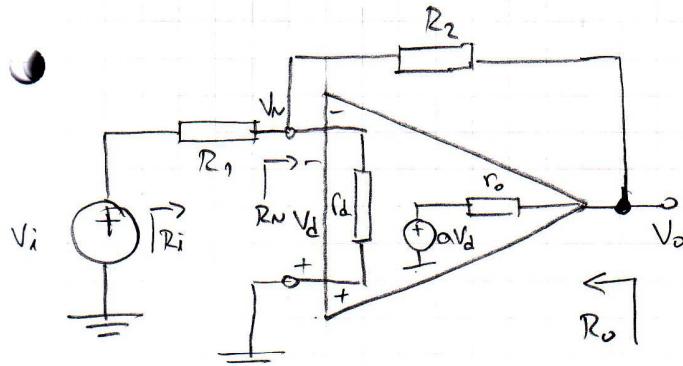


$$A = -\frac{\alpha R_2 - r_o}{(1+\alpha)R_1 + (R_2 + r_o)\left(1 + \frac{R_1}{r_d}\right)}$$

$$r_o \ll R_2, \frac{R_1}{r_d} \ll 1, \alpha R_2 \gg r_o$$

$$\Rightarrow A = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{T}}$$

$$T = \alpha \cdot \beta = \alpha \cdot \frac{R_1}{R_1 + R_2}$$

moga biti
ispunjeno

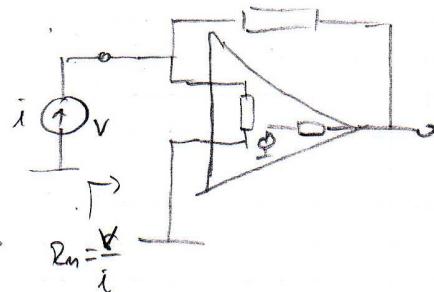

$$R_n = \frac{R_2 + r_o}{1 + \alpha + \frac{R_2 + r_o}{r_d}} \approx \frac{R_2}{1 + \alpha} \quad \text{← smanjenje otpočetka}$$

$$R_i = R_1 + R_n = R_1 + \frac{R_2 + r_o}{1 + \alpha + \frac{R_2 + r_o}{r_d}}$$

$$R_o \approx \frac{r_o}{1 + T} \quad \text{← smanjenje otpočetka}$$

Prijevor

7.1 (liste vrijednosti)

$$a) R_1 = R_2 = 100k\Omega$$

$$T = \alpha \cdot \beta = 10^5$$

$$A = -0,999999$$

$$R_n = 0,5 \Omega$$

$$R_i = R_1 + R_n \approx 100k\Omega$$

$$R_o = \frac{75}{1+10^5} = 0,75m\Omega$$

$$b) R_1 = 1k\Omega, R_2 = 1M\Omega$$

$$T = 199,8$$

$$A = -995$$

$$R_n = 5 \Omega$$

$$R_i = R_1 + R_n = 1,005k\Omega$$

$$R_o = \frac{75}{1+199,8} = 0,374 \Omega$$


Statičke resurse OP-a
(neurivne o f)

- Ulažna struja pomaka I_{pom} (I_{off} - input offset current)

$$I_{\text{pom}} = ||I_+|| - ||I_-||$$

- Ulažna struja I_{ue} (I_b input bias current)

$$I_{\text{ue}} = \frac{|I_+| + |I_-|}{2}$$

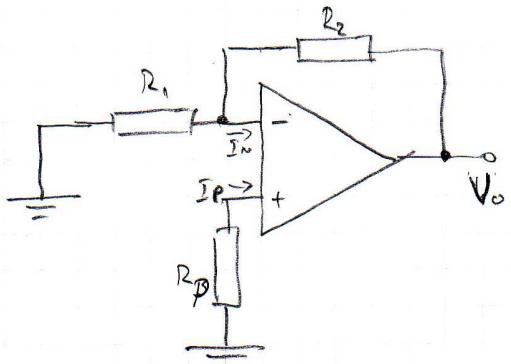

$$I_B = \frac{I_N + I_P}{2} \gg, I_{\text{os}} = I_P - I_N$$


$$\begin{aligned} E_0 &= V_o = \left(1 + \frac{R_2}{R_1}\right) \left[(R_1 \parallel R_2) I_N - R_P I_P \right] \\ &\Downarrow \\ E_0 &= \left(1 + \frac{R_2}{R_1}\right) (-R_1 \parallel R_2) I_{\text{os}} \end{aligned}$$

$$R_P = R_1 \parallel R_2$$

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) \left\{ \left[(R_1 \parallel R_2) - R_P \right] I_B - \left[(R_1 \parallel R_2) + R_P \right] \frac{I_{\text{os}}}{2} \right\}$$

- Greška ulaznog napona pomaka:
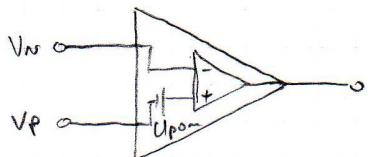
$$V_o = \alpha [V_p + V_{\text{os}} - V_N]$$



Ulažna greška

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) \left\{ V_{\text{os}} + \left[(R_1 \parallel R_2) - R_P \right] I_B + \left[(R_1 \parallel R_2) + R_P \right] \frac{I_{\text{os}}}{2} \right\}$$

za OP s FET na ulazu V_{os} dominira
s BIPOLARNIM dominira I_B


↑ vrijeđi za INV
NEINV.

Eliminacija smetnji

$$R_p = R_1 \parallel R_2$$

- Manji iznos: otpora reda 1k-10k Ω

INTEGRATOR

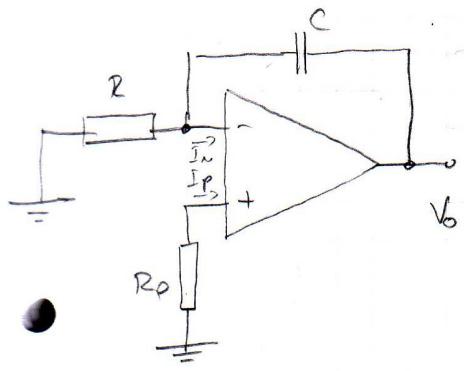

$$V_N = V_P = -R_p I_p$$



$$I_c = \frac{1}{R} (R_{IN} - R_p I_p) = \frac{1}{R} \left[(R - R_p) I_B - (R + R_p) \frac{I_{os}}{2} \right]$$

$$E_o(t) = \frac{1}{RC} \int_0^t -R I_{os} d\tau$$


$$\uparrow R_p = R$$

$$E_o(t) = \left[(R - R_p) I_B - (R + R_p) \frac{I_{os}}{2} \right] \frac{t}{RC}$$

INTERNA KOMP. NAPONA POMALCA

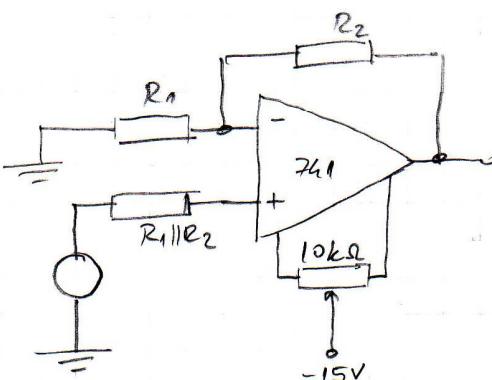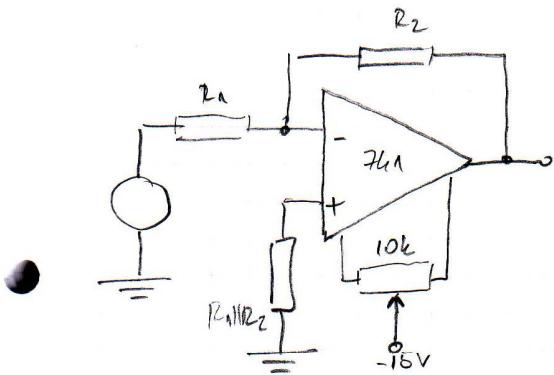



VANJSKA KOMP. NAPONA POMALCA

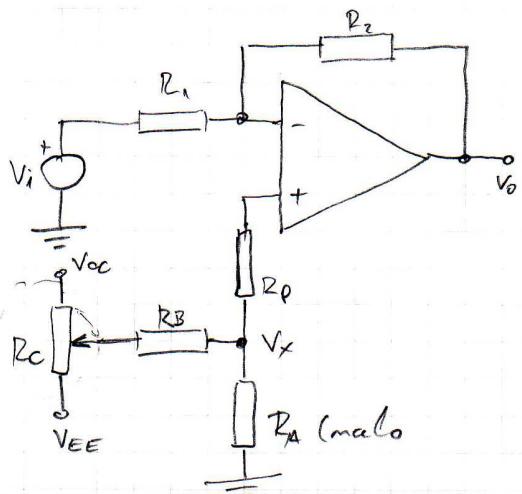


$$\begin{aligned} I_B &= 20 \mu A \\ I_{OS} &= 0,2 \mu A \\ V_{OS} &= 10 \mu V \\ R_2 &= 10 k\Omega \\ R_1 &= 1 k\Omega \end{aligned}$$

$$R_p = R_1 // R_2$$

DINAMIČKE NESAVRŠENOSTI OP-a

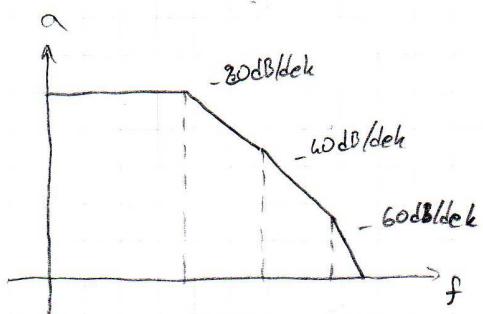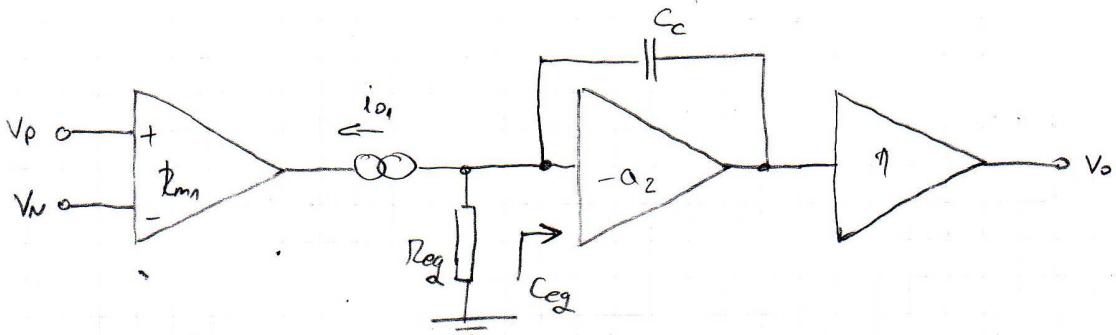

A-f kosa kl. nekompenzirani OP-a

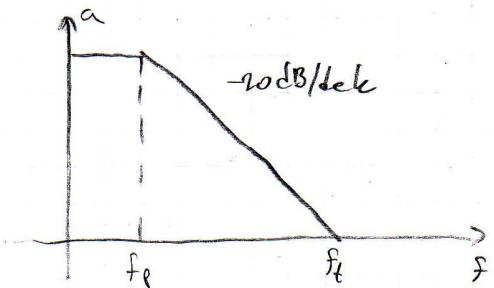


kompenzirani OP

$$f_t = \alpha \cdot f_b$$

$$a(jf) = \frac{\alpha_0}{1 + j \frac{f}{f_b}}$$

Din. nesavršenosti

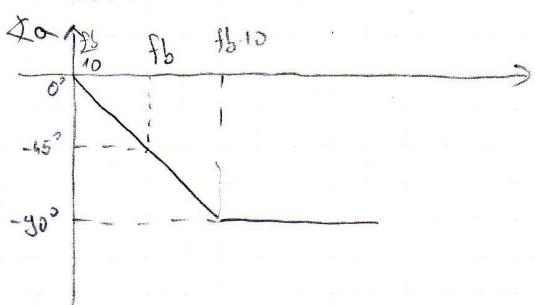- frekv. ovisnost pojačanja u otvorenoj petljii
- Ulazna i izlazna impedancija
- Vrijeme posasta izlaznog napona
- Konačna brzina posasta izlaznog napona (slow rate) $(\frac{dU}{dt})_{max}$
- Šum



$$\varphi_a = -\tan^{-1}\left(\frac{f}{f_b}\right)$$

$$|\alpha(jf)| \text{ for } f < f_b \rightarrow |\alpha| \angle 0^\circ$$


$$|\alpha(jf)| \text{ for } f = f_b \rightarrow \frac{|\alpha|}{\sqrt{2}} \angle 45^\circ$$

$$|\alpha(jf)| \text{ for } f > f_b \rightarrow \frac{|\alpha|}{f} \angle 90^\circ$$

$$A = \frac{\alpha}{1 + \alpha\beta} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{\beta}} = A_{IDEALNO} \cdot \frac{1}{1 + \frac{1}{T}}$$


\uparrow
 $1/\beta$

$T = \alpha \cdot \beta$


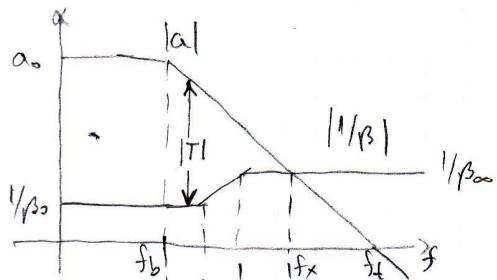


$$|T|_{dB} = |\alpha|_{dB} - |1/\beta|_{dB}$$
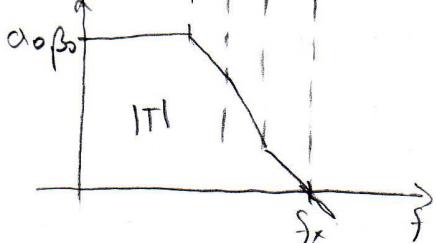
$$\triangleq T = \triangleq \alpha - \triangleq (1/\beta)$$





Nenivectrujúce pojačalo

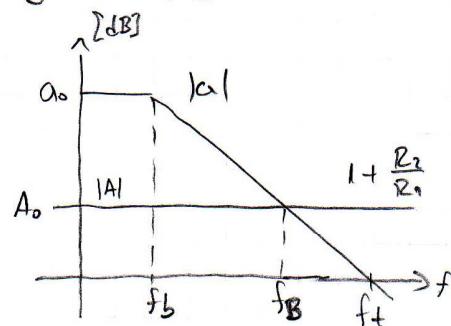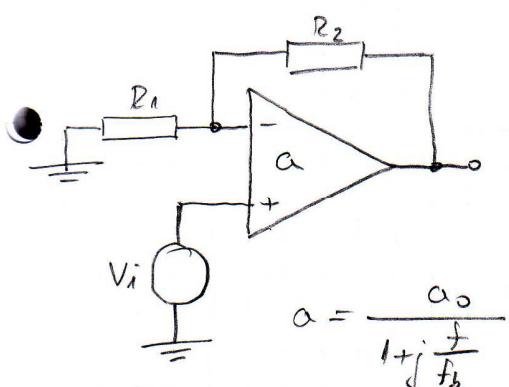


$$A(jf) = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right)\left(1 + j \frac{f}{f_b}\right) \frac{1}{\alpha_0}} = A_{IDE} \cdot \frac{1}{1 + \frac{1}{T(jf)}}$$

$$f_B = f_b \left(1 + \alpha_0 \frac{R_1}{R_1 + R_2}\right)$$



Invertirajuće pojačalo

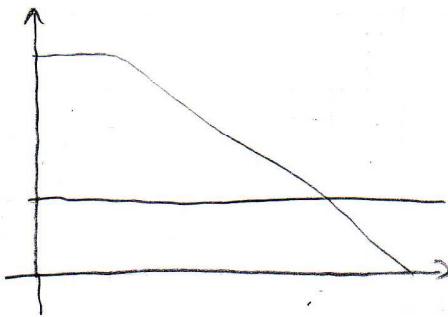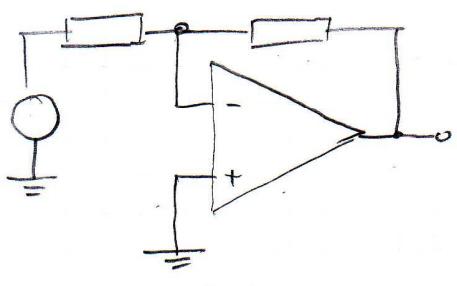

Uložne i izlazne impedancije

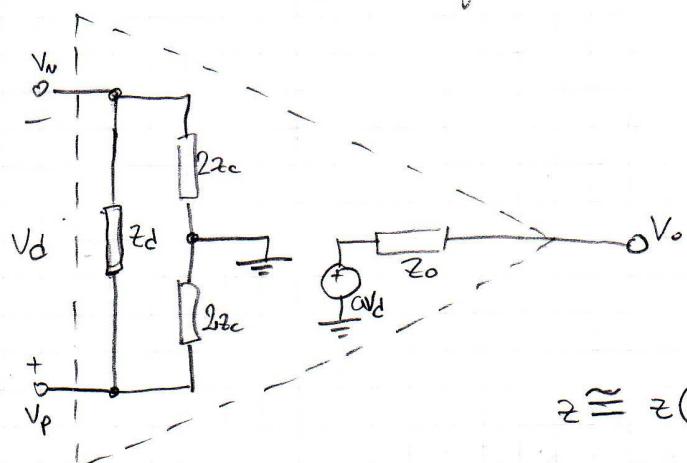

$$z \approx z(1+T)^{\pm 1}$$

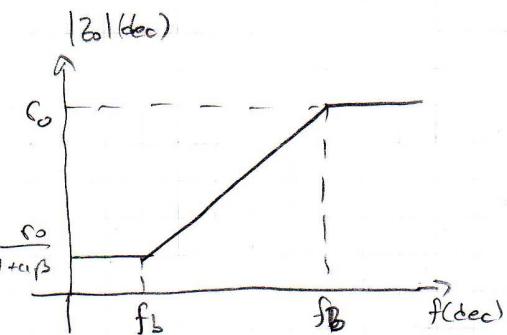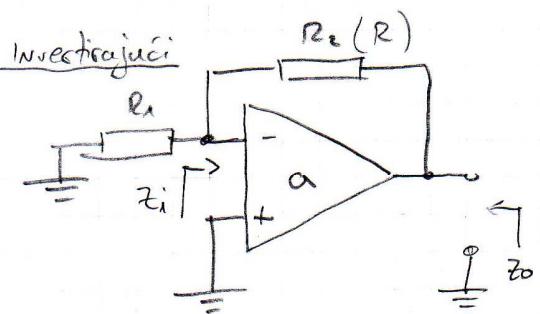

↳ karakteristika izlazne otpore visokim frekvencijama

$$Z_o \approx \frac{R_o}{1+\alpha\beta}$$


$$\beta \approx \frac{R_o}{R_1 + R_o}$$

$$Z_i \approx \frac{R}{1+\alpha}$$



$$Z_i \approx R_i \frac{1+j\frac{f}{f_L}}{1+j\frac{f}{f_H}}$$

$$R_i \approx \frac{R}{1+\alpha_o}$$
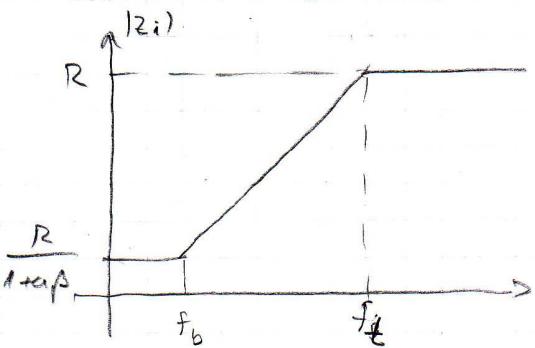
$$Z_o \approx R_o \frac{1+j\frac{f}{f_L}}{1+j\frac{f}{f_H}}$$



VRIJEME PORASTA IZLAZNOG NAPONA

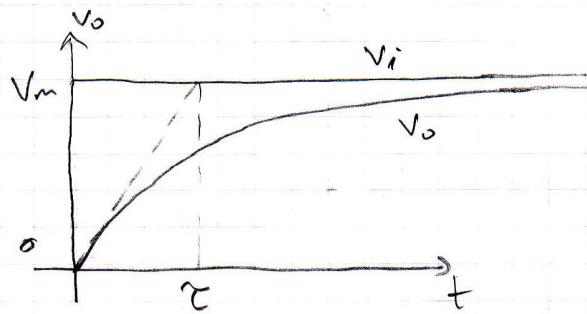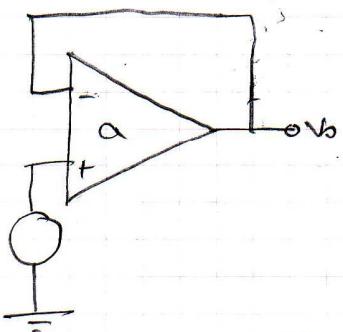


$$t_r = \frac{0.35}{f_t}$$

$$t_r = \tau (\ln 0.9 - \ln 0.1)$$

$$\tau = \frac{1}{2\pi f_t}$$

IZMJENIČNA (AC) POJAČALA

AC invertirajuće

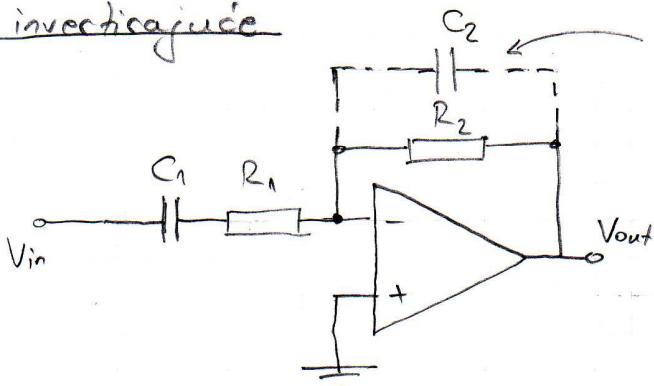

ograničava gornju frekvenčku karakteristiku pojačala

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \cdot \underbrace{\frac{jf}{f_1 + jf}}_{\text{ZBOG KAPACITETA}} \cdot \frac{1}{1 + \frac{1}{\alpha\beta}}$$

ZBOG KAPACITETA



$$f_1 = \frac{1}{2\pi R_1 C_1} \quad \leftarrow \text{DONJA GRANIČNA FREKU.}$$

$$\beta = \frac{z_1}{z_1 + z_2}$$


$$z_1 = X_{C_1} + R_1 = \frac{1}{j\omega C_1} + R_1$$

$$z_2 = X_{C_2} \| R_2$$

$$|Z_{in}| = |Z_1| = |R_1 + \frac{1}{j\omega C_1}|$$

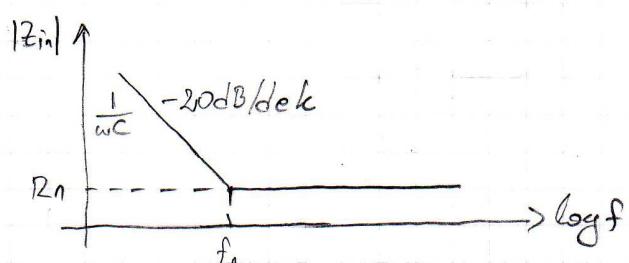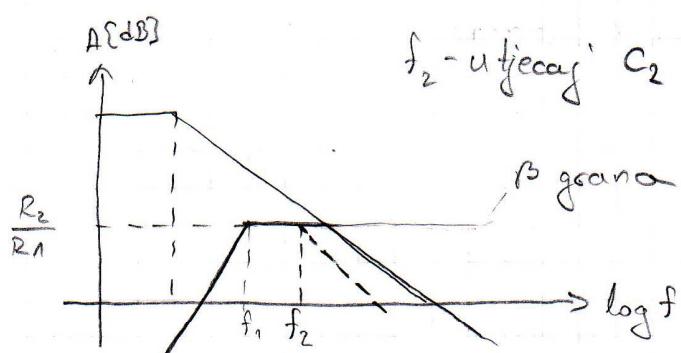

AC reinvertirajuće

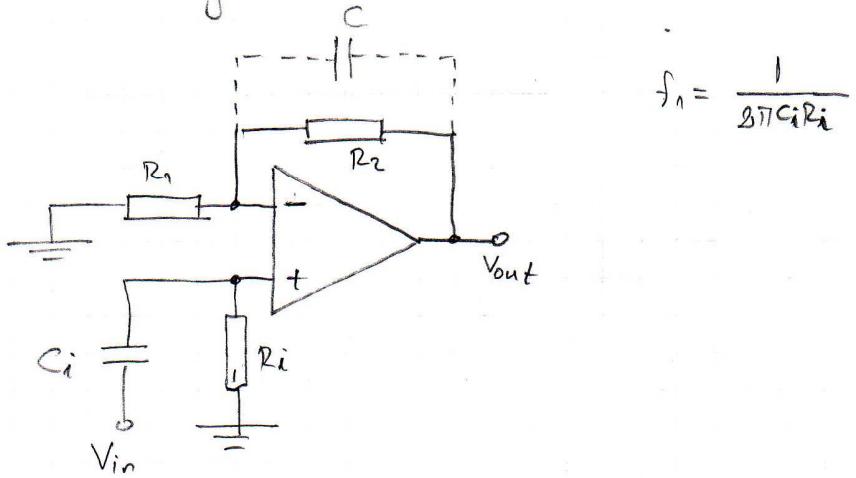


$$f_i = \frac{1}{2\pi C_i R_i}$$

SKLOPOVI ZA REALIZACIJU ANALOGNIH FUNKCIJA LINEARNIH

ZBRAJANJE

Invertirajuće zbrajalo

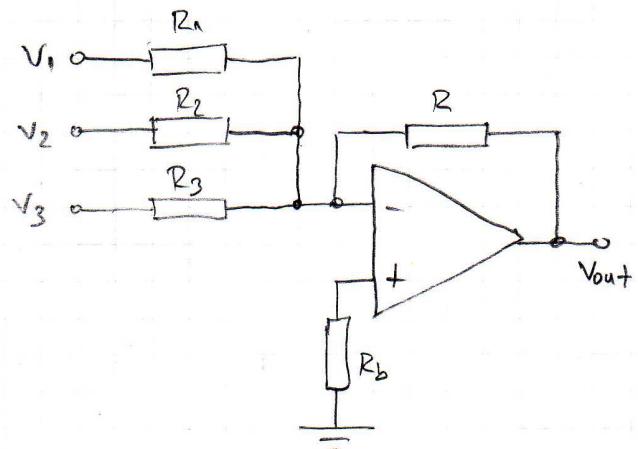


$$V_{out} = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \cdot R$$


↑ predznak

$R_b \approx R_1 \parallel R_2 \parallel R_3 \parallel R$ za smanjenje smetnjič

Neinvertirajuće

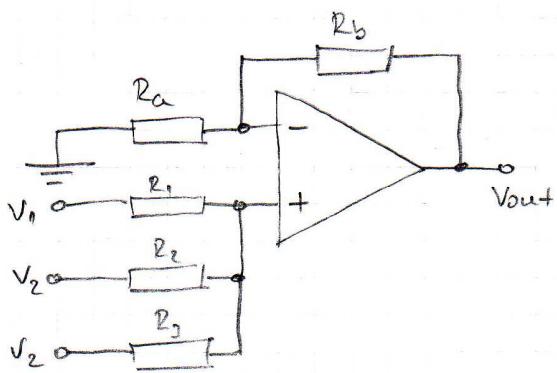


radomjestaška shema

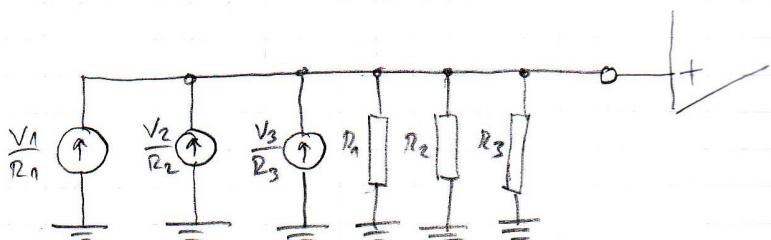

$$V_{out} = \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) R_p \left(1 + \frac{R_b}{R_1} \right)$$

$$R_p = R_1 \parallel R_2 \parallel R_3$$


Zbrajalo za diferencijalne signale

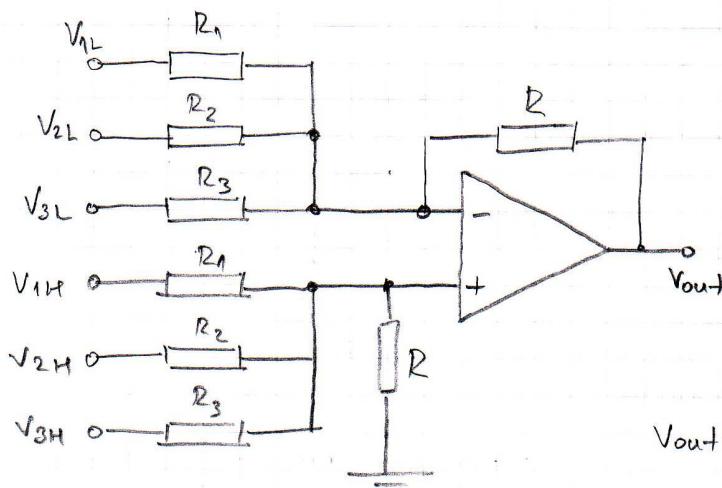

$$V_{out} = (V_{1H} - V_{1L}) \frac{R_n}{R_n} + (V_{2H} - V_{2L}) \frac{R}{R_2} + (V_{3H} - V_{3L}) \frac{R}{R_3}$$

POMAK ISTOSMJEERNE RAZINE

Invertirajuće

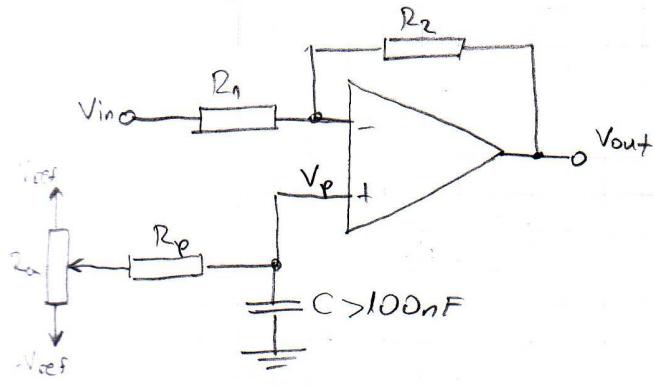


R_p - zaštita za pojačalo, u slučaju da R_a ode u krajnjem polje \rightarrow Voef direktno u uz pojačala

c - otklanjanje VF smetnje, DC komponenti ne smeta



$$V_{out} = - \frac{R_2}{R_1} V_i + V_p \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{\text{DC komponenta}}$$

Neinvertirajuće

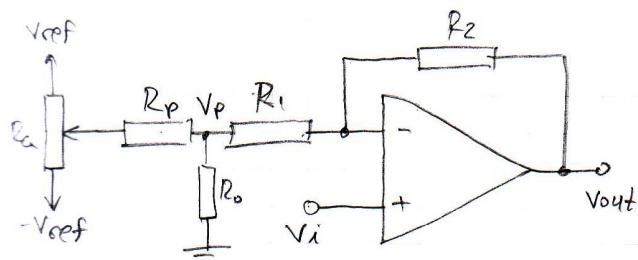

$$V_{out} = V_i \left(1 + \frac{R_2}{R_1 + R_o}\right) - V_p \frac{R_2}{R_1}$$

DERIVIRANJE

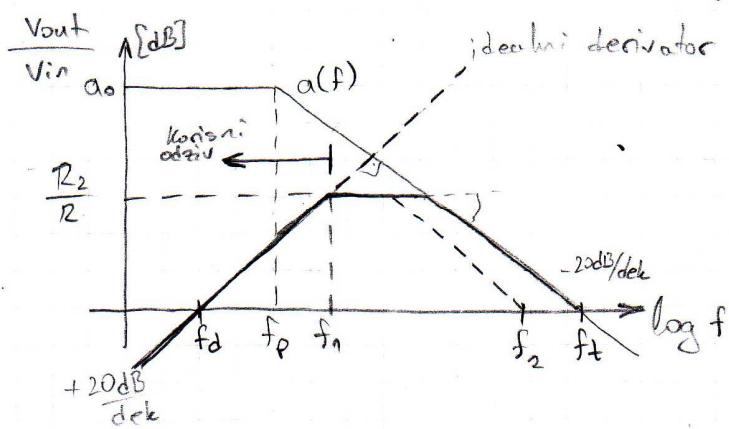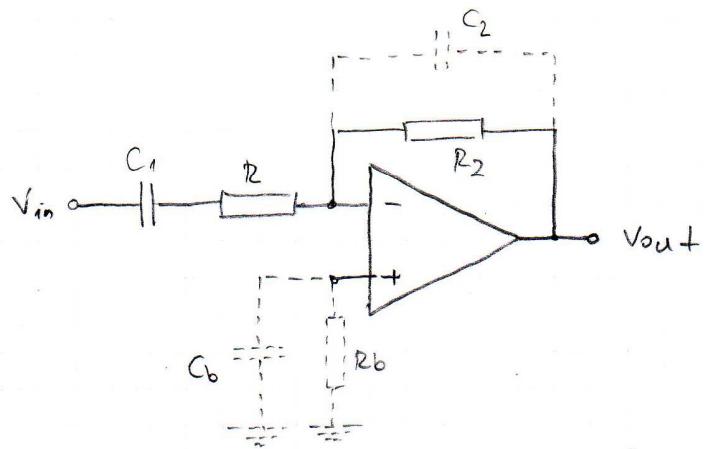

- sa R susimro pojačanje kako bi osigurali stabilnost pojačala

- f_2 - utjecaj od C_2

- od f_1 prema nize frekvencije iskoristiti odriv

$$f_n = \frac{1}{2\pi C_1 R}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{R_2}{Z_1}}{1 + \frac{1}{\alpha \beta}} \quad \leftarrow \text{uz zaremanarenje } C_b, R_b, C_2$$

$$\beta = \frac{Z_1}{R_2 + Z_1}$$

$$Z_1 = R + X_C_1 = R + \frac{1}{j\omega C_1}$$


$$\alpha = \frac{\alpha_0}{1 + j \frac{f}{f_p}}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-R_2 C_1 s}{1 + s(RC + \frac{1}{\alpha_0 2\pi f_p}) + s^2 \frac{C_1 (R + R_2)}{\alpha_0 2\pi f_p}}$$



- U korisnom području $f < f_1$

$$V_{out} = -R_2 C_1 \frac{dv_i}{dt}$$

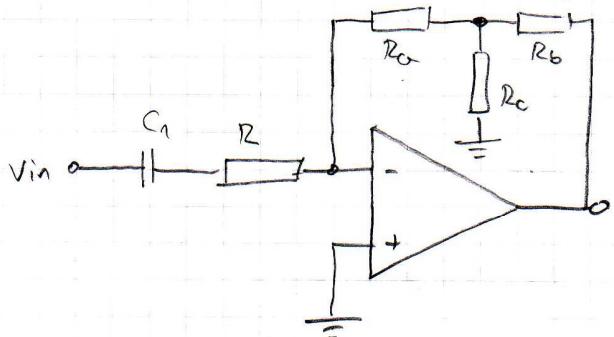- Ako je potrebna velika vremenska konstanta \Rightarrow



INTEGRATOR

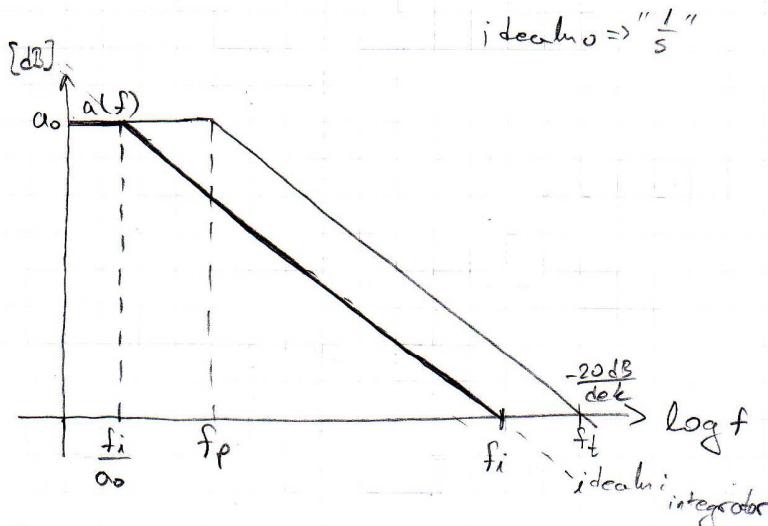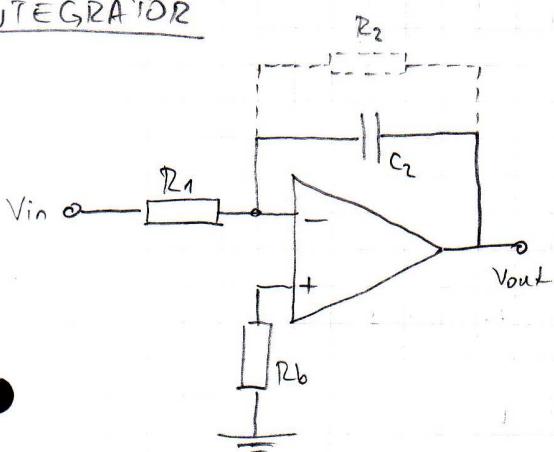

- zu "praktische" Integratoren $f_i \ll f_t$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{1}{R_1 C_2 s} \cdot \frac{1}{1 + \frac{s + 2\pi f_p}{\omega_0 2\pi f_p} \cdot \frac{s + R_1 C_2 s}{R_1 C_2 s}}$$


$$\omega_i = \frac{1}{R_1 C_2} \Rightarrow f_i = \frac{1}{2\pi R_1 C_2}$$

- zu $f \ll f_i$

$$\frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = -\frac{1}{\frac{1}{\omega_0} + \frac{s}{\omega_i}} \quad \rightarrow \quad V_{\text{out}}(t) = -\frac{1}{\zeta} \int_{t_0}^{t_0+T} V_{\text{in}}(t) dt + V_0$$

$$\zeta = R_1 C_1$$

NEGATIVNI KONVERTOR IMPEDANCije (NIC)

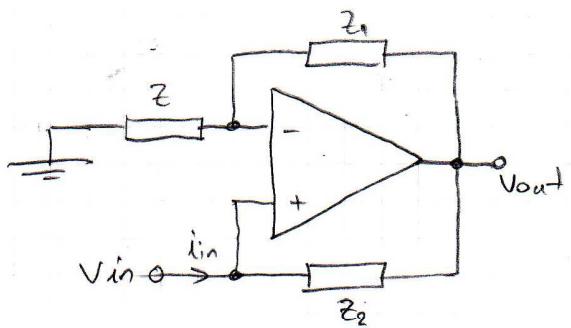


$$V_{out} = V_{in} \left(1 + \frac{Z_1}{Z_2} \right)$$

$$V_{in} - V_{out} = i_{in} Z_2$$

$$\Rightarrow Z_{in} = -Z \frac{Z_2}{Z_1}$$

nadomješće shema

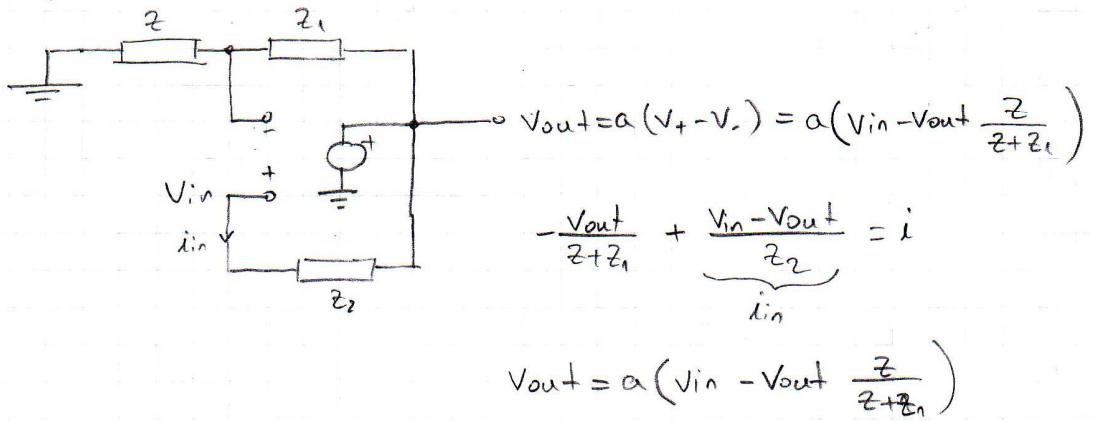

$$V_{out} \left(1 + \frac{Z_a}{Z+Z_1} \right) = a \cdot V_{in} \Rightarrow V_{out} = \frac{a \cdot V_{in}}{1 + \frac{Z \cdot a}{Z+Z_1}} = \frac{V_{in}}{\frac{1}{a} + \frac{Z}{Z+1}}$$

$$\lim_{a \rightarrow \infty} V_{out} = \left(1 + \frac{Z_1}{Z_2} \right) V_{in}$$


$$i_{in} = \frac{V_{in} - V_{out}}{Z_2} = \frac{V_{in}}{Z_2} - \frac{1}{Z_2} \left(1 + \frac{Z_1}{Z} \right) V_{in}$$

$$i_{in} = V_{in} \left[\frac{1}{Z_2} - \frac{1}{Z_2} \left(1 + \frac{Z_1}{Z} \right) \right]$$

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{1}{\frac{1}{Z_2} - \frac{1}{Z_2} \left(1 + \frac{Z_1}{Z} \right)} = \frac{Z \cdot Z_2}{Z - Z \left(1 + \frac{Z_1}{Z_2} \right)} = \frac{Z \cdot Z_2}{Z - Z - Z_1} = -Z \cdot \frac{Z_2}{Z_1}$$

AC/DC PRETVORBA


Precizni poluvratični ispravljač

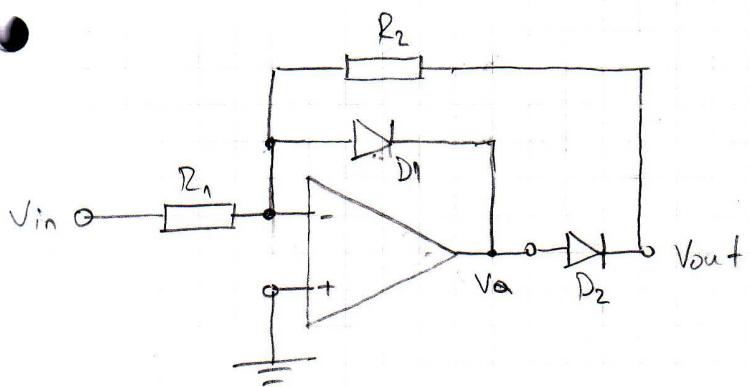



za $V_{in} > 0$, $V_a \rightarrow$ negativan
D1 vodi, D2 ne vodi
 R_2 - ne teče struja

$V_{in} < 0$, V_a - pozitivan, D1 ne vodi, D2 vodi,
pozitivna veza zatrosena kroz R_2

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

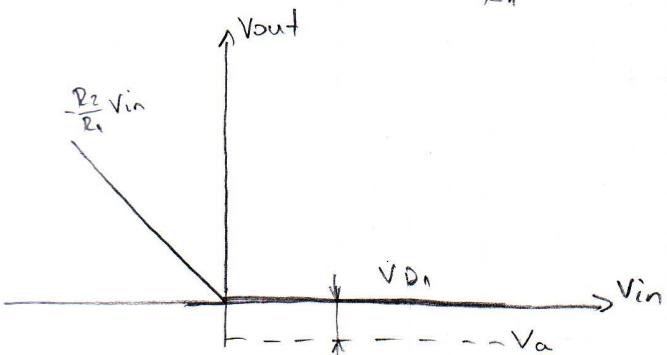


Punovratični ispravljač

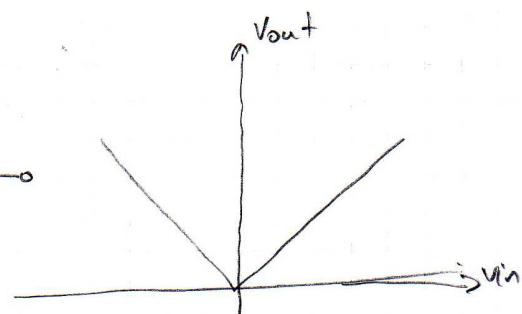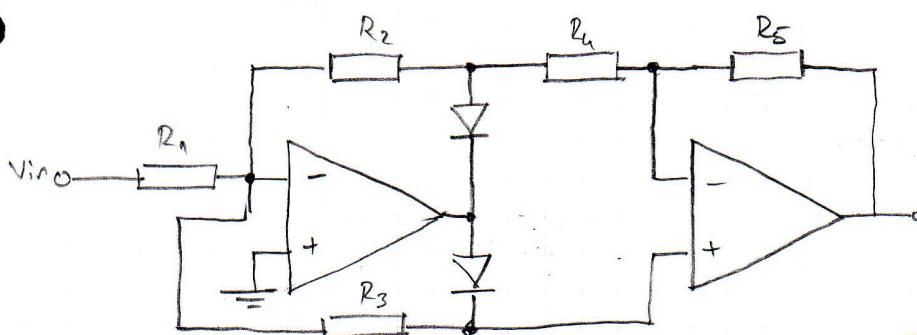

ZADATCI

①

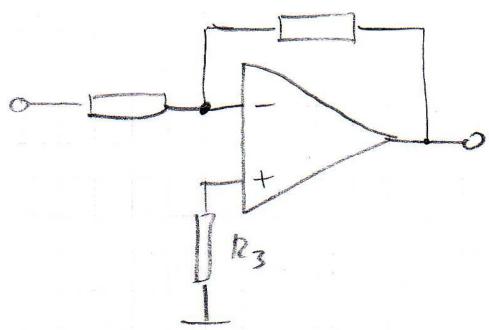

$$A = -\frac{R_2}{R_1} \Rightarrow R_2 \\ R_{ul} = R_1 \\ \left. \begin{array}{l} \end{array} \right\} \Rightarrow R_3 = R_1 // R_2$$


$$\frac{dU_{iz}}{dt} = 1 \text{ V/us}$$

$$U_{iz\max} = 8$$

$$f_{max} = \frac{\left(\frac{dU_{iz}}{dt}\right)_{max}}{2\pi \cdot U_{max}} = 19,9 \text{ kHz}$$

②
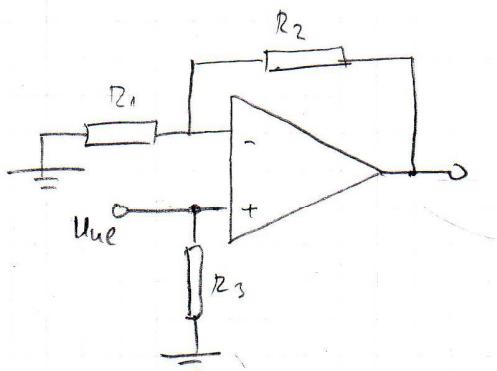
$$A = 10 \\ R_{ul} = 10 \text{ k}\Omega \\ f = 10 \text{ kHz} \\ f_p = 10 \text{ Hz} \\ a_0 = 70 \text{ dB} \\ f_d = 1 \text{ MHz}$$



$$A|_{f=}$$

$$A = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = 9 \Rightarrow R_2 = 9R_1$$

$$R_{ul} = R_3$$

$$R_3 = R_1 // R_2$$

$$\frac{R_1 R_2}{R_1 + R_2} = R_{ul} \Rightarrow R_1 = 10 \frac{R_{ul}}{9} = 11,11 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega, R_3 = 10 \text{ k}\Omega$$

$$\alpha = \frac{a_0}{1 + j \frac{f}{f_p}}$$

$$\alpha = \frac{a_0}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}}$$

$$20 \log a_0 = 70 \text{ dB}$$


$$a_0 = 10^{\frac{70}{20}} = 10^{3.5} = 3,16 \cdot 10^3$$

$$\alpha = \frac{a_0}{\sqrt{1 + \left(\frac{10 \text{ kHz}}{10 \text{ Hz}}\right)^2}} = 3,16$$

$$A = \frac{\left(1 + \frac{R_2}{R_1}\right)\alpha}{1 + \alpha + \frac{R_2}{R_1} + \frac{R_2}{C_d}} = 2,38$$

SACABAHTER

nadomjesna shema

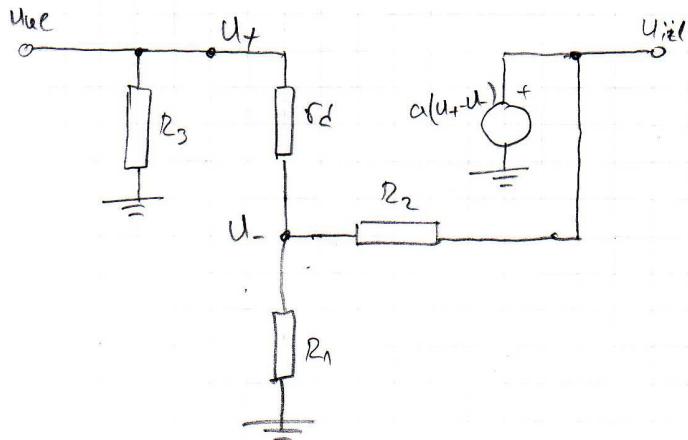

$$\left. \begin{aligned} \frac{U_+ - U_-}{R_d} - \frac{U_-}{R_1} + \frac{U_{izl} - U_-}{R_2} &= 0 \\ U_+ = U_{in} \\ U_{izl} = \alpha(U_+ - U_-) \end{aligned} \right\} A$$

Dodavanjem izvora s unutarnjim otpalom R_g

$$R_3 \parallel R_g$$

$$U_{izl, posm} = \left\{ U_f + I_{in} \left[(R_3 \parallel R_g) - (R_1 \parallel R_2) \right] + I_{posm} \frac{(R_3 \parallel R_g) + (R_1 \parallel R_2)}{2} \right\}$$

$$\begin{aligned} T_{min} &= 5^\circ C \\ T_{max} &= 35^\circ C \\ T_0 &= 15^\circ C \end{aligned}$$

$$\begin{aligned} \Delta T_1 &= -10^\circ C \\ \Delta T_2 &= 20^\circ C \end{aligned}$$


$$\frac{\Delta U}{\Delta T} = \left[\left(\frac{dU}{dT} \right) + \left(\frac{dI_{of}}{dT} \right) \cdot R_3 \right] \cdot \left(1 + \frac{R_2}{R_1} \right)$$

$$\Delta U_1 = \Delta T_1 \cdot [] = -1,25 mV$$

$$\Delta U_2 = \Delta T_2 \cdot [] = +2,5 mV$$

$$-1,25 \leq \Delta U \leq 2,5 V$$

premjenica
pojačanja

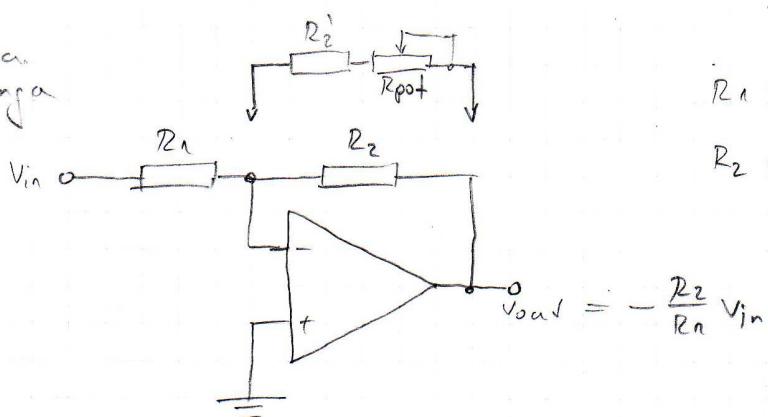

R_1 - ne mijenjam
 R_2 - može

$$A_{min} = -\frac{R_2}{R_1}$$

$$A_{max} = -\frac{R_2 + R_{pot}}{R_1}$$