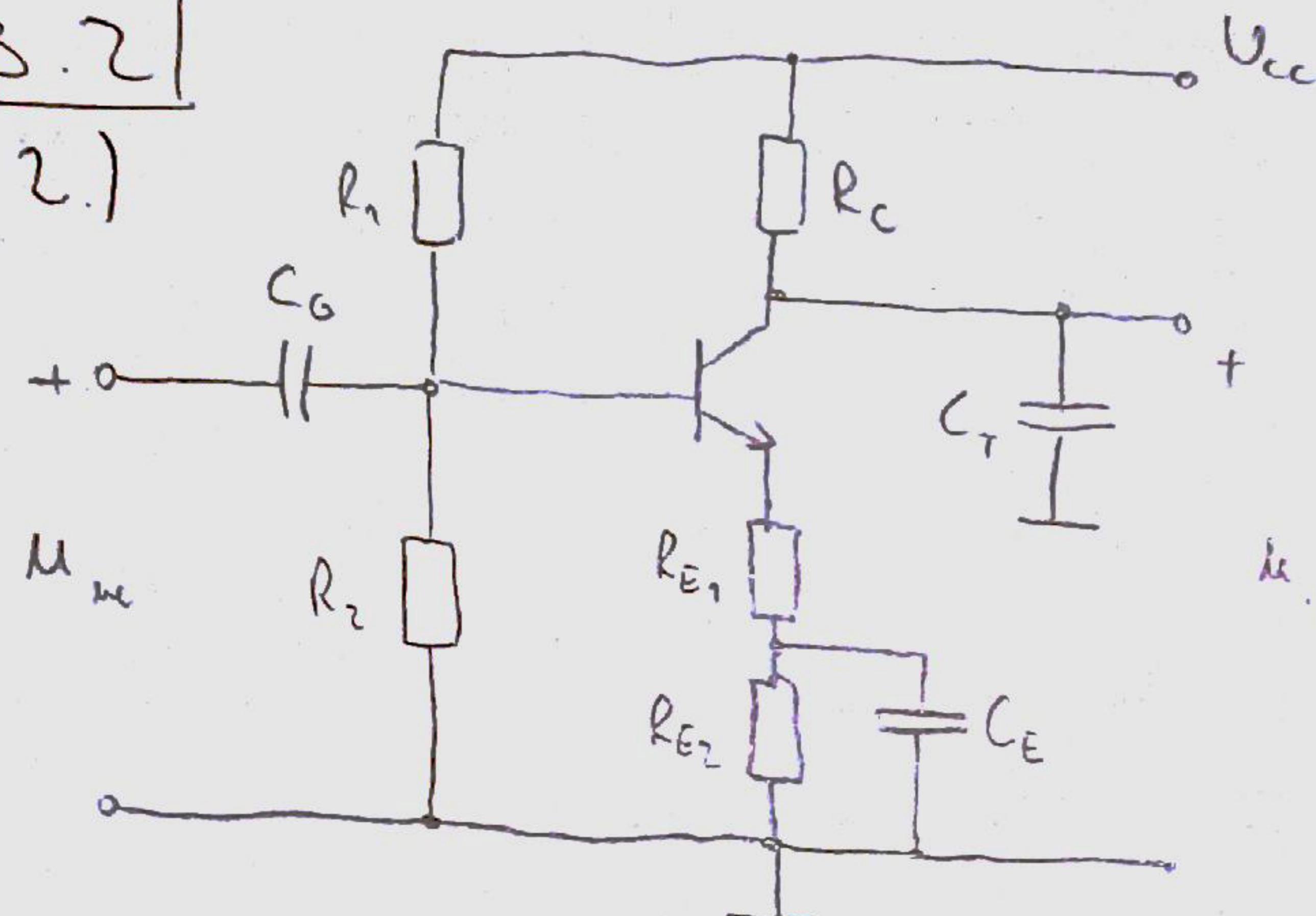


# ELEKTRONIKA 2

## 3. LAB. VJEŽBA

**[3.2]**

2.)



$$U_{cc} = 12V$$

$$R_1 = 8,2k\Omega$$

$$R_2 = 3,3k\Omega$$

$$R_c = 1,8k\Omega$$

$$R_{E1} = 150\Omega$$

$$R_{E2} = 820\Omega$$

$$C_G = 1\mu F$$

$$C_E = 33\mu F$$

$$C_T = 100\mu F$$

$$\beta = h_{FE} = 150$$

### STATIKA

$$U_{BB} = \frac{R_2}{R_1 + R_2} U_{cc} = 3,443V$$

$$R_E = R_1 // R_2 = 2353\Omega$$

$$U_{BB} - I_{BQ} R_B - U_{BEQ} - (\gamma + \beta) I_{BQ} (R_{E1} + R_{E2}) = 0$$

$$I_{BQ} = \frac{U_{BB} - U_{BEQ}}{R_B + (\gamma + \beta)(R_{E1} + R_{E2})} = 18.43\mu A$$


$$I_{CQ} = \beta I_{BQ} = 2,765mA$$

$$U_{CEQ} = U_{cc} - I_{CQ} R_c - (\gamma + \beta) I_{BQ} (R_{E1} + R_{E2})$$

$$U_{CEQ} = 4.3236V > U_{BEQ} \rightarrow \text{NAP}$$

$$r_{B'E} = \frac{U_T}{I_{BQ}} = 1356\Omega$$


$$r_{BB} = 0\Omega$$

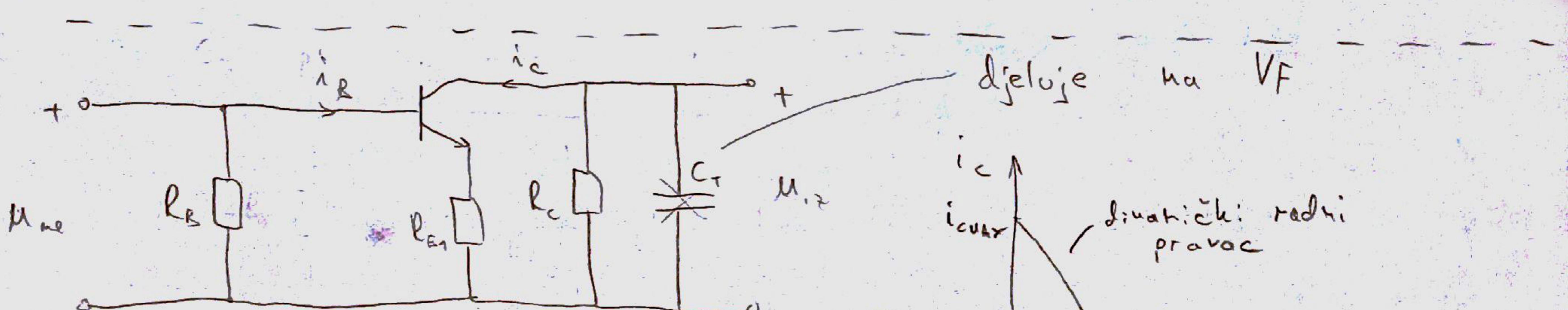

$$U_{12Q} = U_{cc} - I_{CQ} R_c = 7.023V$$

$$u_{ce} = -i_c (R_c + R_{E1}) \quad (i_e \approx i_c)$$

$$i_c = -\frac{1}{R_c + R_{E1}} u_{ce}$$

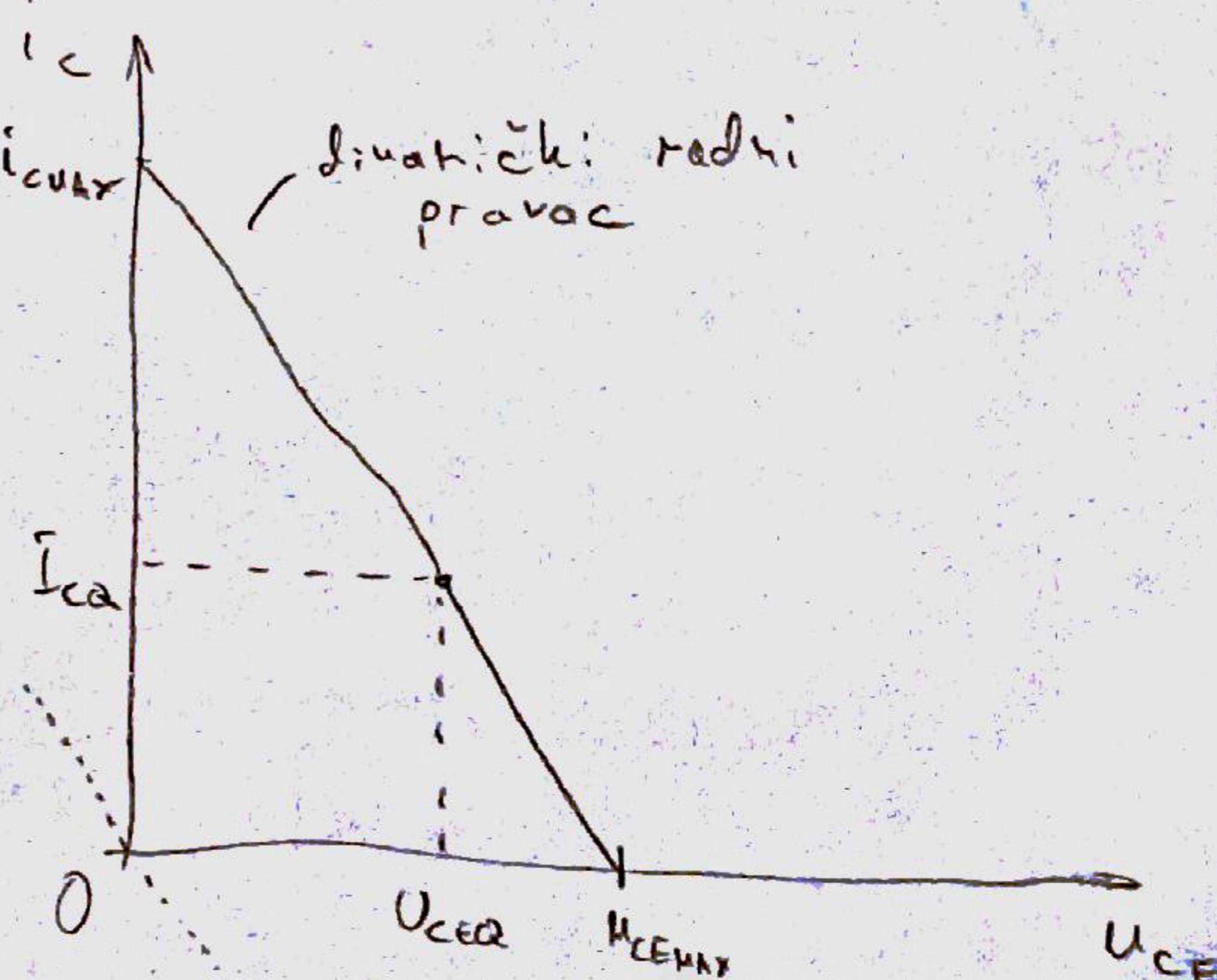

\*uhupni hod

$$(i_c - I_{cQ}) = -\frac{1}{R_c + R_{E_1}} (U_{ce} - U_{cEQ}) \quad \text{- dinanički radni pravac}$$

$$U_{z2} = -i_c R_c$$


$$i_c = -\frac{1}{R_c + R_{E_1}} (U_{ce} - U_{cEQ}) + I_{cQ}$$

$$|\Delta U_{iz_{MAX}}| = \Delta i_{cMAX} R_c$$


$$\Delta i_{cq} = i_c (U_{ce} = 0) - I_{cQ} = 2.217 \text{ mA}$$

$$\Delta i_{cd} = I_{cQ} = 2.765 \text{ mA}$$

$$|\Delta U_{iz_{MAX}}| = 3.9906 \text{ V}$$

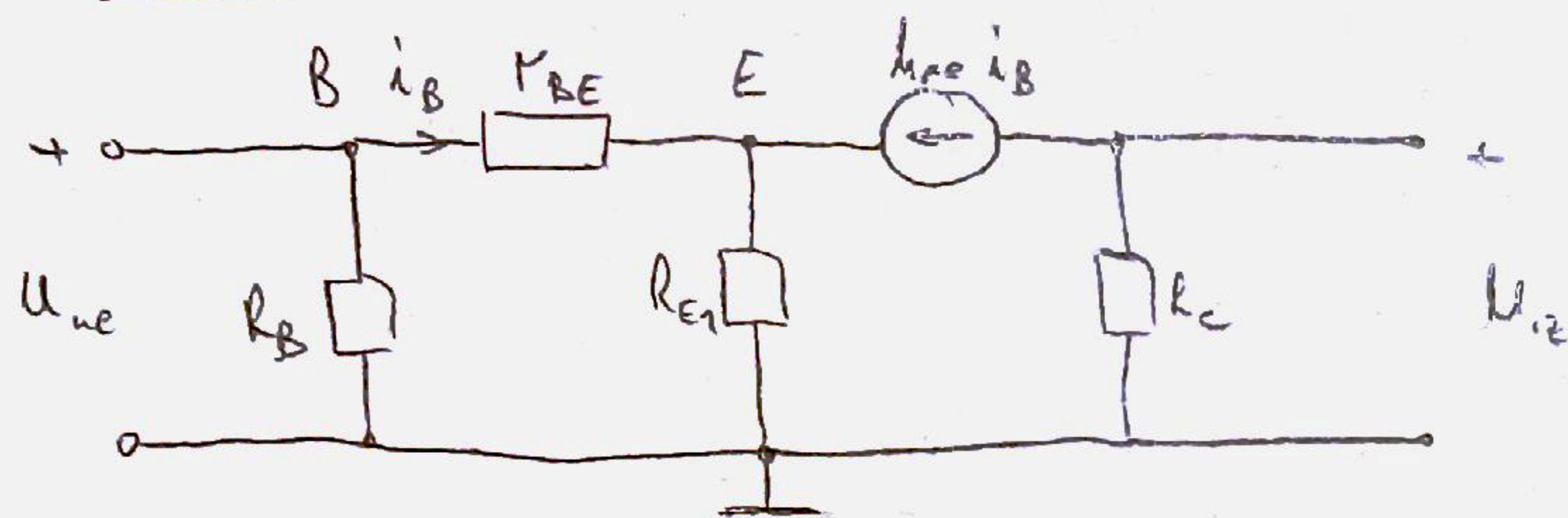
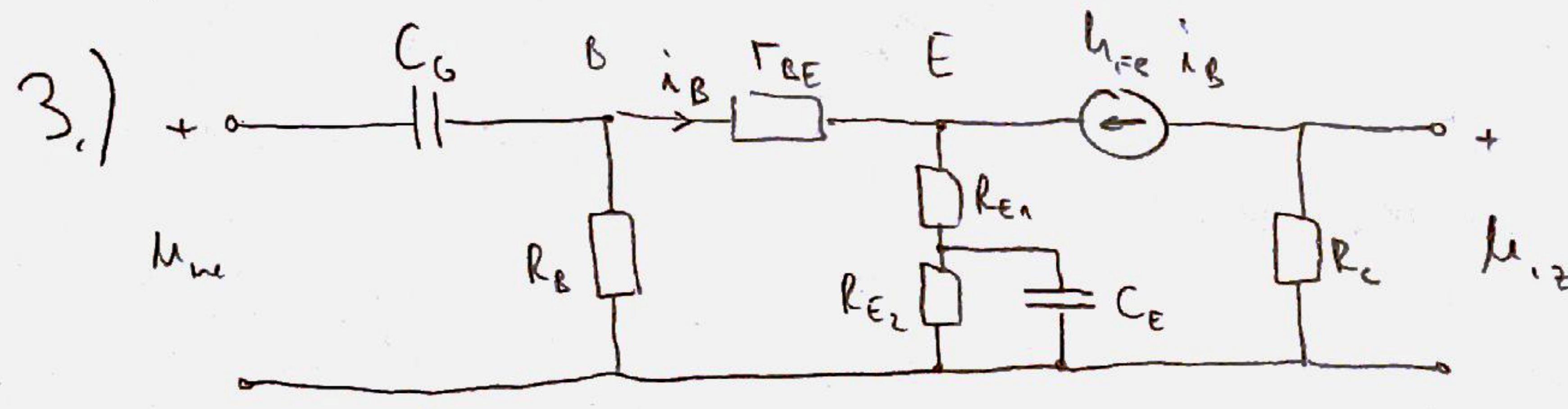
$$A_{vo} = \frac{U_{z2}}{U_{in}} = \frac{U_{z2}}{i_B} \cdot \frac{i_B}{U_{in}} = -h_{FE} R_C \cdot \frac{1}{r_{BE} + (1+h_{FE})R_{E1}} = -11.247$$



$$* \tau_{G1} = C_G \cdot (R_B \parallel \underbrace{(r_{BE} + (1+h_{FE})R_{E1}}_{24006})) \quad \dots \omega_G > \omega_E \dots \tau_G < \tau_E$$

$$\tau_{G1} = 2.743 \cdot 10^{-3} \text{ s} \quad \omega_{G1} = 466.6 \text{ rad/s} \quad \times$$

$$\tau_{E1} = C_E \left( R_{E2} \parallel \left( R_{E1} + \underbrace{\frac{r_{BE} + R_B}{1+h_{FE}}}_{124.56} \right) \right) \quad \dots \omega_G > \omega_E$$

$$\tau_{E1} = 5.76 \cdot 10^{-6} \text{ s} \quad \omega_{E1} = 173.594 \cdot 10^3 \text{ rad/s} \quad \cancel{\omega_G > \omega_E}$$

$$\omega_E > \omega_G \quad \tau_{G2} = C_G \cdot (R_B \parallel \underbrace{(r_{BE} + (1+h_{FE})(R_{E1} + R_{E2}))}_{147.826}) = 2.316 \cdot 10^{-3} \text{ s} \quad \omega_{G2} = 431.75 \text{ rad/s}$$

$$\tau_{E2} = C_E \left( R_{E2} \parallel \left( R_{E1} + \underbrace{\frac{r_{BE}}{1+h_{FE}}}_{159} \right) \right) = 4.394 \cdot 10^{-6} \text{ s} \quad \omega_{E2} = 227.56 \cdot 10^3 \text{ rad/s}$$

$$\tau_1 = R_{E2} C_E = 2.706 \cdot 10^{-5} \text{ s} \quad \omega_1 = 36.95 \cdot 10^3 \text{ rad/s}$$

# ELEKTRONIKA 2

## 3. LAB, VJEŽBA


3.2

3.) \* na stavku

$$\omega_{E_2} \gg \omega_{G_2}, \omega_n$$

$$\omega_d = \omega_{E_2} = 227560 \text{ rad/s}$$
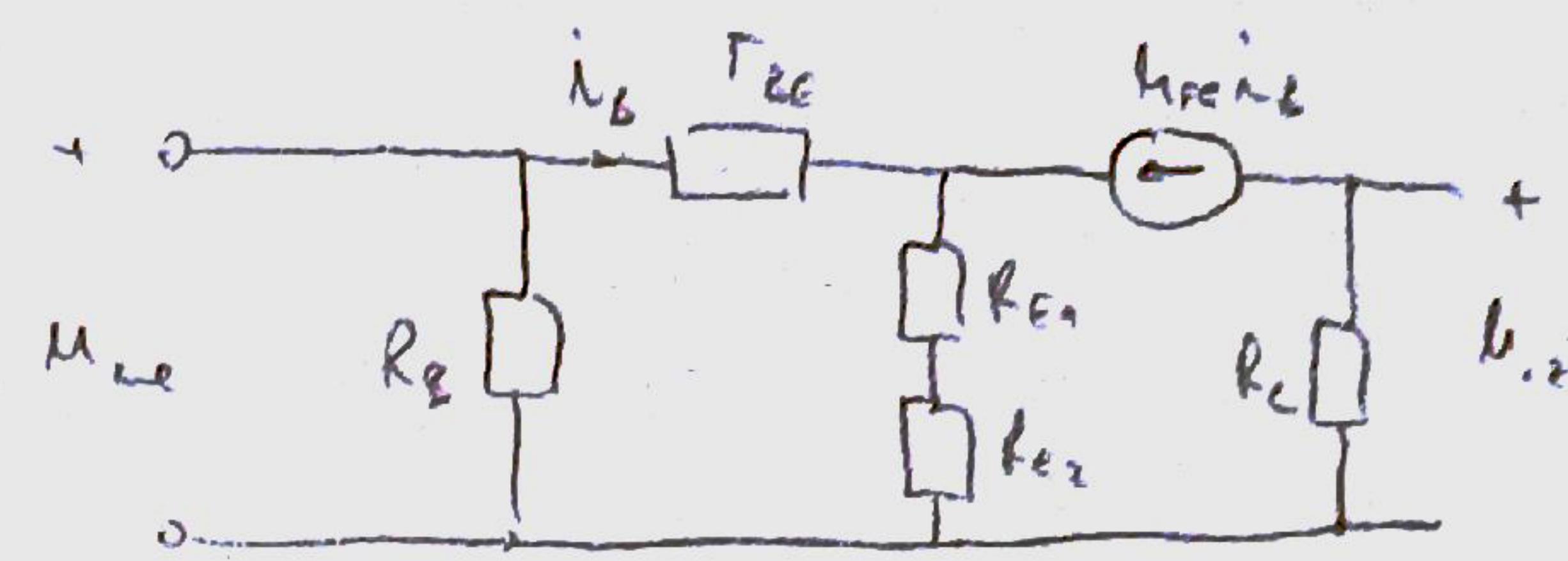
$$f_d = \frac{\omega_d}{2\pi} = 36.218 \text{ kHz}$$



$$A_{VM} = \left| \frac{u_{out}}{u_{in}} \right| = \frac{u_{out}}{i_B} \cdot \frac{i_B}{u_{in}} = -h_{fe} R_C \cdot \frac{1}{R_E + (1-h_{fe})(R_E + h_{fe}2)}$$

$$A_{VM} = -1.826$$

$$A(j\omega) = A_{VM} \frac{j \frac{\omega}{\omega_{G_2}}}{1 + j \frac{\omega}{\omega_{G_2}}} \cdot \frac{1 + j \frac{\omega}{\omega_n}}{1 + j \frac{\omega}{\omega_{E_2}}}$$

$$A(j\omega) = -1.826 \frac{j\omega \cdot 2.316 \cdot 10^{-3}}{1 + j\omega \cdot 2.316 \cdot 10^{-3}} \cdot \frac{1 + j\omega 2.706 \cdot 10^{-5}}{1 + j\omega 4.394 \cdot 10^{-6}}$$

$$A(j\omega) = -1.826 \frac{j \frac{\omega}{937.75}}{1 + j \frac{\omega}{937.75}} \cdot \frac{1 + j \frac{\omega}{36.95 \cdot 10^3}}{1 + j \frac{\omega}{227.56 \cdot 10^3}}$$

