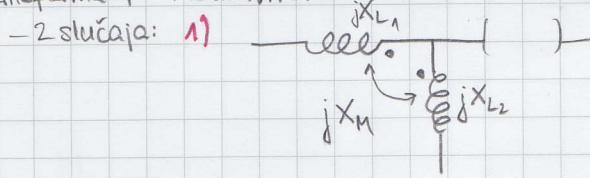


Masovne OE


- teorija: transformacija induktiviteta

- 2 slučaja: 1)




- na spoju 2 zavojnice je jedna grana

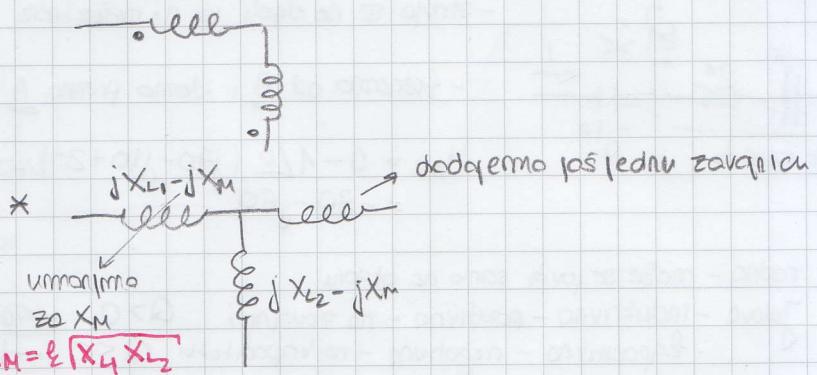
- ako zavojice skupu gledaju ili ne gledaju taj će se postupak pet



2) tacnice ne dijelju isto

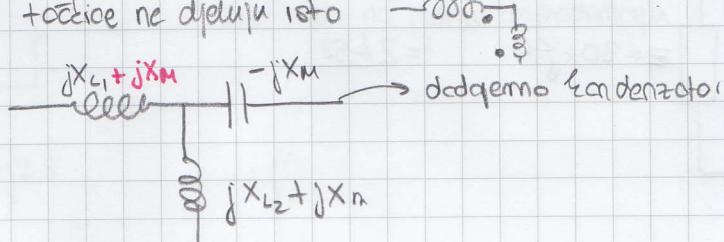

①

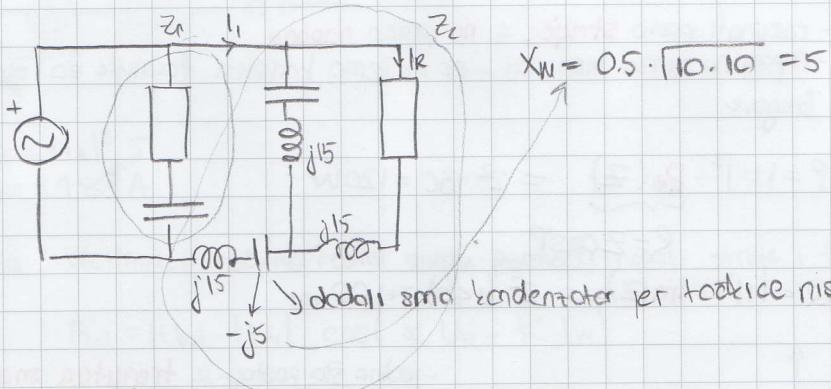

$$P = I_R^2 \cdot R$$

na Z_1 i Z_2 ih naponi, Z_1 norm uopće ne treba

$$I_1 = \frac{100}{Z_2} = 0.6 - j5.8$$


$$Z_2 = [j10 || (15 + j5)] + j10 = 17.15 \angle 84^\circ \Omega$$

$$I_R = I_1 \cdot \frac{j10}{j10 + 15 + j5} \rightarrow \text{torna gdje ne ide} = 2 \angle 53^\circ$$


ukupna struja \downarrow ukupna impedanca

$$P = 2^2 \cdot 15 = 60W$$

2) Koliko napon mjeri V

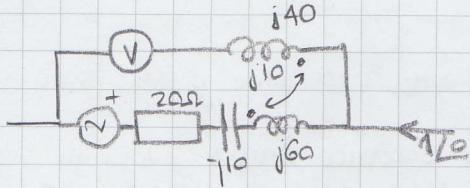

- transformacija među induktivitetu

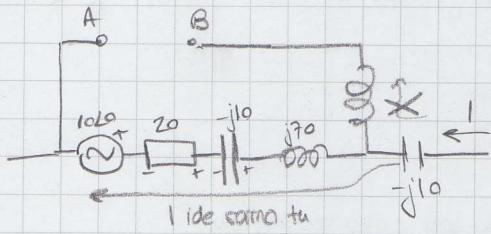



- struja se ne dijeli jer ne može kroz voltmeter

$$- \text{energija od } B \text{ i idemo prema } A \quad U_V = |U_{AB}| = 30\sqrt{5} \text{ V}$$

$$U_{AB} = 0 - 1\angle 0^\circ (j70 - j10 + 20) - 10\angle 0^\circ \\ = -30 - j60$$

teorija: 3 snage: radna - može se javiti samo na otporu

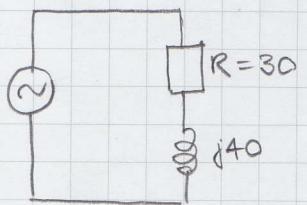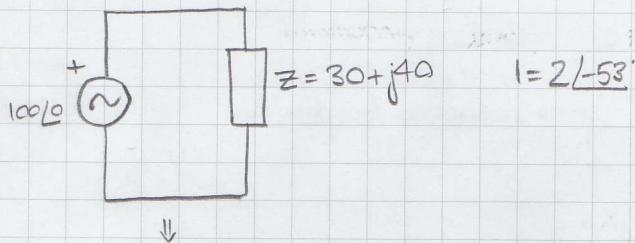Jalova - induktivna - pozitivna - na zavojnici $Q > 0$ → \nearrow
- kapacitivna - negativna - na kapacitetu $Q < 0$ → \downarrow





- računati preko struje, a ne preko napona
- naponi na njima nisu isti - ne možemo koristiti formule za istosmjerne struje


$$P = I^2 \cdot \underbrace{\text{Re}(Z)}_{R} = 2^2 \cdot 30 = 120 \text{ W}$$

$$R = Z \cos \varphi$$
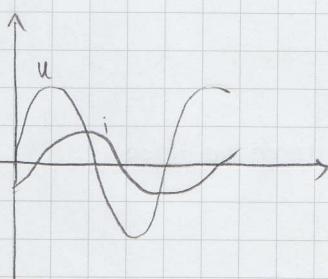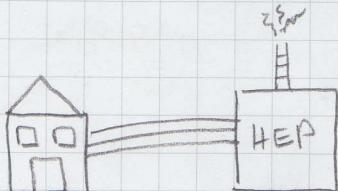
$$Q = I^2 \cdot \underbrace{\text{Im}(Z)}_{+40} = 2^2 \cdot (+40) = +160 \text{ var}$$



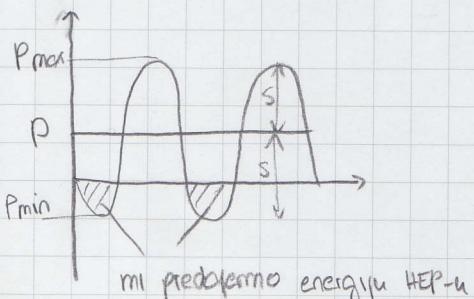- jedina što postoji je trenutna snaga
 $p(t) = u(t) \cdot i(t)$




- trenutna snaga ima: pozitivne i negativne dijelove
svak maksimum i minimum
- mi pišemo P - srednju vrednost od P_{max} i P_{min}
- amplituda je prividna snaga S
 $- P = \frac{P_{\text{max}} + P_{\text{min}}}{2}$


$$- S = \frac{P_{\text{max}} - P_{\text{min}}}{2}$$

$$S = \sqrt{P^2 + Q^2}$$

induktivni trokut snage

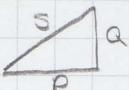


kapacitivni trokut snage

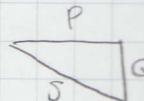

- S nije broj, to je vektor
 $S = U \cdot I^*$

↳ kompleksni broj

$$\begin{aligned}
 S &= U \cdot I^* \\
 &= 100 \angle 0^\circ \cdot 2 \angle -53^\circ \rightarrow \text{jer je kompl. broj} \quad |I| = 2 \angle -53^\circ \\
 &= 200 \angle -53^\circ \\
 &= 120 + j160 \\
 &P + jQ
 \end{aligned}$$

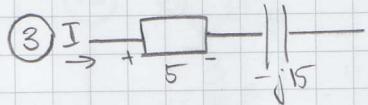


$$|I| = \frac{|U_r|}{R} = 6.32$$

$$P = \frac{|U_r|^2}{R} = |I|^2 \cdot R = 200 \text{ W}$$

$$Q = |I|^2 \cdot X_C = -600 \text{ var}$$


↓
jer je kapacitet

④

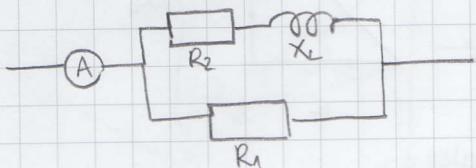

sve svesti na jednu impedanciju

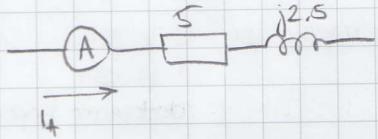
$$Z_{lk} = 10 \parallel (6 + j8) = 5 + j2.5$$



$$\begin{aligned}
 P_{lk} &= |I_A|^2 \cdot 5 \\
 |I_A| &= 19.83 \text{ A}
 \end{aligned}$$


teorija: Wattmeter racuna radnju snagu pomocu napona, struje i fulta razmedju

$$P_W = |U_W| \cdot |I_W| \cdot \cos(\phi_{U_W} - \phi_{I_W})$$

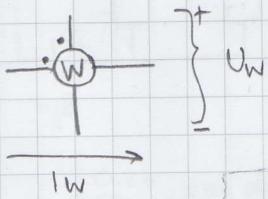

točice znače kao plus (jedan za U, jedan za I)

⑤

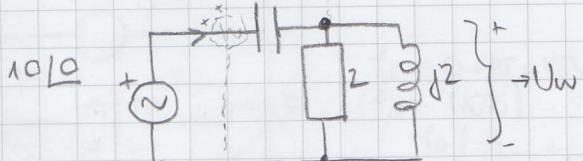

$$Z_{lk} = -j2 + [2 \parallel j2] = 1 - j1 \Omega$$




$$|I_W| = |I_{lk}| = \frac{10 \angle 0^\circ}{Z_{lk}} = 5\sqrt{2} \angle 45^\circ$$

$$U_W = |I_{lk}| [2 \parallel j2] = 10 \angle 90^\circ$$

$$P_W = 10 \cdot 5\sqrt{2} \cdot \cos(90 - 45^\circ)$$



$$P_W = 50 \text{ W}$$

teorija: kompenzacija jalone snage

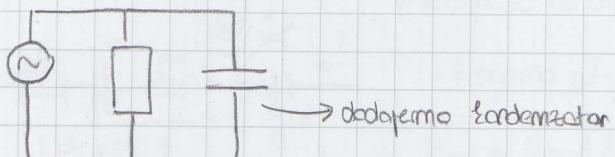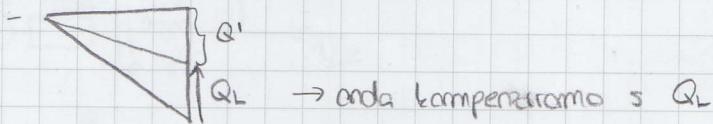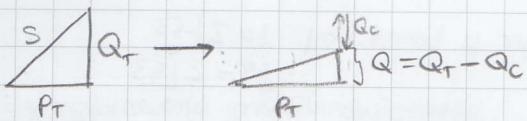


$$\textcircled{6} \quad \cos \phi = 0.707 \\ R = 22 \Omega$$

2 slučaja:

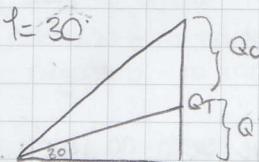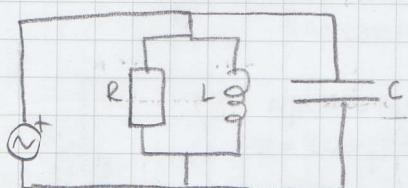

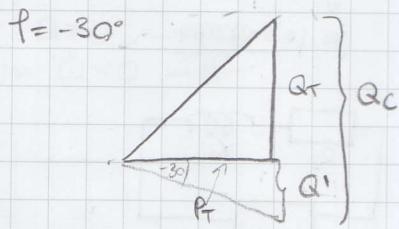$\theta = 30^\circ$
treba normirati struju
jer trebamo neformalni izpočetak



$$Q_C = \frac{|U|^2}{X_C} - \text{samo zato što je direktno spojen na izvor}$$

$$Q_C = U^2 \cdot \text{cw} \quad \rightarrow -\frac{1}{\text{cw}}$$

$$Q_C \approx C$$

P_T se ne mijenja jer: U je ISTI

I je ISTI

dodjeljuje se isti

$$P_T = \frac{22 \cdot C^2}{20} = 2200 \quad \rightarrow \text{zato što su spojeni paralelno}$$

$$Q_T = P_T \cdot \tan(\arccos 0.707) = +2200 \text{ var}$$

$$Q' = P_T \cdot \tan(30^\circ) = 1270 \text{ var}$$

$$Q' = Q_T - Q_C$$

$$Q_C = Q_T - Q' = -930 \text{ var}$$

$$-930 = -220^2 \cdot C \cdot 2\pi \cdot 50$$

$$C = 61.16 \mu\text{F}$$


$$\textcircled{7} \quad U_{AB} = 6.903 \text{ V}$$

$$I_{ef} = ?$$

$$R = X_C = X_L = 10 \Omega$$

$$I_1 = \frac{U}{10 - j10}$$

$$I_2 = \frac{U}{j10}$$

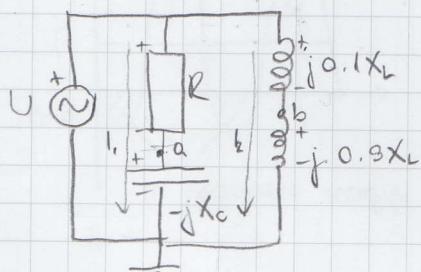

$$I_A = 0 + I_1 \cdot (1 - j10) = U \cdot \frac{-j10}{10 - j10}$$

$$I_B = 0 + I_2 \cdot j3 = U \cdot \frac{3}{10}$$

$$U_{AB} = I_A - I_B = U \frac{-j10}{10 - j10} - U \frac{3}{10} = 6.903$$


$$U \left(\frac{-j10}{10 - j10} - \frac{3}{10} \right) = 6.903$$

$$|U| = 10 \text{ V}$$

$$Z = (10 - j10) \parallel j10 \quad \rightarrow \quad Z = \frac{10}{10 + j10} = \frac{\sqrt{2}}{2} \Omega$$

$$I_{ef} = \frac{10}{10 + j10} = \frac{\sqrt{2}}{2} \text{ A}$$

(8)


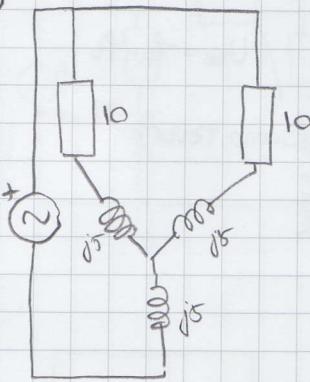


$$Z_{UK} = 5 + j2.5 + j5$$

-medno i mosni spoj

(9) $Z_1 \approx 13.14$. Odredite R_1


-pretvorba iz zvezde u trokut

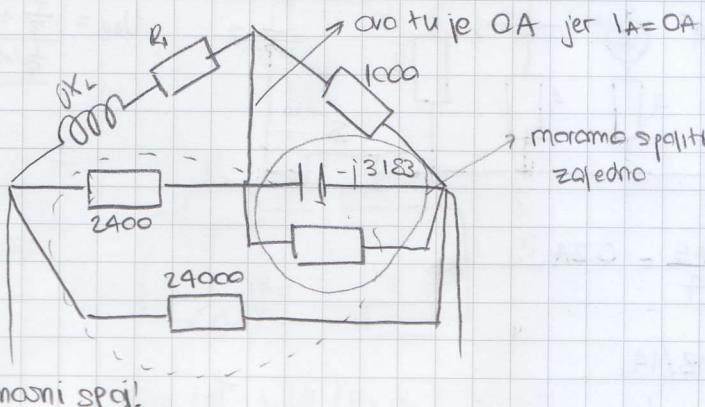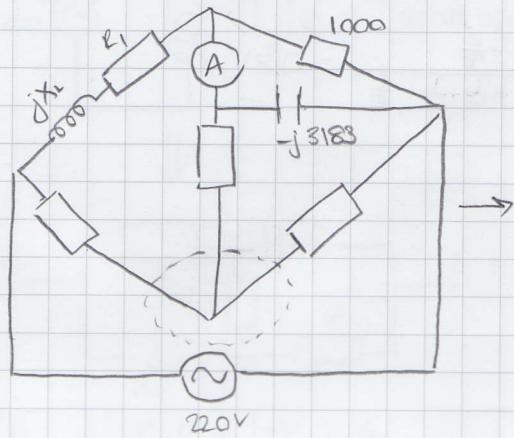

$$(R_1 + jX_L)(2400 \parallel -j3183) = 1000 \cdot 2400$$

$$R_1 + jX_L = 1000 + j754$$

(10)

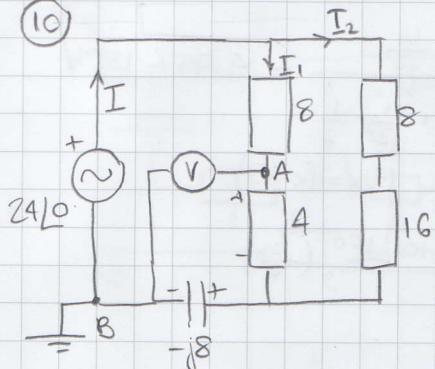

$$Z_{UK} = [(8+4) \parallel (8+16)] - j8 = 8 - j8$$

$$I = \frac{2410}{Z_{UK}} = 1.5 + j1.5A$$

$$I_1 = I \cdot \frac{24}{24+12} = 1 + j1.1A$$


$$I_A = 0 + I(1-j8) + 1 \cdot 4 = 16 - j8$$

$$I_B = 0$$

$$U_{AB} = 16 - j8 - 0$$

$$|U_{AB}| = U_r = \underline{\underline{17.9V}}$$

(11)

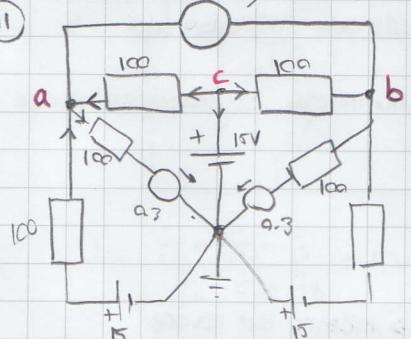

$$f_c = 0 + 15 = 15V$$

f_a : (KZS)

$$-f_a \left(\frac{1}{100} + \frac{1}{100} \right) - f_b \left(\frac{1}{100} \right) - f_c \left(\frac{1}{100} \right) - 0 \left(\frac{1}{100} + \frac{1}{100} \right)$$

$$= +0.3 + 0 - 0.3 + \underline{\underline{15}}$$



$$\xrightarrow{\text{nemamo } 100 \text{ vad}} 2f_a - \frac{15}{100} = \frac{15}{100} \Rightarrow f_a = 15V$$

$$2f_b - \frac{15}{100} = -0.6 - \frac{15}{100} \Rightarrow f_b = -30V$$


$$f_b \left(\frac{1}{100} + \frac{1}{100} \right) - f_c \left(\frac{1}{100} \right) = -0.3 - 0.3 - \frac{15}{100}$$

$$\frac{2f_b}{100} - \frac{15}{100} = -0.6 - \frac{15}{100} \Rightarrow f_b = -30V$$
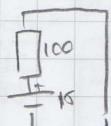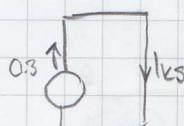
$$U_{ab} = f_a - f_b = 15 - (-30) = 45V$$



Millmanov teorem

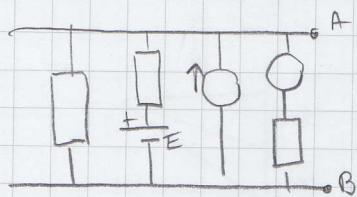

$$U_{AB} = \frac{0 + \frac{E}{R} + I + I}{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R}} \quad / \text{ nema izvora } \quad / \text{ nacrtajte } \quad / U_{AB} = f_a - f_b$$


nema otpora (samo izvor)

$$f_a \left(\frac{1}{R} + \frac{1}{R} \right) - f_b \left(\frac{1}{R} + \frac{1}{R} \right) = I + I + \frac{E}{R}$$

$$(f_a - f_b) \left(\frac{1}{R} + \frac{1}{R} \right) = I + I + \frac{E}{R}$$

$$U_{AB} = \frac{I + I + \frac{E}{R}}{\frac{1}{R} + \frac{1}{R}}$$



(12) JR 15.

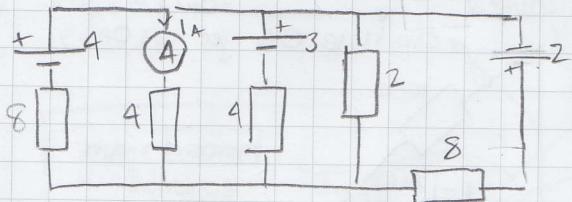

$$U_{AB} = \frac{\frac{4}{8} + \frac{3}{4} - \frac{2}{8}}{\frac{1}{8} + \frac{1}{4} + \frac{1}{4} + \frac{1}{2} + \frac{1}{8}} = 0.8V$$

$$I_A = \frac{U_{AB}}{4} = 0.2A$$

(13) ZI 13/14.

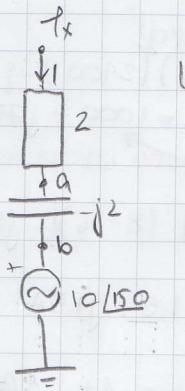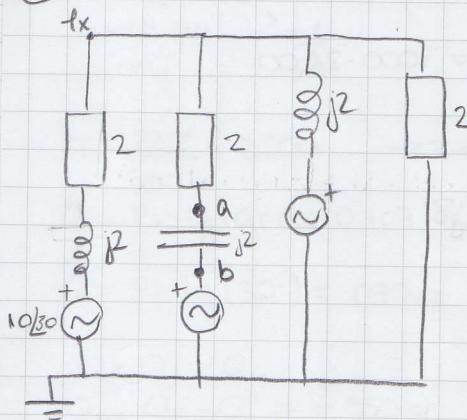

$$U_{AB} = 1 \cdot (-j2) \rightarrow I = \frac{U_{AB}}{-j2}$$

$$I = \frac{f_x - f_b}{2 - j2} = \frac{4.75 \angle -133^\circ - 10 \angle -150^\circ}{2 - j2}$$



$$U_x = \frac{U_1}{2+j2} + \frac{U_2}{2-j2} + \frac{U_3}{j2} = 4.75 \angle -133^\circ V$$

$$f_x = 4.75 \angle -133^\circ V \quad (U_x = f_x - 0)$$

$$U_{AB} = \frac{4.75 \angle -133^\circ - 10 \angle -150^\circ}{2-j2} (-j2)$$

$$= 7.1 \angle -103^\circ V$$


Theveninov teorem

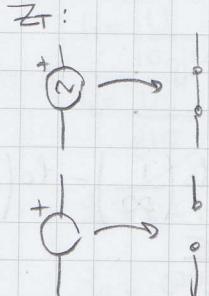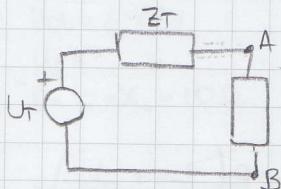


- možemo element koji nosi naziv
- uobalimo Theveninovu impedanciju

- gledamo pozivnu mrežu, istražujemo izvore


(14)

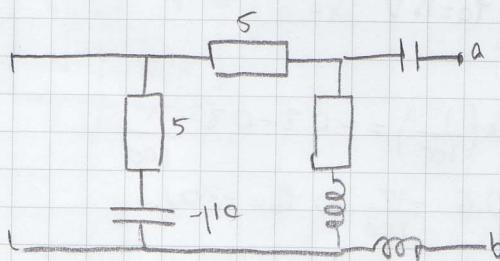

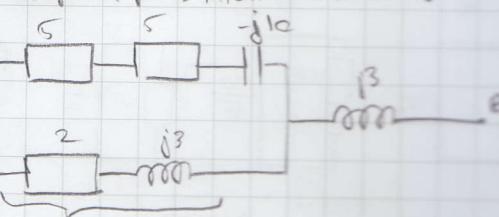tražimo impedanciju \rightarrow mićemo sve izvore



$$Z_T = 2.79 + j3.43 \Omega$$




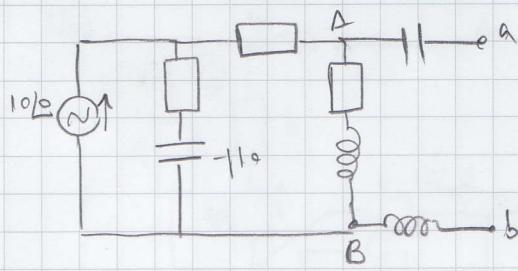


$$U_{AB} = I_2 (2 + j3)$$

$$I_2 = 10 \angle 0^\circ \left(\frac{5 - j10}{5 + 10 + (5 + 2 + j3)} \right) \\ = 8,05 \angle -33^\circ \text{ A}$$


$$U_{AB} = U_T = 29 \angle 23^\circ \text{ V}$$

(15)

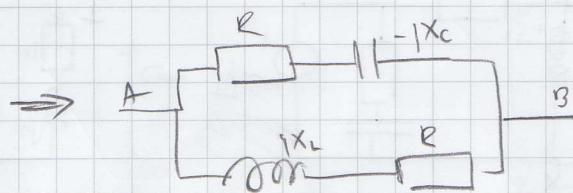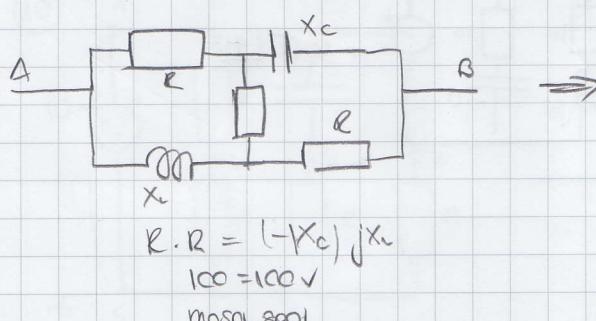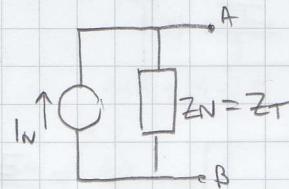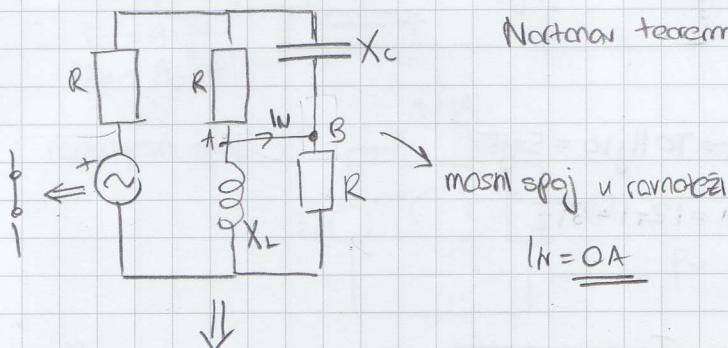

$$Z_N = (R - jX_C) // (R + jX_L) = 10 \Omega$$




(16)

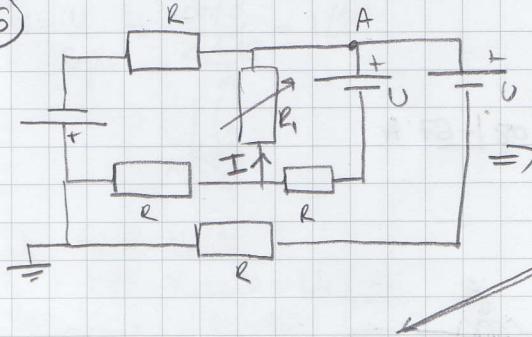

Millman


Thevenin:

míčemna zanikajici element

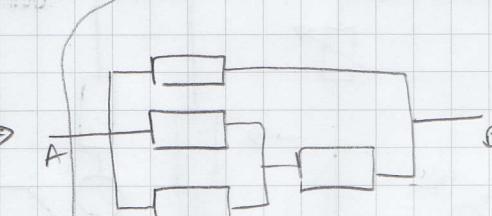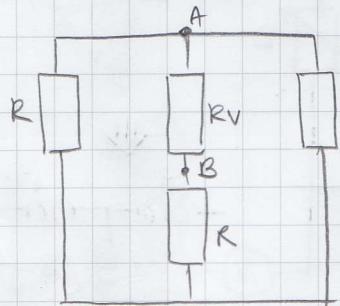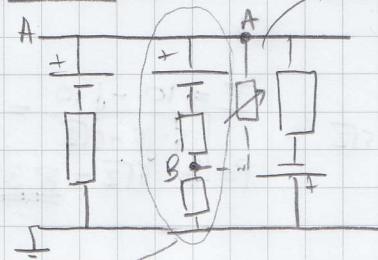


$$10 // 15 = 6 \Omega$$
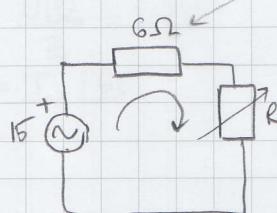
$$U = \frac{25}{10} + \frac{25}{10} + \frac{25}{10} = 5 \text{ V}$$



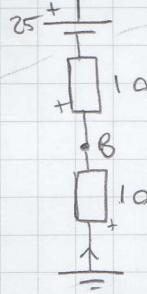
$$I = \frac{15}{6 + R_1} \\ R_1 = 9 \Omega$$




$$I = \frac{I_A - 0}{10 + 10} = -\frac{20}{20} = -1 \text{ A}$$

$$I_B = -20 + 1 \cdot 10 = -10 \text{ V}$$

$$U_T = 5 - (-10) = 15 \text{ V}$$

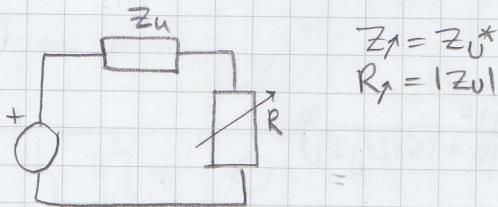

$$Z_1 = Z_U^*$$

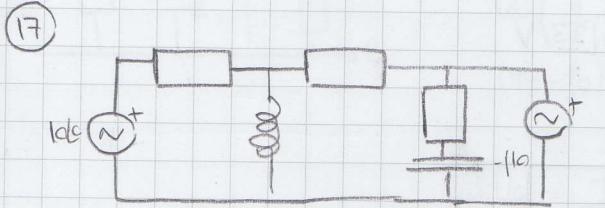


A circuit diagram showing a series circuit. The circuit consists of a rectangular loop with vertices labeled 4, 10, 18, and 6. A resistor is represented by a rectangle at vertex 10. An inductor is represented by a coil symbol at vertex 18. A capacitor is represented by two parallel lines at vertex 4. Arrows indicate the direction of current flow around the loop.

$$z_1 = 10 + j10 = 5 + j5$$

$$R_T = |Z_T| = 5\sqrt{2}$$

U_T:

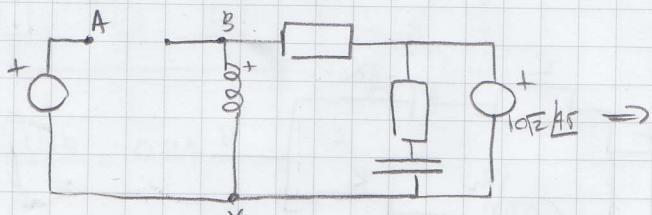


$$I = \frac{10\sqrt{2} \angle 45^\circ}{10 + j10} = \underline{\underline{1A}}$$

$$V_{ab} = f_a - f_b = f_a$$



$$f_X = -1 \cdot j(\alpha v)$$

$$f_a = f_x + i \Omega L_0 = 10 - j10V$$

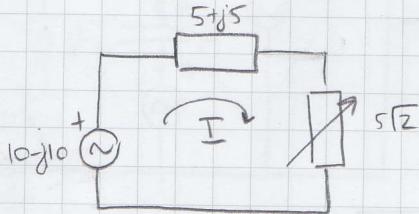



$$I = \frac{10 - j10}{5 + j5 + j\sqrt{2}} = 1.08 \angle -67^\circ A$$
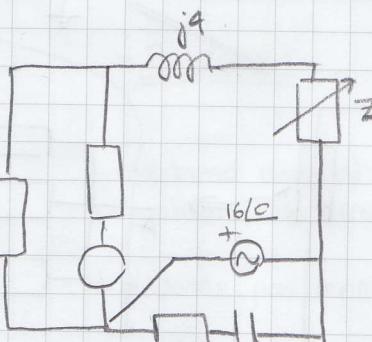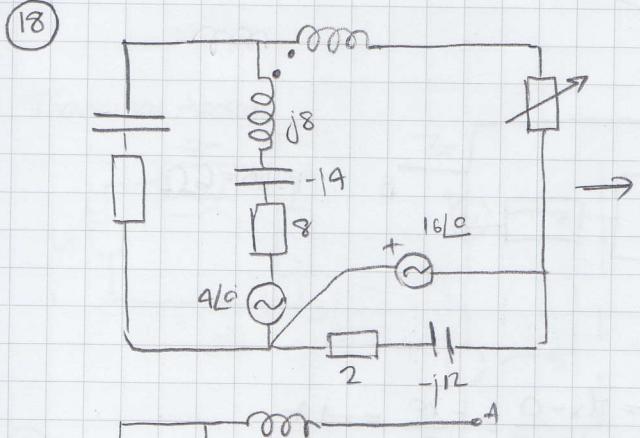
$$P = 12, \quad \underline{\underline{S\sqrt{2} = 8.3W}}$$



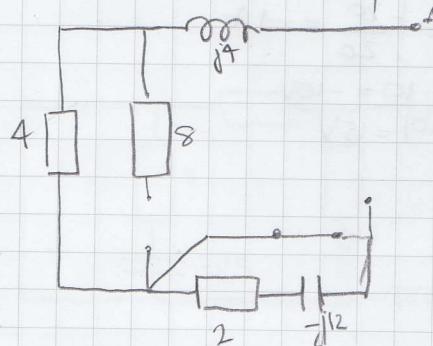The diagram illustrates a magnetic dipole moment vector j^4 pointing downwards, represented by three vertical tick marks. Below it, a horizontal line segment with arrows at both ends represents a current loop, with the label $j^8 - j^4$ positioned below the line.




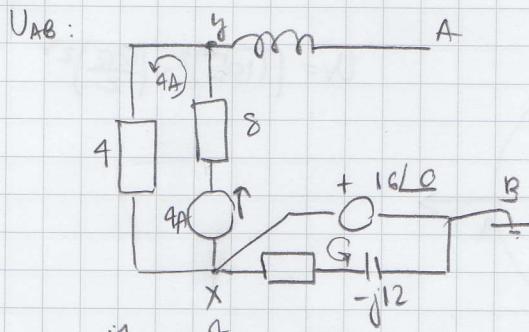

$$Z_T = 4 + j4$$

$$Z_1 = 9 - j4$$

metodam esmi spolu:

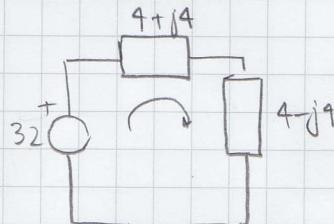

$$P_B = 0$$

$$-I_K = P_B + 16 \text{ V} = 16 \text{ V}$$

$$P_Y = P_X + 4A \cdot 4 = 16 + 16 = 32 \text{ V}$$


$$P_A + P_Y = 32 \text{ V}$$

$$U_{ab} = P_A - P_B = 32 \text{ V}$$


$$4+4 + j4 - j4$$

$$I = \frac{32}{8} = 4 \text{ A}$$
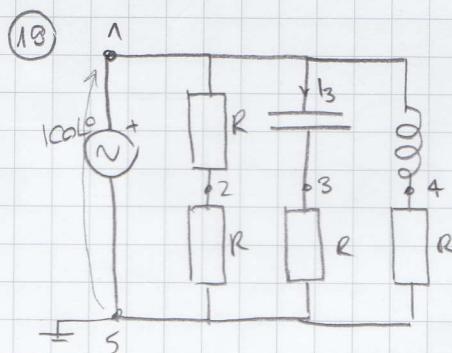
$$P = 4^2 \cdot 4 = \underline{\underline{64 \text{ W}}}$$



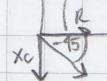
$$I_3 = \frac{U}{R-jX_c} = \frac{100 \text{ V}}{Z \angle -90^\circ} = 1 \angle 90^\circ$$



$$U_R = I_3 \cdot R = U_R \angle 90^\circ$$

$$U_C = 1 \angle 90^\circ \cdot X_L \angle -90^\circ = U_C \angle -90^\circ$$
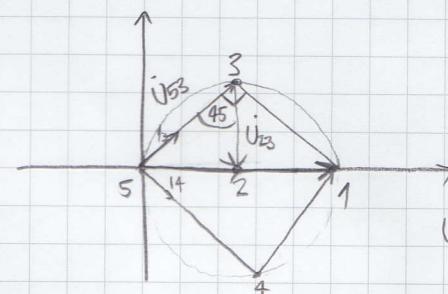
$$I_4 = \frac{U_R}{Z \angle 90^\circ} = 1 \angle -45^\circ$$




• 2. ier je impedance
grane 2R

$$3 \rightarrow 2 \quad U_{23}$$


$$2 \rightarrow 3 \quad U_{32}$$

U_{53} zaostaje za 45°

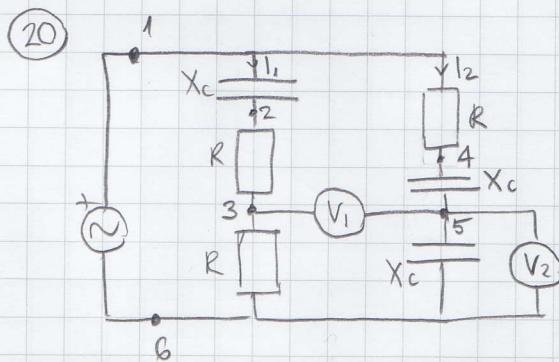

$$I_1 = \frac{U \text{ V}}{Z} = 1 \angle 26^\circ$$



$$I_2 = I_1 \angle 63^\circ$$

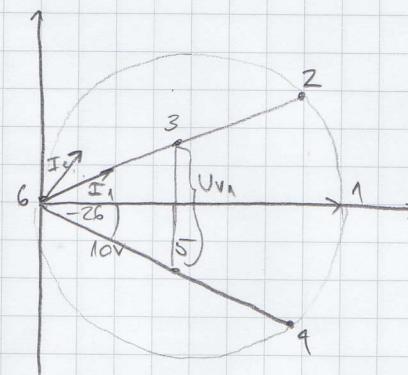

$$\underline{\underline{U_{11} = 10 \sin(26)}}$$

$$\underline{\underline{U_{12} = 2 \cdot 10 \sin(26)}}$$

21)

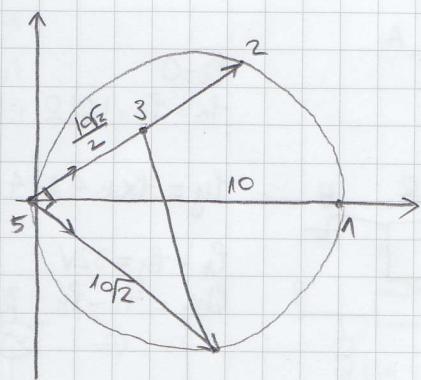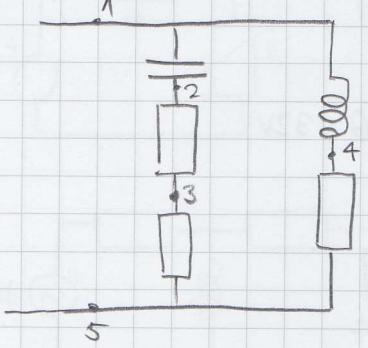

$$U = \sqrt{(10\sqrt{2})^2 + (10\sqrt{2})^2}$$