

Elementi - samo pasivni  $\rightarrow$  6



moraš postaviti smjerove struja da bi svi imali isto rješenje

3 vrste matrica - za varijable

- za stavljanje elemenata

orientirani graf - služi za opisivanje izgleda mreže

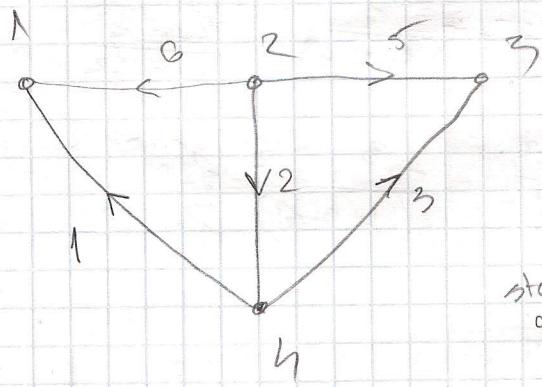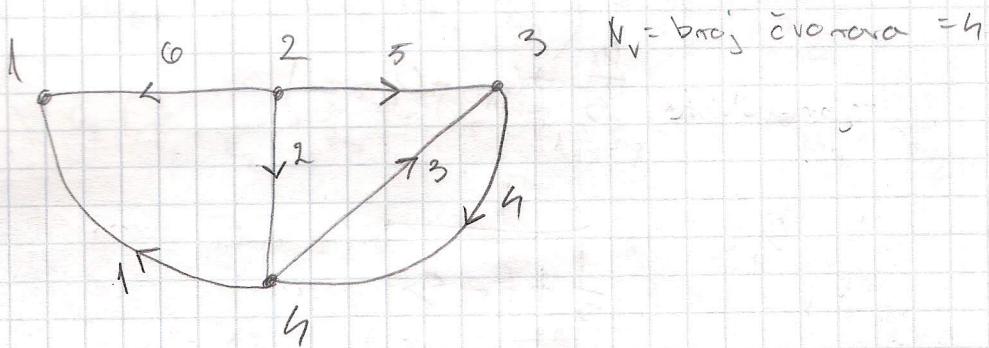jedna grana ima 1 element  $\Rightarrow N_b$  broj grana = 6



stablo - najmanji broj grana

koje će spojiti sve čvorove

6, 5, 3  $\rightarrow$  spome

$$\text{broj stablnih grana} \approx N_t = N_v - 1$$

$$\text{broj spome} \approx N_s = N_b - N_t$$

$$A \rightarrow (N_v - 1) \times N_b = 3 \times 6$$

uzemljeni čvor ne ulazi u matricu

$$A = \begin{bmatrix} -1 & 0 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & -1 & 1 & -1 & 0 \end{bmatrix} \begin{array}{l} \check{c}_1 \\ \check{c}_2 \\ \check{c}_3 \end{array}$$

matrica incidencija - odnos



grana i čvorova  
ulazi -1 izlazi 1 nema -0

$S$  = spojna matrica, u njoj ulaze petlje


$$S \rightarrow N_f \times N_b = 3 \times 6$$

$$S = \begin{bmatrix} 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 1 & 0 \\ -1 & -1 & 0 & 0 & 0 & 1 \end{bmatrix} \quad \begin{array}{l} P_1 \\ P_2 \\ P_3 \end{array}$$

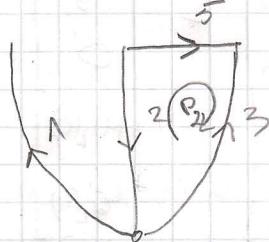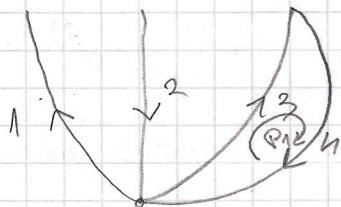$g_1 \ g_2 \ g_3 \ g_n \ g_5 \ g_6$  jedinična matrica ako smo pravilno radići



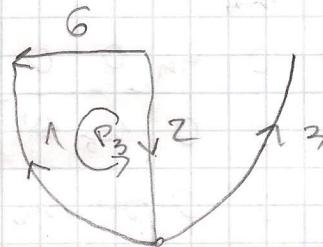stablo ne čini petlju, dodavanjem spone dobivamo petlju




smjer petlje je u smjeru spone grana u smjeru petlje 1, kontra -1, menaju veze 0

$$Q \rightarrow N_f \times N_b = 3 \times 6 \text{ matrica rezova}$$

$$Q = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 & 1 & 0 \end{bmatrix} \quad \begin{array}{l} R_1 \\ R_2 \\ R_3 \end{array}$$

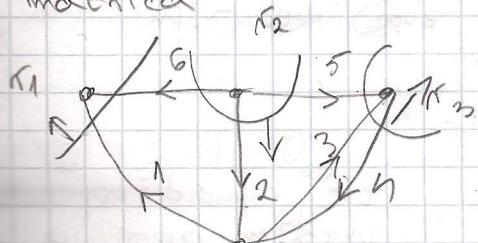$g_1 \ g_2 \ g_3 \ g_n \ g_5 \ g_6$  jedinična matrica



sveki rez treba prevezati jednu stablenu granu i me mora možmo bit ravni - rez je u smjeru one grane koju smo prevezali

u smjeru rez -1, kontra -1, menja -0

matrice strujno-napomskih odnosa

$$U_b = Z_b I_b + U_{ob}$$

$$I_b = \gamma_b U_b + I_{ob}$$

$$\begin{bmatrix} U_1 \\ U_2 \\ U_3 \\ U_n \\ U_5 \\ U_6 \end{bmatrix} = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 \\ \mu R_1 & \frac{1}{3C_2} & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{3C_3} & 0 & 0 & 0 \\ 0 & 0 & 0 & R_n & 0 & 0 \\ 0 & 0 & 0 & 0 & sL_5 & sM \\ 0 & 0 & 0 & 0 & sM & sL_6 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_n \\ I_5 \\ I_6 \end{bmatrix} + \begin{bmatrix} -U_0 \\ -\mu U_0 \\ -\frac{U_c(0)}{3} \\ 0 \\ M I_2(0) \\ I_6(0) \end{bmatrix}$$


6x6 jer

je 6 grana

6 struja

grana

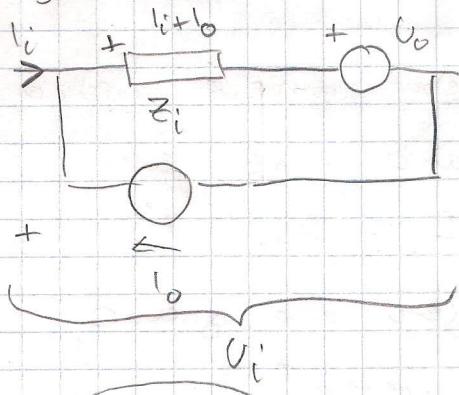jedna grana mora imati jedan element, mogu mu bit priđeljeni jedan napomski i jedan strujni izvor



pariti dali se poklapaju sa strujom  $I_i$

$$U_i = Z_i(I_i + I_o) + U_o$$

$$U_1 = I_1 \cdot R_1 - U_0$$

$$U_2 = I_2 \cdot \frac{1}{3C_2} + \mu U_1$$

$$U_3 = I_3 \cdot \frac{1}{3C_3} \cdot I_3 - \frac{U_c(0)}{3}$$

$$U_n = R_n I_n$$

$$U_5 = \left( I_6 + \frac{I_L(0)}{s} \right) sL_5 + sM I_5$$

$$U_6 = I_5 sL_5 + sM \left( I_6 + \frac{I_L(0)}{s} \right)$$

zbog međuinduktiviteta

ove jednadžbe vrstim gore u matrice

točka prebacim plus znak kako ga vidi

ako strujni početni uvjet imamo na zavojnicu koja ima međuinduktivitet ostavimo ga tako jer ako ga prebacimo u napomski moramo ga

staviti i u drugu zavojnicu

$$U_2 = \frac{1}{3C_2} \cdot I_2 + \mu \cdot R_1 I_1 - \mu U_0 \text{ jer je ovisan napomski izvor}$$

ne smije postojati ovisnost napona o naporu, ali može o strujama

$$I_G = \frac{1}{sL_G} U_G - \frac{i_L(o)}{s} - \frac{N}{L_G} I_S$$

$$U_b = Z_b I_b + U_{ob}$$

$$I_b = Y_b U_b + I_{ob}$$

$$Z_p I_p = U_{op}$$

$$Z_p = S \cdot Z_b \cdot S^T$$

$$Y_b = Z_b^{-1}$$

$$U_{op} = -S U_{ob} = S \cdot Z_b I_{ob}$$

iz njih se mogu odrediti ostale matricne jednadžbe

$$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \text{za petlje}$$

- za čvorove koristimo matricu  $A$ , a za rezorce  $Q$


$$Y_\pi U_\pi = I_\pi$$

$$Y_\pi = Q \cdot Y_b \cdot Q^T$$


$$\frac{1}{\frac{R_1}{SC_2} - \alpha \mu R_1} \begin{bmatrix} \frac{1}{SC_2} & -\mu R_1 \\ -\alpha \mu R_1 & R_1 \end{bmatrix}^T = \frac{SC_2}{R_1} \begin{bmatrix} \frac{1}{SC_2} & -\alpha \\ -\mu R_1 & R_1 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} & 0 \\ -\mu SC_2 & SC_2 \end{bmatrix}$$


$$Y_b = \begin{bmatrix} \frac{1}{R_1} & 0 & 0 & 0 & 0 & 0 \\ -\mu SC_2 & SC_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & SC_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{R_4} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$I_\pi = Q \cdot Y_b \cdot U_{ob}$$



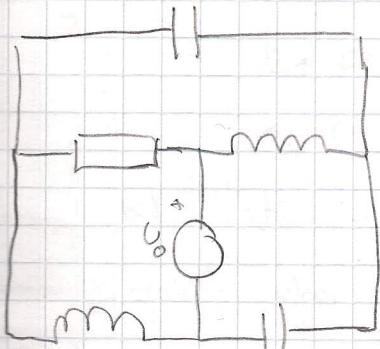


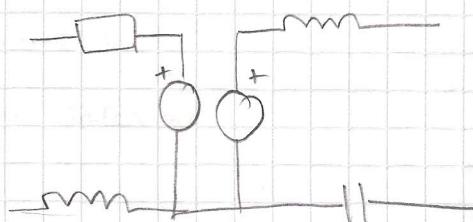izvor nije s ničim u seriji  $\rightarrow$  posmicanje izvora



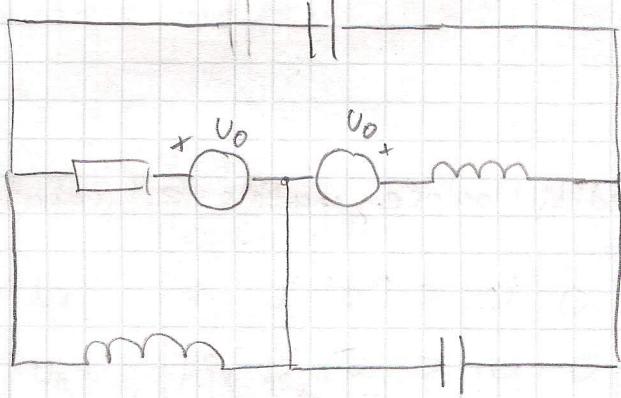


ili:

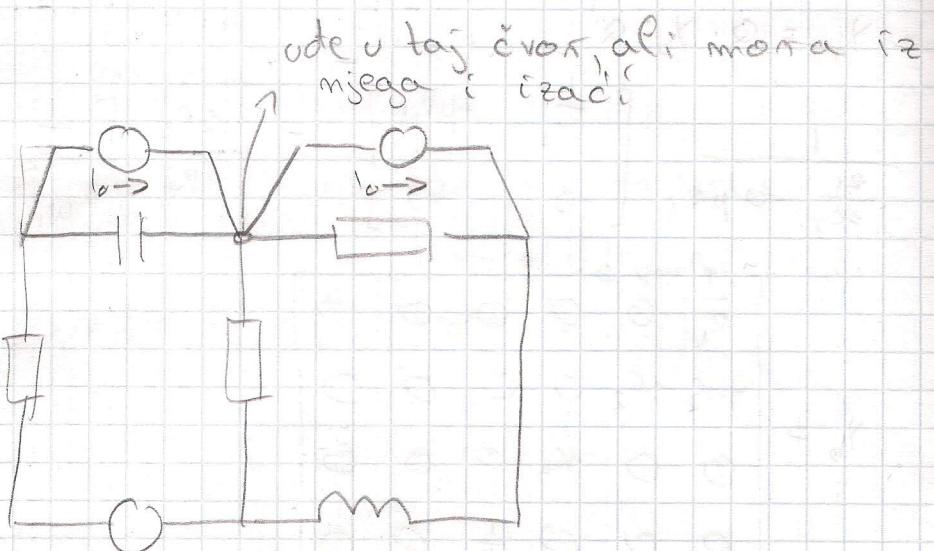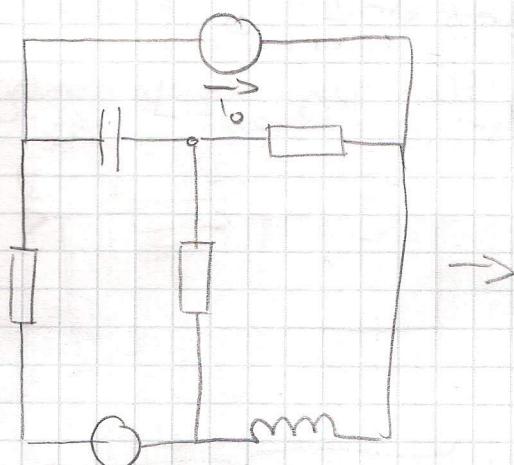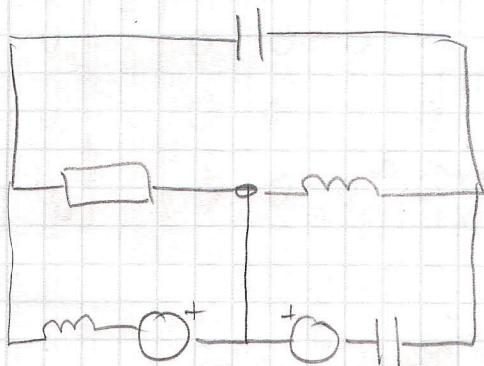
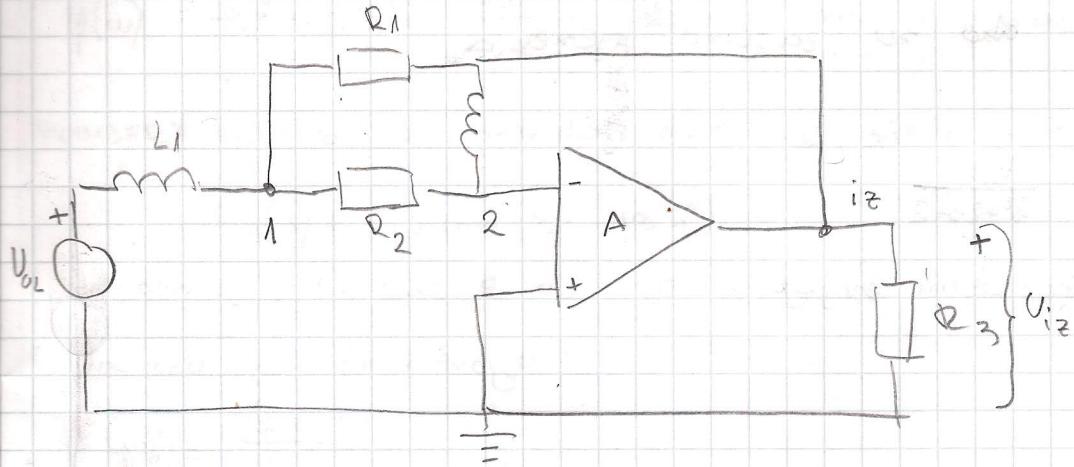
# PAUZA

smjerovi izvora ostaju isti

paziti ako imamo neki drugi  
ovisni izvor jer onda mijenjamo  
mapome i struje



$$R_1 = R_2 = R$$

$$L_1 = 1$$

$$L_2 = 2$$

$$R_3 = 3$$

$$A \rightarrow \infty$$

$$T(s) = \frac{U_{iz}(s)}{U_{il}(s)}$$

majčesice se to traži

majčesice se koristi metoda napoma čvorova

$$1. \quad U_1 \left( \frac{1}{sL_1} + \frac{1}{R_2} + \frac{1}{R_1} \right) - U_2 \frac{1}{R_2} - U_{iz} \cdot \frac{1}{R_1} = U_{il} \frac{1}{sL_1}$$

$$2. \quad U_2 \left( \frac{1}{R_2} + \frac{1}{sL_2} \right) - U_1 \cdot \frac{1}{R_2} - U_{iz} \frac{1}{sL_2} = 0$$

$$U_2 = 0$$

$$U_{iz} = U_{il} \cdot \frac{2s}{s^2 + 2s + 2}$$

$$T(s) = \frac{-2s}{s^2 + 2s + 2}$$

prijenosna funkcija

$\rightarrow$  polovi  $\Rightarrow$  mazivnik = 0

$$\times \quad s^2 + 2s + 2 = 0 \quad s_{\alpha} = \frac{-2 \pm \sqrt{4}}{2}$$

omoliko koliko imamo spremnika energije tolikog je stupnja ova jednadžba

$\rightarrow$  mala  $\Rightarrow$  brojnik = 0

$$0$$

$$2s = 0$$

$$s_{\alpha 1} = 0 \quad s_{\alpha 2} \rightarrow \infty$$


mora biti isti broj polova i nula

sustav je stabilan ako je svim polovima

$$\operatorname{Re}\{s_{\alpha i}\} < 0$$

granično stabilan: barem jedan pol  $\operatorname{Re}\{s_{\alpha i}\} = 0$

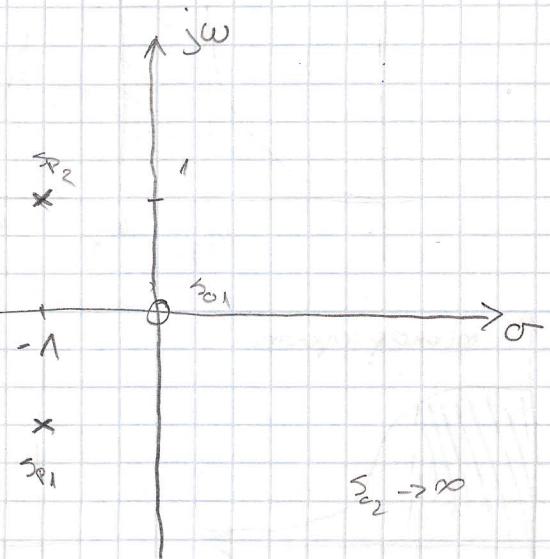nestabilan barem jedan  $\operatorname{Re}\{s_{\alpha i}\} > 0$



$$T(s) = \frac{\pi(s - s_{oi})}{\pi(s - s_{ei})} \cdot K \quad \text{ako su zadana rješenja}$$

$$T(s) = \frac{(s-0)(s-\infty)}{(s+1+j)(s+1-j)} \cdot K = \frac{ks}{s^2 + 2s + 2}$$

$$T(1) = \frac{2}{2} \quad \text{zadan početni uvjet}$$

$$T(1) = \frac{k \cdot 1}{1+2+2} = \frac{-k}{2}$$

$$k = -2$$

### FREKVENCISKA KARAKTERISTIKA

- nakon nekog vremena frekvencije dodu možu 0

- dok se to ne dogodi traje prijelazna pojava

$$T(j\omega) = T(s) \Big|_{s=j\omega} = \frac{-2j\omega}{(j\omega)^2 + 2j\omega + 2} = \frac{-2j\omega}{2 - \omega^2 + 2j\omega} = |T(j\omega)| e^{j \arg T(j\omega)} = A(\omega) \angle \varphi(\omega)$$


$$A(\omega) = \left| \frac{-2j\omega}{2 - \omega^2 + 2j\omega} \right| = \frac{2\omega}{\sqrt{(2 - \omega^2)^2 + 4\omega^2}}$$

amplituda je pozitivni realni broj




$$A(\omega) [dB] = 20 \log A(\omega) = 20 \log 2\omega - 20 \log \sqrt{(2 - \omega^2)^2 + (2\omega)^2}$$

$$A(\omega=0)=0$$

$$A(\omega \rightarrow \infty) = 0$$

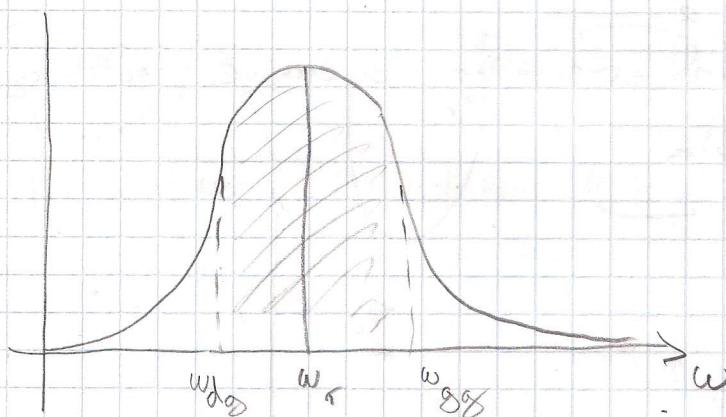

Pojasno propusni filter

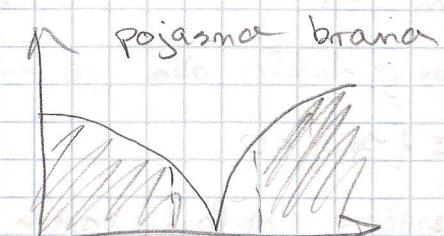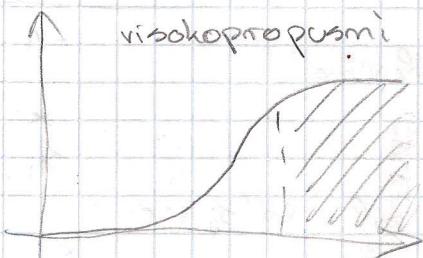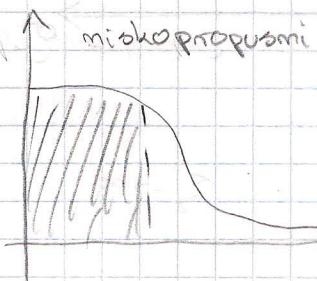

$$\varphi(w) = -90^\circ - \arctan \frac{2w}{2-w^2} \quad \text{paziti na kvadrant}$$

PRIMER: Kolika je pobuda ako je odziv u stacionarnom stanju?

$$U_{iz}(t) = 5,2 \cos(3t - 10,4^\circ)$$

prirodne frekvencije su se priužile i sustav se ponaša kao da mu je frekvencija 3

$$T(j\omega_0) = \frac{U_{iz}}{U_{0z}}$$

$$U_{iz} = 5,2 \underbrace{\text{ } \text{ } \text{ } \text{ } \text{ } \text{ }}_{10,4^\circ} \quad \omega_0 = 3$$

$$U_{0L} = \frac{U_{iz}}{T(j3)}$$

$$A(3) = \frac{2 \cdot 3}{\sqrt{(2 \cdot 0)^2 + 2 \cdot 3^2}} = 0,67$$

$$\varphi(3) = -90^\circ - \arctan \frac{6}{-7} = -90 - (-10,6 + 180^\circ) = -130,6$$

$$U_{0L} = \frac{5,2 \underbrace{\text{ } \text{ } \text{ } \text{ } \text{ }}_{10,4^\circ}}{0,67 \underbrace{\text{ } \text{ } \text{ } \text{ } \text{ }}_{-130,6}} = 8 \underbrace{\text{ } \text{ } \text{ } \text{ } \text{ }}_{-150^\circ}$$

$$U_{0L}(t) = 8 \cos(3t - 150^\circ)$$