

ZADACI SE MOGU

NACI NAI:

[morgoth.zemris.fei.hr/diglog/!!](http://morgoth.zemris.fei.hr/diglog/)

## MASOVNE




$$A \cdot B$$



A	B	I	IL	XOR
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0

$$A \rightarrow A$$

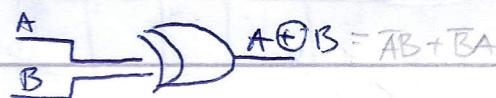

$$\begin{aligned} A \cdot A &= A \\ A \cdot 1 &= A \\ A \cdot 0 &= 0 \\ A + 1 &= 1 \end{aligned}$$

1. zadatok

P1:

$$L = 001100110$$

minimizacija distanca - broj bitova u tojini seta

$$B = 101010101$$

dva broja razlikuju

$$R = 010101010$$

otključuje grešku  $d_{min} \geq t+1$

$$L: B \quad d=5$$

$$d_{min} = 4$$

$$t \geq 2t+1$$

$$L: R \quad (d=4)$$

$$t = 1,5 \rightarrow \text{zaključujemo na prvi redak}$$

cijeli broj (logično, jer ve moći  
npr. poda grešku ispraviti)

## Hammingov kod

nepotpuni paket  $\rightarrow$  samo se broji koliko je jedinica  $\oplus 1010111$  pa samo

stavi ispred (priaviti isti princip)  $\rightarrow$  (može se i staviti ispred, ali ispred je čeće)

## Zad.

67  $\rightarrow$  zapisati nepotpun paritetni Hammingov kod (Hammingov kod - zapisi tu broj bitova za niti

$$E = 1100 \rightarrow 1110011$$

$$P = 12345678$$

$$F = 0111$$

$$\begin{array}{ccccccccc} C_0 & C_1 & P_1 & C_2 & P_2 & C_3 & P_3 & C_4 & P_4 \\ \underline{0} & \underline{1} & \underline{1} & \underline{0} & \underline{1} & \underline{0} & \underline{0} & \underline{1} & \underline{1} \end{array}$$

potezji broj 2 (po koliko ih  
stoji i preostalo  $\rightarrow 2^1 \rightarrow$  sebe  
ili neko drugi,  $2^2 =$  sebe i 7)  
Rokanj po 8 poteza ...)

$$R_j = 011011000111$$

2006-2007. 1 MI 2. zad

BCD Redovizam

$$\Sigma_m(0, 1, 2, 3, 4, 5, 6, 7, 8, 9)$$

$x_3 x_2 x_1 x_0 x_2$	$x_3 x_2 x_1 x_0 x_1$	$x_3 x_2 x_1 x_0 x_0$
$x_3 x_2$	$x_3 x_2$	$x_3 x_2$
$x_0 x_2$	$x_0 x_2$	$x_0 x_2$
$x_3$	$x_3$	$x_3$
$x_2$	$x_2$	$x_2$
$x_1$	$x_1$	$x_1$
$x_0$	$x_0$	$x_0$
00	00	00
01	01	01
10	10	10
11	11	11
12	12	12
13	13	13
14	14	14
15	15	15
16	16	16
17	17	17
18	18	18
19	19	19

$$\bar{x}_3 + \bar{x}_1 x_2$$

BCD

0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	
1011	
1100	
1101	
1110	
1111	

XSS

0000	00
0001	01
0010	10
0011	11
0100	00
0101	01
0110	10
0111	11
1000	00
1001	01
1010	10
1011	11
1100	00
1101	01
1110	10
1111	11

Aiken (2421)

0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	
1011	
1100	
1101	
1110	
1111	

ne koriste

$x^1$

→ ne smije se u tim krajnjim zbiranjima → pretvara se u detakški, pa

zbroji pa opet pretvara u taj kod

upr.

BCD

$$\begin{array}{l} 1000\ 1000 \\ 70100\ 0100 \\ \hline 132 \end{array} \rightarrow 000100110010$$

K tablice - služe za minimizaciju funkcije

minfunk - međusobno se zbiraju, a unutar sebe se mnoge

maksfunk - obrnuto

$$\begin{array}{l} x\ y\ z \\ 0\ 0\ 0 \\ \bar{x}\cdot\bar{y}\cdot\bar{z} \\ (\text{kad je } f=1) \end{array}$$

$$\begin{array}{l} x\ y\ z \\ 0\ 0\ 0 \\ x+y+z \\ (\text{kad je } f=0) \end{array}$$

zadatci s predušenim zadatcima u kojima se radi o funkciji s  
četiri ulazne varijable i dve izlazne varijable. U zadatku je  
potrebno odrediti funkciju.

$$f(A, B, C, D) = \overline{A}B\overline{C} + \overline{A}CD$$

	AB	CD		
	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$\overline{A}BD$  (hazard)

(c)

A

ZAD

X	X	X	X
1			1

ZADATAK 1. (1.MI. (2006/2007.) grupa A)

(ordje se g i f zadace)

$$z: (A, B, C, D) = (f \oplus 1) \cdot g$$

	AB	CD								
	00	01	11	10	g AB					
	00	1			1	1				
	01	1	1	1		1	1	1	1	1
	11	1	1			1	1	1	1	1
	10	1				1			1	1

$f \oplus 1$

$\oplus 1$

Xorana f

1

$$(f \oplus 1) \cdot g$$

	1	1	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1	1	1
	1				1	1	1	1	1	1

tomo gdje se  
predajući 1  
stavlja u  
tu tablicu

$$\text{jednije je: } z = \prod M(2, 4, 7, 11)$$

14. Potreba je projektovati komparator dvočifrenih brojeva  $a_1a_0$  i  $b_1b_0$ . Rezultat je broja popisanih 1 sa kojim je  $a \geq b$ . Minimalni oblik je  $f(a_1, a_0, b_1, b_0)$ : gledaj:

$$\underbrace{01 \ 10}_{a} = 2$$

$$1 \quad a \quad b$$

$a_1$	$a_0$	$b_1$	$b_0$	$c$		$a_1a_0$	$b_1b_0$	$a_0$
0	0	0	0	0	0	00	00	0
0	0	0	1	0	0	00	01	1
0	0	1	0	0	0	01	10	1
0	0	1	1	0	0	01	11	1
0	1	0	0	1	1	10	00	0
0	1	0	1	1	1	10	01	1
0	1	1	0	0	0	11	10	1
0	1	1	1	0	0	11	11	1
1	0	0	0	1	1	11	00	0
1	0	0	1	1	1	11	01	1
1	0	1	0	1	1	10	10	0
1	0	1	1	0	0	10	11	1
1	1	0	0	1	1	11	11	1
1	1	0	1	1	1	11	10	1
1	1	1	0	1	1	11	11	1
1	1	1	1	1	1	11	11	1

$$f_j = \overline{b_1b_0} + a_1a_0 + a_0\overline{b_1} + a_1\overline{b_1} + a_1\overline{b_0}$$

Pravilo (F(A, B, C))

$\sum m(0, 1, 2, 7)$

$\prod M(3, 4, 5, 6)$

$$ABC \rightarrow AB + CA \vdash A \wedge A \wedge A$$

$$\begin{array}{c} 000 \\ 001 \\ 010 \\ 011 \end{array} \quad m(5, 6, 7)$$

$$\begin{array}{c} 100 \\ 101 \\ 110 \\ 111 \end{array} \quad M(0, 1, 2, 3, 4)$$

implikant  
 $(A+B+C) \cdot (A+\overline{B}+\overline{C})$

A · B · C

primarni implikanti - implikanti koji se više ne mogu skraćiti

bitni primarni implikant

Zad.  $m(38, 42, 46, 50, 54) \rightarrow$  odvijimo potencije  $\rightarrow$  broj 38 i sad venu

$38 = 100110 \rightarrow$  npr. 64, to ne može da 38 adresi, pa

↓

uzeti 32  $\rightarrow$  može adresati i staviti 1,

$f_j: 16 \ 8 \ 4 \ 2 \cdot 1 \rightarrow$  potencije  $\rightarrow$  pa sledi da (osim 4 i 8) ne može, pa

8 ne, 4 može, ostalo 2, pa 2 može i 1 ne može.

		→ brojilo jedinice								
		A	B	C	D	E	F			
38	-100110	-3								
42	-101010	-3	$\sqrt{38}$	1	0	0	1	1	0	grup od
46	-101110	-4	$\sqrt{42}$	1	0	1	0	1	0	3 jedinica
50	-1100010	-3	$\sqrt{46}$	1	1	0	0	1	0	
54	110110	-4	$\sqrt{50}$	1	0	1	1	1	0	grup od
			$\sqrt{54}$	1	1	0	1	1	0	4 jedinice
$x=4$										

$x = \text{primarni}$	$\{ 38, 46$	1 0 - 1 1 0
$x = \text{implizanti}$	$\{ 38, 54$	1 - 0 1 1 0
	$\{ 42, 46$	1 0 1 - 1 0
	$\{ 50, 54$	1 1 0 - 1 0

	38	42	46	50	54
38,46	+	+			
38,54	+			+	
42,46		(+)	+		
50,54				(+)	+

→ otkradao mape i gođe je  
samo jedan + koji će biti

u konacnj funkciji oni su  
bitni primarni implizanti

MIN SOLA

$$y = z \quad \overline{B \cdot A} = K$$

$$z = 2$$




$$f = \bar{A}\bar{B}C\bar{E}\bar{F} + A\bar{B}\bar{C}E\bar{F} + \bar{A}\bar{B}D\bar{E}\bar{F} \\ \text{ili} \quad + \bar{A}\bar{C}D\bar{E}\bar{F}$$

to funkcija je

tako pisao

101. SUTAN




$$\overline{B \cdot A} = C$$

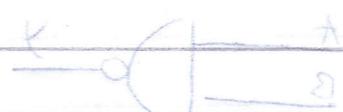

sud obavešt 3UR

$$\overline{B \cdot A} = \overline{B} \cdot \overline{A}$$
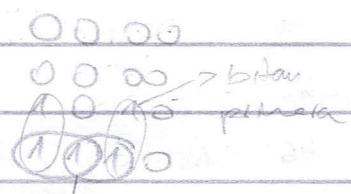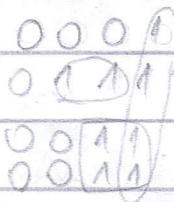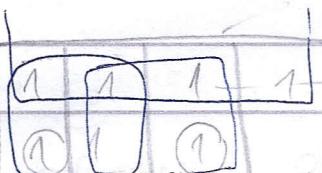
$$\overline{B \cdot A} = \overline{B} \cdot \overline{A} = \overline{B} \cdot \overline{A}$$



bitan primarni - ab se jedinice obični prikaz  
mora na samo jedan nacin zaključiti

MAXTERM

dakli primarni - tako ce mora 1 ne vise koliko

$$\begin{array}{c} AB \\ \text{CO} \end{array} \quad \begin{array}{c} 00 \\ 01 \\ 11 \\ 10 \end{array}$$

zaključiti


00 00 01 11 10  $\rightarrow$  zaključuje mala bit polencija broj 2

$$\begin{array}{c} A \\ \text{S} \\ \text{T} \\ \text{I} \\ \text{O} \end{array} \quad \begin{array}{c} 00 \\ 01 \\ 11 \\ 10 \end{array}$$


$$(A+C+D) \cdot (\bar{B}+\bar{D}) \cdot (\bar{A}+D+\bar{C})$$



NOR/NLU

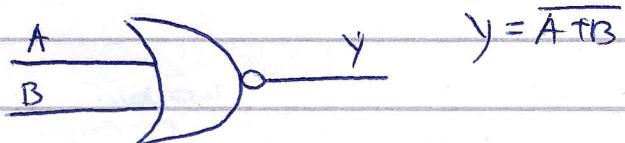

NAND/NL

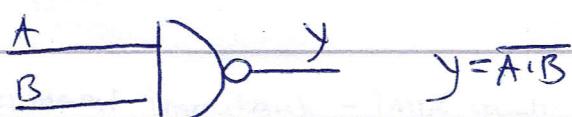

SLE PONODU NOR

$$A \cdot B = \overline{\overline{A} + \overline{B}}$$

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

$$A \rightarrow B = \overline{A} + B$$


$$\overline{A} \rightarrow \overline{B} = \overline{A} \cdot \overline{B}$$

$$A \rightarrow \overline{B} = \overline{A} \cdot B$$

$$\overline{A} + \overline{B} = A \cdot B$$


$$B \rightarrow \overline{B} = \overline{B}$$

## NAND

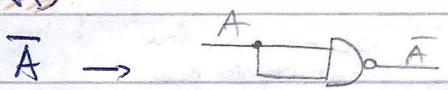


$B + \overline{B} = 1$

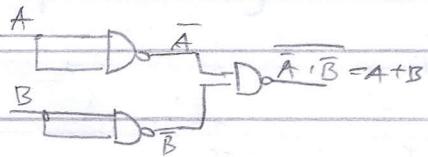$A + B = \overline{\overline{A} \cdot \overline{B}}$



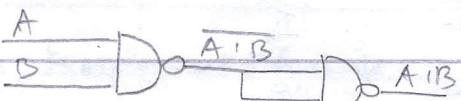$A \cdot B = \overline{\overline{A} \cdot \overline{B}}$



$\overline{A} \neq \overline{A}$   
NET!!!

ZAD. samo NOR

$f = B \cdot (\overline{C} \cdot B) + (\overline{B} \cdot (\overline{A} \cdot \overline{C}))$

$\overline{A} \cdot \overline{C} = \overline{\overline{A} + \overline{C}} = \overline{A} + \overline{C}$

$f = \overline{B} \cdot \overline{C} + (\overline{B} \cdot (\overline{A} + \overline{C}))$

$f = \overline{B} \cdot \overline{C} + \overline{B} \cdot \overline{A} + \overline{B} \cdot \overline{C}$

gamo sam si označil  
že obuvach  
keji TO SE NE ERTAJI!!!

$f = \overline{C} \cdot (\overline{B} + \overline{B}) + \overline{B} \cdot \overline{A}$

$\text{NOR}(C) = \text{NOR}(C, C)$

$f = \overline{C} + \overline{B} \cdot \overline{A}$

$f = \overline{C} + \overline{A} + \overline{B}$

$\text{NOR}(\text{NOR}(\text{NOR}(C), \text{NOR}(A, B)))$

left:  $(\text{NOR}(\text{NOR}(\text{NOR}(C), \text{NOR}(A, B))))$

ZAD. samo NAND

$\overline{A}(\overline{B}C + \overline{B}\overline{C}) + A\overline{C}\overline{D} + C\overline{D}$

$(\overline{A} \cdot \overline{D}) \oplus (\overline{B} \cdot \overline{C})$  je to logický sklopovač, Z DATAGAS

$\overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C} + A\overline{C}\overline{D} + C\overline{D}$

samo prebrojí vseove / aendove

$\underbrace{\overline{AB}}_1 + \underbrace{\overline{CD}}_1$


$3^2 \cdot 2^4 = 9$

$\overline{AB} + \overline{CD}$

$\overline{\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}}$

NAND(NAND(NAND(A), B), NAND(C, NAND(D)))

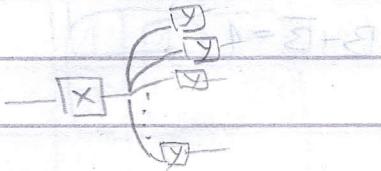**ZADATAK 3.** (Z.MI. (2006/2007) grupa A): Za dveje polodice integriranih logičkih sklopova poznati su podaci prikazani u tabelici. Ako se u nekom sistemu sastavi sklopovi polodice  $P_1$ , pobudjuj sklopove polodice  $P_2$ , koliko se najviše sklopova polodice  $P_2$  može spojiti na ulaz iz jednog sklopa  $P_1$ ?



OL - output low (h-low)  
IL - input low = A

DAVNI

	$I_{OL}$	$I_{OH}$	$I_{IL}$	$I_{IH}$	$I_O$	$I_{OL}$	$I_{OH}$	$I_{IL}$	$I_{IH}$	$I_O$
$n_1$	10	20	10	20	20	10	20	10	20	20
$n_2$	10	20	10	20	20	10	20	10	20	20
$n_3$	10	20	10	20	20	10	20	10	20	20

! pažiti na ujemne jedinice

$$\overline{B} \cdot A = B \cdot \overline{A}$$

$n_1$

vrijma se minimum od tih dva broja

$$I_{OL_1} = I_{OH_1}$$

$$I_{IL_2} = I_{IH_2}$$


(Ustvari očekujemo koliko sklopova moramo)

Spojiti a da prethni sklop ne pregoli

$$h_0 \quad (10) \quad c) (10)$$

**ZADATAK 4.** (Z.MI. (2006/2007) grupa A)

0-OUTPUT!      1-INPUT!

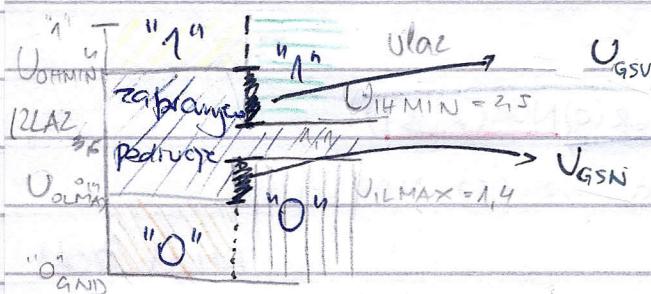

$$U_{OHMIN} - U_{IHMIN} = U_{GSV} - 3.15$$

$$U_{OLMAX} - U_{ILMAX} = U_{GSV} + 0.44$$

$$U_{OLMAX} = 0.4V \quad U_{IHMIN} = 2.5V$$

$$U_{OHMIN} = 4V \quad U_{ILMAX} = 1.4V$$

**ZADATAK 5.** (Z.MI. (2006/2007) grupa A)

$$U = 5V$$

$$f_1 = 100 \text{ MHz}$$

$$P = f C U^2$$

← samo ce  
uvrstiti u  
formulu!

$$f_2 = ?$$

$$P_1 = f_1 C U_1^2$$

$$P_2 = 1/1 P_1$$

(+10%.)

$$P_2 = f_2 C U_2^2$$

ZADATAK 4.  
UNOGAJ


Za neku polodicu logičkih sklopova poznato je sljedeće:  $U_{OHMIN} = 4V$ , stanje zan.

podnosi na ulaz rano:  $3.15V$ ,  $U_{IHMIN} = 2.5V$ ,

stanje zabranjeno podnosi na ulaz rano:  $1.4V$ , koje su granice



iskosmijeve smetnje tog sustava?
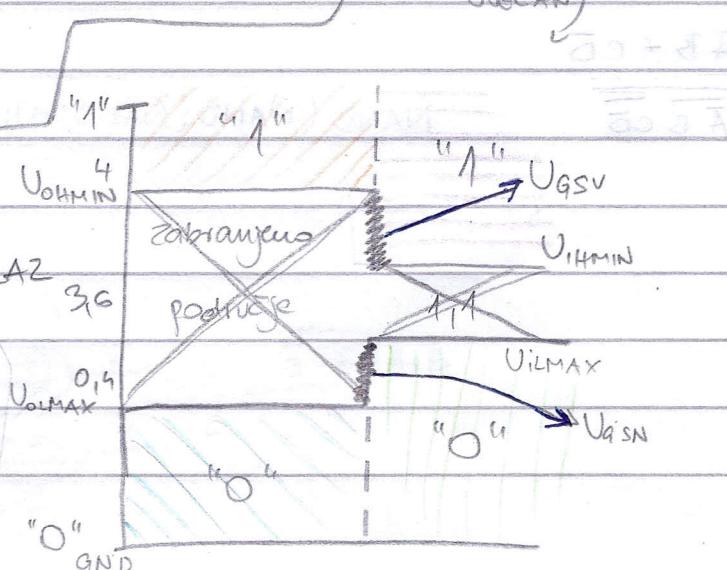
$$e) U_{GSV} = 1.5V, U_{GSN} = 1V, U_{as} = 1V$$



**CMOS** / pull up network

PUN → cito se komplement varijabli

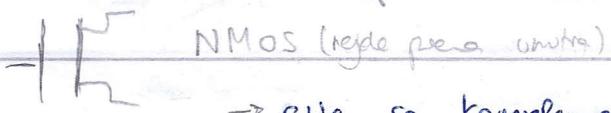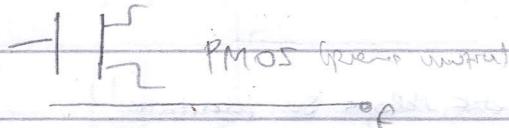

sejta -

paralela +

→ cito se komplement funkcije

PDN → pull down network

INVERTER


$$A \rightarrow \bar{A}$$

(isto je ako i dve A staviti)

A


Ucc

$$f = \bar{A}$$

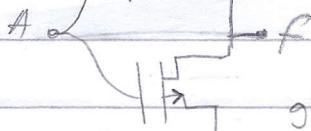


$$g = A$$

$$f = \bar{g} = \bar{A}$$

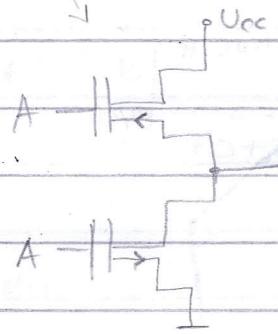

N1


$$A \cdot B = \bar{\bar{A}} + \bar{B}$$

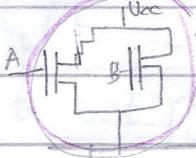

paralela

Ucc

$\bar{A} + \bar{B}$

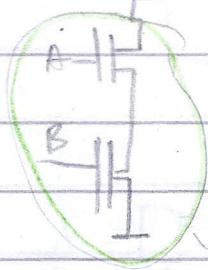


$$g = A \cdot B$$

$$f = \bar{g} = \bar{A} \cdot \bar{B}$$


sejta
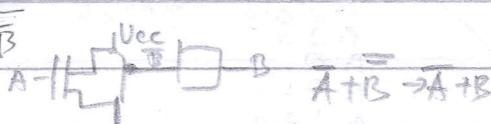
$$f = \bar{A} + B = \bar{A} \cdot \bar{B}$$



$$f = \bar{A} + B$$


$$\bar{A} + B = \bar{A} \cdot \bar{B}$$

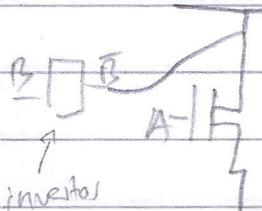

$$\bar{A} \cdot \bar{B}$$



inverzor

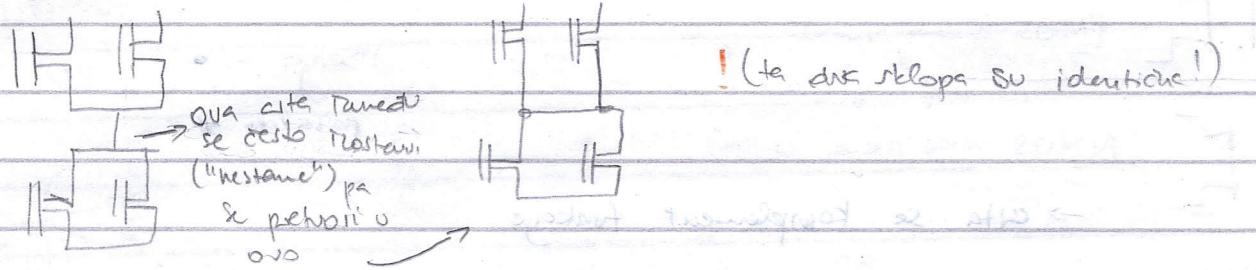ZADATAK → dateći ti je četiri odgovora kada nešta invertira na četiri (četiri) funkcije, ab im, odgovor odabrijući transponirati se ih u sebe.




→ broj tranzistora → zbroj vrijednosti pomnožen sa 2 (je li isti i ispred i dolje stane)

MULTIPLEXOR?

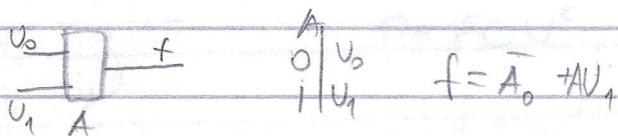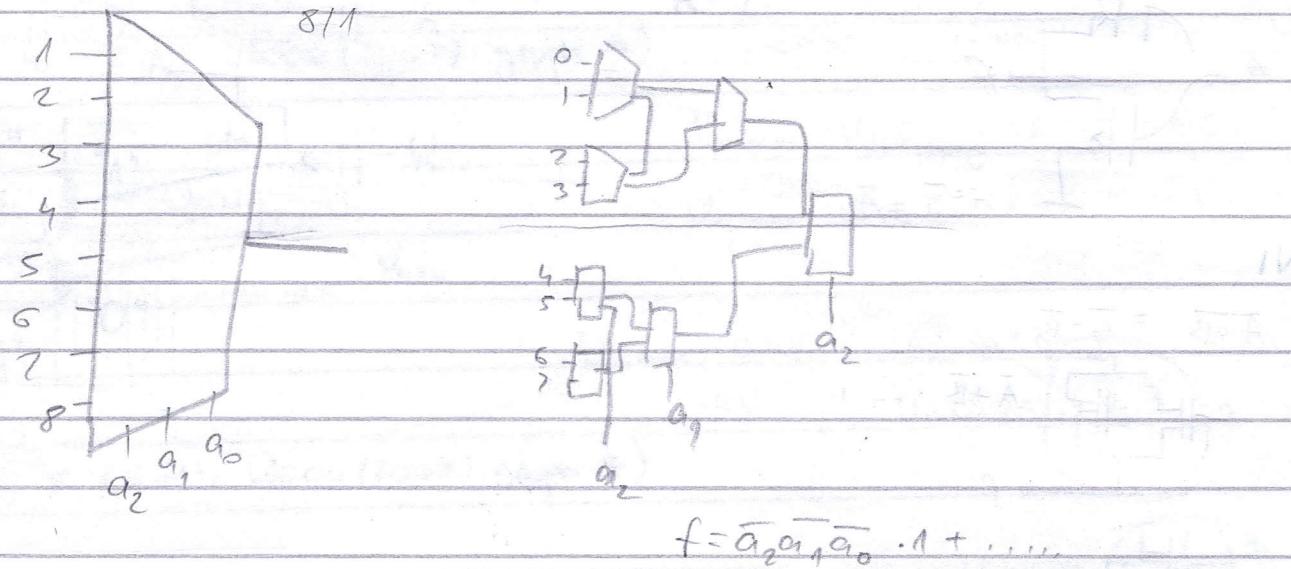


$$f = \bar{a}_2$$

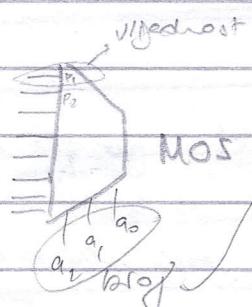


$a_2 \quad a_1 \quad a_0$
P0 0 0 0
P1 0 0 1
P2 0 1 0
P3 0 1 1
n4 1 0 0
P5 1 0 1
P6 1 1 0
P7 1 1 1

DFKODER

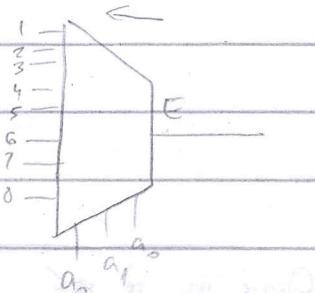

Reziproke Funktion

$$f(A, B, C)$$

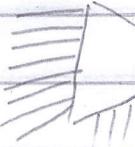


A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


ZAD.

$$F = \overline{B} (ACDG + \overline{CEP}) + \overline{B}(A\overline{C}D)$$


projektovací schéma

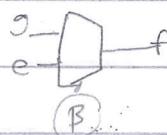

A	B	F
0	0	0
0	1	1

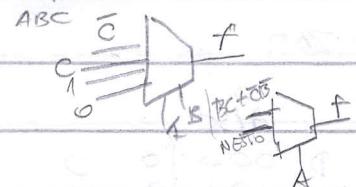

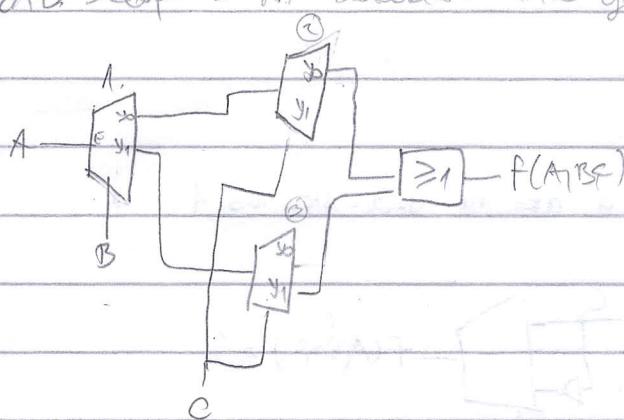ZAD Sklop = hi dekoder - kdežto ještě něco všechno máme



$$1. y_0 = A\overline{B}\overline{C}$$

$$y_1 = A\overline{B}C$$

$$3. y_0 = A\overline{B}C$$

$$y_1 = ABC$$


$$4. y_0 = A\overline{B}\overline{C}$$

$$y_1 = A\overline{B}C$$

$$f = A\overline{B}\overline{C} + ABC$$


$$f = A(\overline{B}\overline{C} + B\overline{C})$$

$$f = A \cdot \overline{B} \oplus C$$

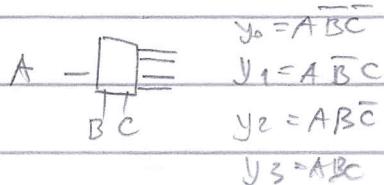

$$\begin{array}{c} 0 \quad \bar{C} \bar{B} \\ | \quad C \quad B \\ 1 \quad \bar{C} \quad \bar{B} \\ 2 \quad C \quad \bar{B} \\ 3 \quad C \quad B \end{array}$$

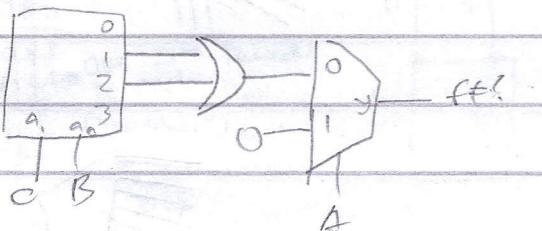
$$f = \bar{A}(\bar{C}B + C\bar{B}) + A(D)$$



Ovdje mi je vec  
malo popustio  
koncentraciju



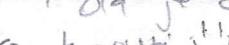nadam se da se  
pri ovo ostalo  
vidi i da je od  
nekak koristi



ZAD

ABC

D <sub>0</sub>	0 0 0	0	0
D <sub>1</sub>	0 1 0	1	1
D <sub>2</sub>	0 1 1	1	
D <sub>3</sub>	1 0 0	0	
	1 0 1	1	C
D <sub>4</sub>	1 1 0	1	
D <sub>5</sub>	1 1 1	0	C

ZAD

ako u istic i rezultat = 0, a ako ne onda stavimo 1

