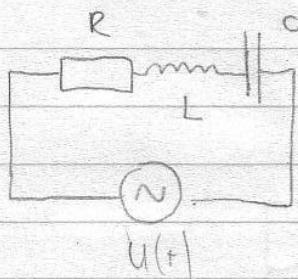


0

05

$$u(t) = U_m \sin(\underline{\omega t} + du) \rightarrow 2\pi f$$

$$U_{max} = \sqrt{2} |U_{ef}|$$




$$|| X_C = \frac{1}{\omega C} \quad 1 - 90^\circ \text{ kaski napon za } 90^\circ = -j \frac{1}{\omega L}$$

$$\text{mm } X_L = \omega L \quad 1 + 90^\circ \text{ prohodni struj za } 90^\circ = j\omega L$$

$$u = \dot{u} = U_{ef} / du \quad * /$$

$$= U_{ef} \cdot \cos du + j U_{ef} \cdot \sin du$$

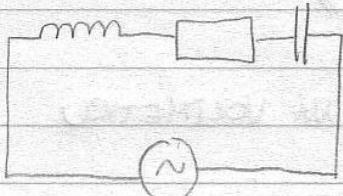$\underbrace{\hspace{1cm}}_{Re\{u\}} \quad \underbrace{\hspace{1cm}}_{Im\{u\}}$



$$R = 4 \Omega$$

$$X_L = 10 \Omega$$

$$U = 100V$$

$$X_C = 7 \Omega$$

$$Z_{uk} = R + X_L + X_C$$

$$\Rightarrow Z_{uk} = 4 + j10 - j7 =$$

$$= R + jX_L - jX_C$$

$$= 4 + j3 \Omega$$

$$= Z_{uk} \lfloor p$$

$$= \sqrt{4^2 + 3^2} \quad \lfloor \arctg \frac{3}{4}$$

$$= 5 \lfloor 36,87 \Omega$$

$$I = I \angle 0^\circ$$

$$I \angle 0^\circ = \frac{U}{Z} = \frac{100 \angle 0^\circ}{5 \angle 36,87^\circ}$$

$$\star \frac{5 \angle 30^\circ}{10 \angle 45^\circ} = 0.5 \angle -15^\circ$$

$$I = \frac{100}{5} = 20 \text{ A}$$


$$0^\circ = \underline{\Delta u} - 36,87^\circ$$

$$\underline{\Delta u} = 36,87^\circ$$

$$U_R = I \cdot R$$

$$= 20 \angle 0^\circ \cdot 4 \angle 0^\circ$$


$$= 80 \angle 0^\circ //$$

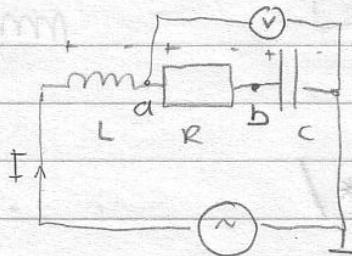

$$U_L = I \cdot X_L = 20 \angle 0^\circ \cdot 10 \angle 90^\circ = 200 \angle 90^\circ //$$

$$U_C = I \cdot X_C = 20 \angle 0^\circ \cdot 7 \angle -90^\circ = 140 \angle -90^\circ //$$

NAPON NA VOLTMETRU


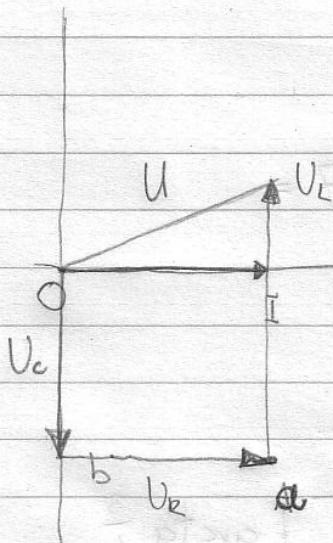


$$U_V = U_R + U_C =$$

$$= 80 \angle 0^\circ + 140 \angle -90^\circ$$

$$= 80 - j 140$$


$$U_V = \sqrt{80^2 + 140^2} =$$

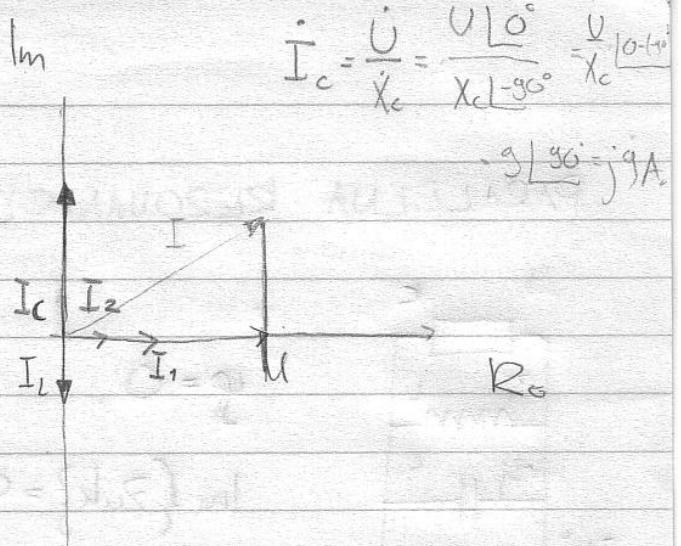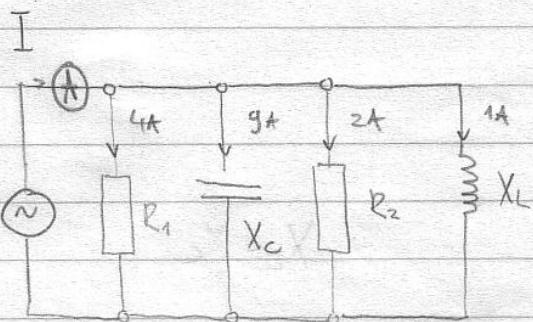

STRUJA KROZ OTPORNIK
JE U FAZI S
NAPONOM

$$I = 4 + j \cdot 2 - j = 6 + 8j = 10 / 53^\circ$$

$$I = \sqrt{6^2 + 8^2} = 10 A,$$

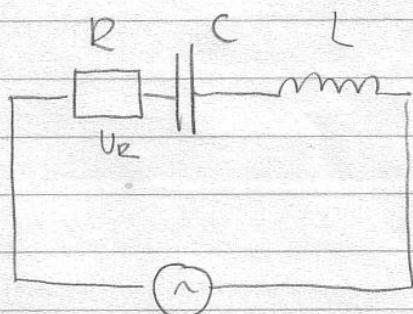

$$Y = 0$$

$$X_C = X_L$$

$$\operatorname{Im}\{Z_{\text{uk}}\} = 0$$


$$\frac{1}{\omega C} = \omega L$$

$$\omega = \frac{1}{\sqrt{LC}}$$


$$Z_{\text{uk}} = R$$

$$I = I | 0^\circ$$
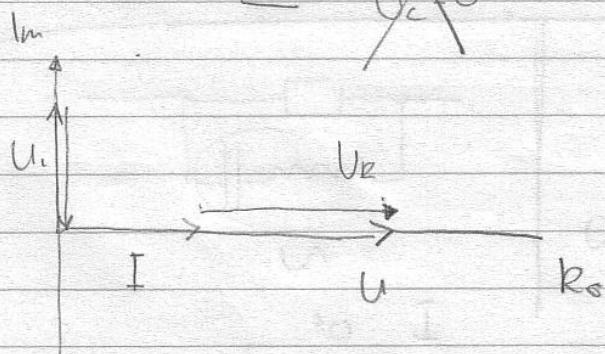
$$\begin{aligned} U_R &= 0 \\ U_C &= 0 \end{aligned}$$



PARALELNA REZONANCIJA

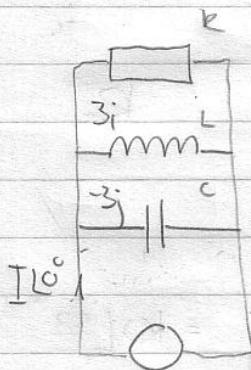

$$\varphi = 0$$

$$X_L = X_C$$

$$\operatorname{Im}\{Z_{uk}\} = 0$$



$$\frac{1}{Z_{uk}} = \frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C}$$

~~$$I_L = 0$$~~



~~$$I_C = 0$$~~

$$Z_{uk} = R$$
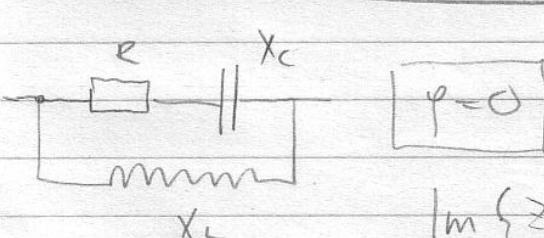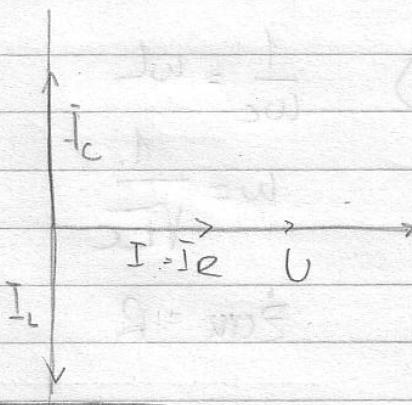
$$Z_{LC} = \frac{X_L \cdot X_C}{X_L + X_C} = \frac{3j(-3j)}{3j - 3j} = \infty$$



$$\operatorname{Im}\{Z_{uk}\} = 0$$

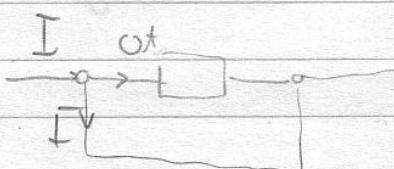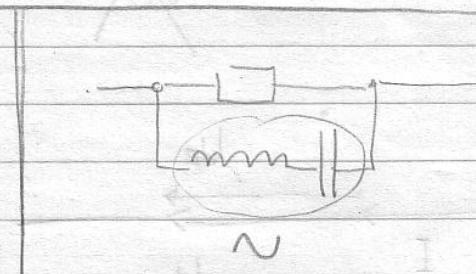

VUT IMPEDANCJE

Samo je jedan

$$\dot{S} = \dot{U} \cdot (\dot{I})^* = U \cdot I | \varphi \quad \text{VA}$$

→ Vektorska
(prirodna)
snaga

$$= U \cdot I \cdot \cos \varphi + j \cdot U \cdot I \cdot \sin \varphi$$

P

j Q

$Q > 0$ ind.

Mali živac

[W]

radna
snaga


[VA_r]

jabaci
snag

$Q < 0$ kap

$$Z_i = R + jX$$

$$-3-j4$$

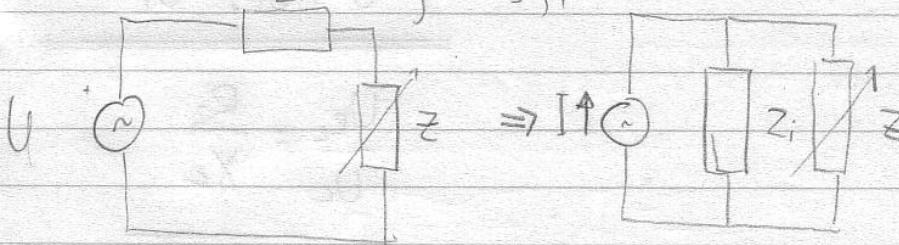


$$\begin{aligned} &\text{za max snagu} \\ &\text{naj } Z = \\ &Z = (Z_i)^* = 3+j4 \end{aligned}$$

$Z \rightarrow$ radni otpor (R)


P Q

P, S, cos φ

$$R = |Z_i| = \sqrt{(Re)^2 + (Im)^2}$$

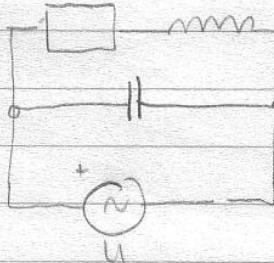


$$C = ? \Rightarrow \cos \varphi$$

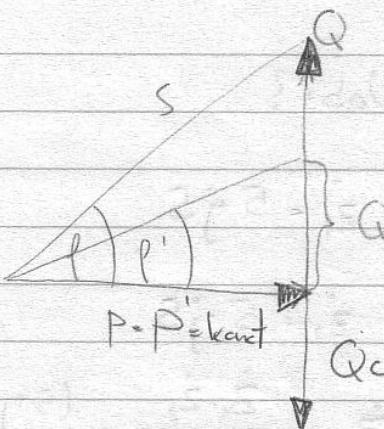

$$= \sqrt{3^2 + 4^2} = 5 \Omega$$

za kompenzaciju jačine


SNAGE KONDENZATOR IDE
PARALELNO

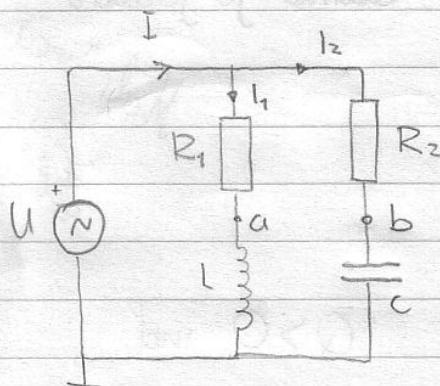

$$U_{ab} = ?$$

$I_1 \rightarrow RL$ (nalazi se izmedu 0° i 90°)

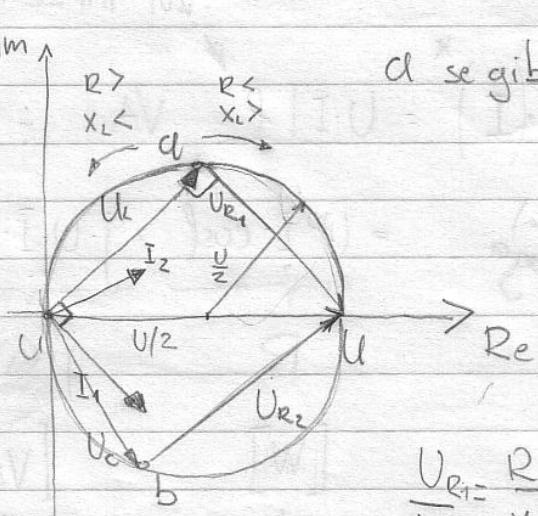I na $R \rightarrow 0^\circ$
 na $L \rightarrow -90^\circ$
 na $C \rightarrow 90^\circ$




$$\frac{U_{R_1}}{U_L} = \frac{R \cdot I_1}{X_L \cdot I_1} = \frac{R}{X_L}$$

$$U = \sqrt{U_{R_1}^2 + U_L^2}$$

$$\frac{U_{R_2}}{U_C} = \frac{R_2}{X_C}$$

$$U = \sqrt{U_{R_2}^2 + U_C^2}$$

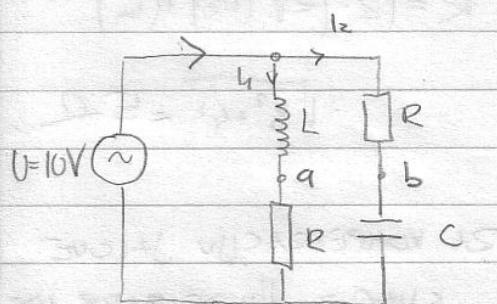


$$R = X_L = X_C = 5 \Omega$$

$$U_{ab} = ?$$

$$z_1 = 5 + j5$$




$$z_2 = 5 - j5$$
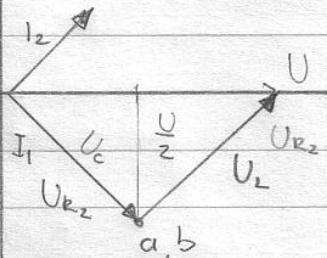
$$\frac{\dot{z}_w}{\dot{z}_w} \cdot \frac{\dot{z}_1 \cdot \dot{z}_2}{\dot{z}_1 + \dot{z}_2} = \frac{(5+j5)(5-j5)}{5+j5+5-j5} = 5 \Omega$$



$$U_{ab} = U_{R_2} - U_L$$

$$= -U_C + U_{R_1}$$

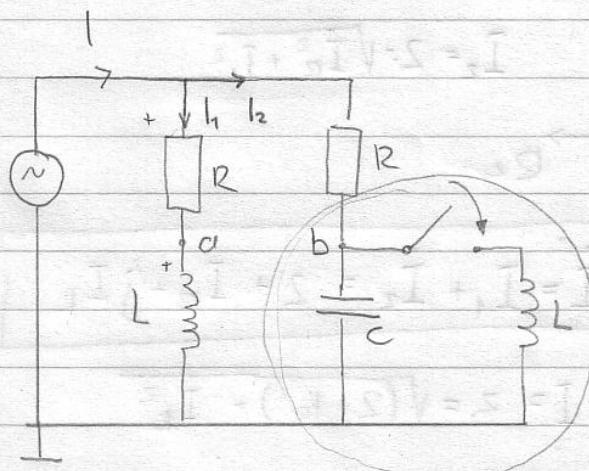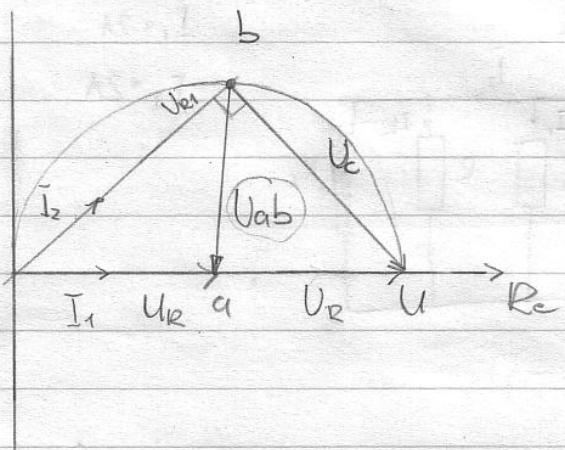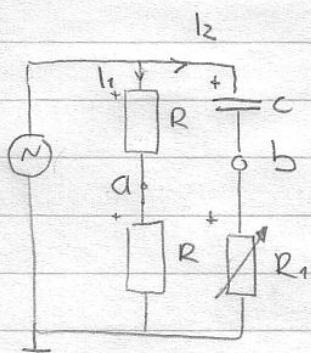


$$R = X_L = X_C = 10 \Omega$$

$U_{ab} = ?$ (kako se promjeni kad se sklopka zatvori)

$$I_1 = -45^\circ \Rightarrow \text{jer su } R : X_C \text{ jednaki}$$

$$Z_{X_C} = \infty$$
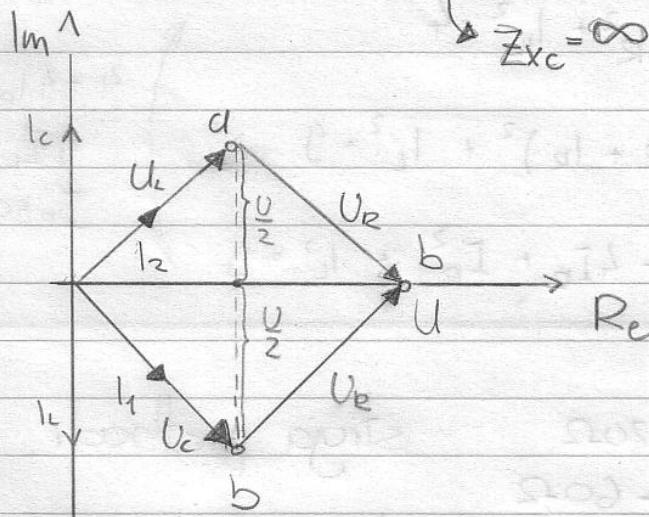
$$I_2 = 45^\circ \Rightarrow \text{jer su } R : X_C \text{ jednaki}$$




$$U_{ab} = U$$

$$U_{ab} = \frac{U}{\sqrt{2}}$$

$$I_C = \frac{U}{X_L} = 10A$$

na $L C \Rightarrow U$

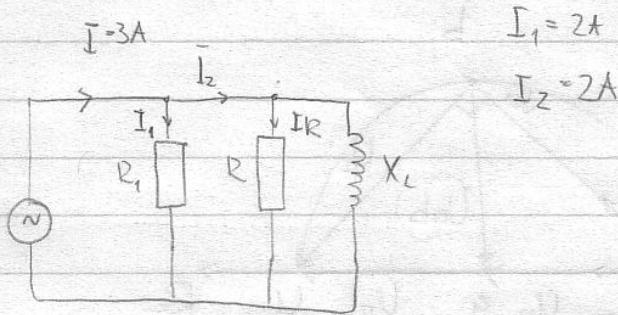


$$I_1 = 2A$$

$$I_R = 2A$$

$|m_A|$

$$\dot{I}_2 = \dot{I}_R - j \dot{I}_L$$

$$I_2 = \sqrt{I_R^2 + I_L^2}$$

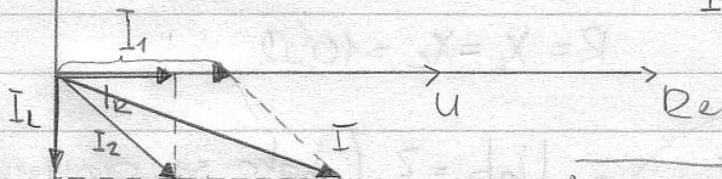

$$\boxed{\dot{I} = \dot{I}_1 + \dot{I}_2 = 2 + I_R - j I_L}$$


$$I = 3 = \sqrt{(2 + I_R)^2 + I_L^2}$$

$$I_R^2 + I_L^2 = 4$$

$$(2 + I_R)^2 + I_L^2 = 9$$

$$4 + 4I_R + I_R^2 + I_L^2 = 9$$
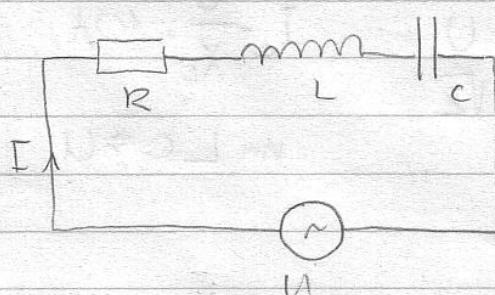
$$\left. \begin{aligned} 4 + 4I_R &= 9 - 4 \\ 4I_R &= 1 \\ I_R &= 0.25A \end{aligned} \right\}$$



$$X_L = 20\Omega$$

$$X_C = 60\Omega$$

struja prethodni

ukupnom naponu za

30°


$$\dot{I} = I_1 \angle \varphi_1$$

$$\dot{U} = U_1 \angle \varphi_1$$

$$\varphi_1 = 30^\circ + \varphi_u$$

$$\dot{Z} = \frac{\dot{U}}{\dot{I}} = \frac{U_1 \angle \varphi_1}{I_1 \angle 30^\circ + \varphi_u} = Z \angle -30^\circ$$
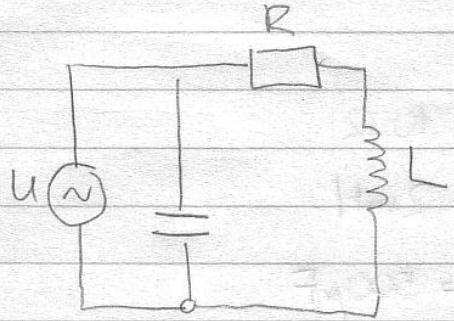
$$\dot{Z} = R + jX_L - jX_C = R - j40 \Rightarrow \rho = \arctg \frac{-40}{R} \quad 8.$$



$$R = 30 \Omega$$

$$L = 2 \text{ mH}$$

$$C = 45 \mu\text{F}$$

$$\rho = ?$$

(U, I u Faz)

RESONANZ

$$\rho = 0$$

$$\operatorname{Im}\{Z_{uk}\} = 0$$


$$Q = 0$$

$$Z_{uk} = RL \parallel C = \frac{(R + jX_L)(-jX_C)}{R + jX_L - jX_C} = \frac{X_L X_C - jR X_C}{R + j(X_L - X_C)} \cdot \frac{R - j(X_L - X_C)}{R - j(X_L - X_C)}$$

$$= \frac{R X_L X_C - R X_C (X_L - X_C)}{R^2 + (X_L - X_C)^2} - j \frac{R^2 X_C + X_L X_C (X_L - X_C)}{R^2 + (X_L - X_C)^2} = 0$$

$$R^2 X_C + X_L X_C (X_L - X_C) = 0 \quad | : X_C$$
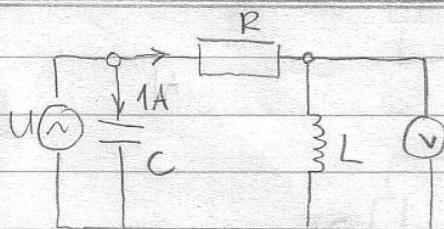
$$30^2 + \omega L \left(\omega L - \frac{1}{\omega C} \right) = 0$$



$$I_c = 1 \text{ A}$$

$$\operatorname{Im}\{Z_{uk}\} = 0$$


$$U_V = 6 \text{ V}$$

$$R^2 + X_L (X_L - X_C) = 0$$

$$U = 10 \text{ V}$$

$$X_L = ?$$


$$X_C = \frac{U}{I_c} = 10 \Omega$$

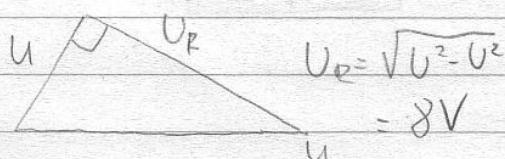

$$U_R = \sqrt{U^2 - U_C^2}$$

$$U_R = 8 \text{ V}$$

$$\frac{U_R}{U_L} = \frac{|I_C| \cdot R}{|I_C| \cdot X_L} = \frac{R}{X_L} = \frac{8}{6}$$

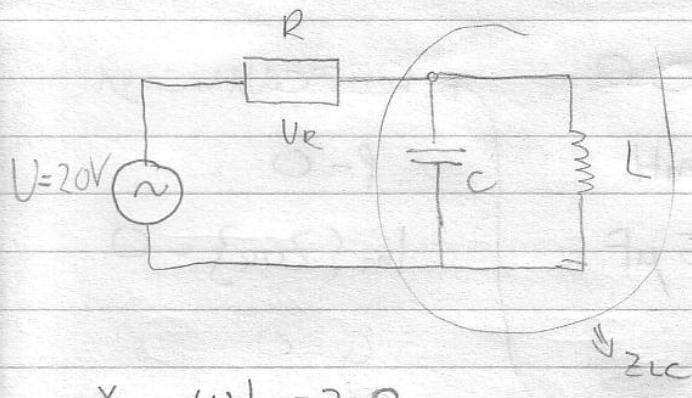

$$R = 10 \Omega$$

$$L = 2 \text{ mH}$$

$$C = 500 \mu\text{F}$$

$$\omega = 1000 \text{ rad/s}$$

$$X_L = \omega L = 2 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{10^3 \cdot 0,5 \cdot 10^{-3}} = 2 \Omega$$

$$Z_{LC} = \frac{j X_L (-X_C)}{j X_L - j X_C} = \infty$$

$$Z_{\text{th}} = R + Z_{LC} = \infty \Omega$$

$$I_{UK} = 0$$

$$U_R = 0V$$

$$I_L = \frac{\dot{U}_{LC}}{j X_L} = \frac{20}{j 2} = -j 10A$$

$$\dot{U}_{RC} = 20$$

$$I_R = \frac{\dot{U}_{LC}}{-j X_C} = j 10A$$



$$U(t) = 10 \sin(\omega t + \frac{\pi}{4})$$

$$i(t) = 2 \cos(\omega t)$$

$$i_2(t) \quad z_2 = 20 \angle 30^\circ$$

$$\dot{U} = \frac{10}{\sqrt{2}} \angle 45^\circ$$
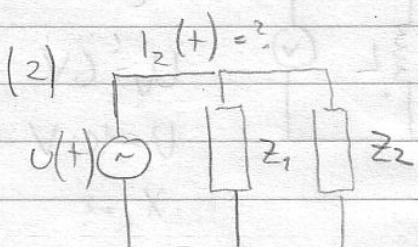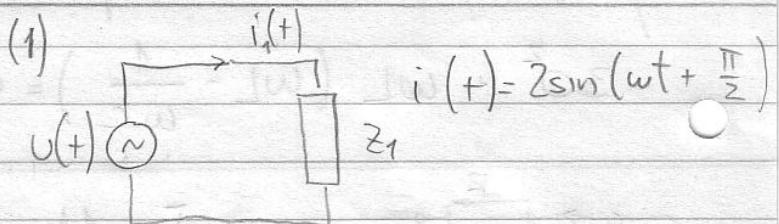
$$\dot{I} = \frac{2}{\sqrt{2}} \angle 90^\circ$$




$$\dot{Z} = \frac{\dot{U}}{\dot{I}} = \frac{\frac{10}{\sqrt{2}} \angle 45^\circ}{\frac{2}{\sqrt{2}} \angle 90^\circ} = 5 \angle -45^\circ$$

$$\dot{Z}_{UK} = \frac{\dot{Z}_1 \cdot \dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} = \frac{100 \angle -15^\circ}{3,53 - j 3,53 + j 17,32 + j 10} = \frac{100 \angle -15^\circ}{21 + j 6,5} = \frac{100 \angle -15^\circ}{22 \angle 17^\circ} = 45 \angle -32^\circ$$

$$I_2 = \frac{U}{Z_{lk}} = \frac{\frac{10}{\sqrt{2}} \angle 45^\circ}{\frac{4\sqrt{2}}{1} \angle -32^\circ} = 1.57 \angle 77^\circ$$

$$i_2(t) = 1.57\sqrt{2} \sin(\omega t + 77^\circ)$$

RADIJANI!

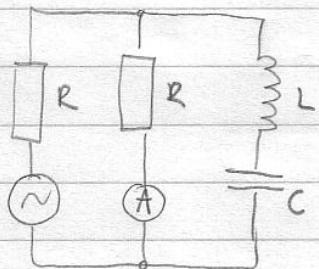

$$U(t) = 10\sqrt{2} \sin(314t) \text{ V}$$

$$R = 100 \Omega$$


$$X_L = 10 \Omega$$

$$C = ?$$

$$X_L = X_C$$

$$I_A = 0 \quad X_C = 10 \Omega$$

$$\frac{1}{\omega C} = 10$$

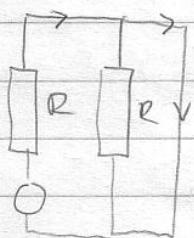


$$Z_{eq} = R$$

$$I_{lk} = \frac{10}{100} = 0.1 \text{ A}$$

$$U_C = I X_C = 1 \text{ V}$$

TYWIA
ZK
PREOSPEWNIKT!

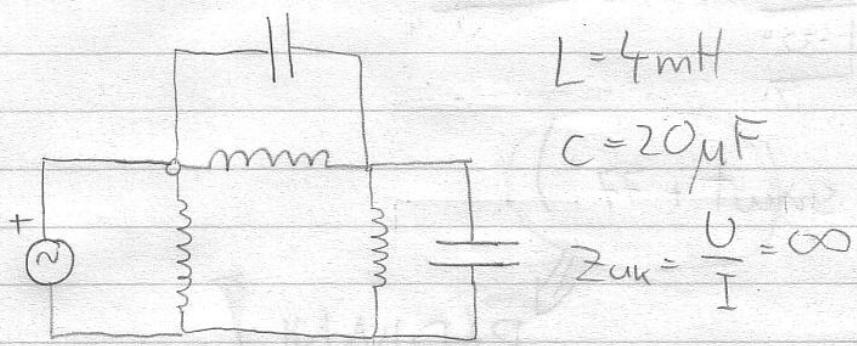


$$f = ?$$

$$\boxed{I = 0}$$

$$Y_{\text{uk}} = 0 \quad G = \frac{1}{R}$$
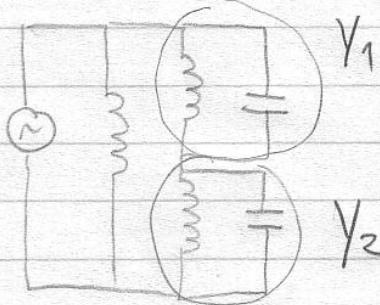
$$X_C = \frac{-j}{\omega C} = \frac{1}{B_C}$$



$$\underline{B_C = j\omega C}$$

$$\underline{X_L = j\omega L = \frac{1}{B_L}}$$

$$B_L = \frac{-j}{\omega L}$$

$$\dot{Y}_1 = B_C + B_L = j(B_C - B_L)$$

$$\dot{Y}_2 = \dot{Y}_1$$


$$\dot{Y}_{12} = \frac{\dot{Y}_1 \cdot \dot{Y}_2}{\dot{Y}_1 + \dot{Y}_2} = \frac{j(B_C - B_L) \cdot j(B_C - B_L)}{2 \cdot j(B_C - B_L)} = j \frac{B_C - B_L}{2}$$

$$\dot{Y}_{\text{uk}} = \dot{Y}_{12} + B_L =$$


$$= j \frac{B_C}{2} - j \frac{B_L}{2} - j \frac{B_L}{2}$$

$$B_C = 3 B_L$$

$$\omega C = \frac{3}{\omega L}$$

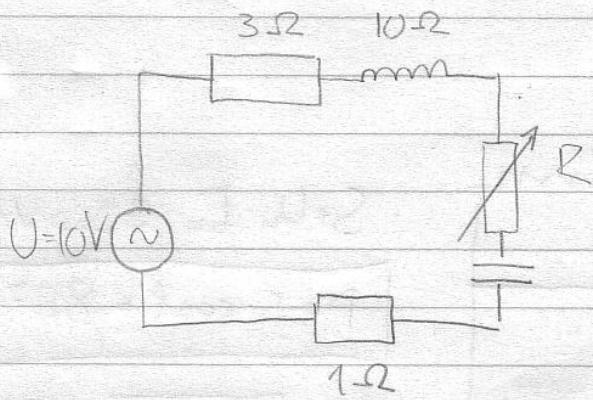

P_{MAX} na $R = ?$

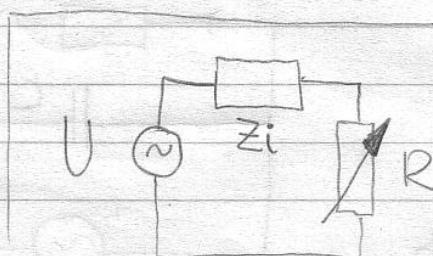

$$Z_i = 3 + j10 - j7 + 1$$

$$= 4 + j3$$

$$R = |Z_i| = \sqrt{4^2 + 3^2} = 5\Omega$$

$$P = U_R \cdot I$$

$$= I \cdot R \cdot I = I^2 R$$

$$= \frac{100}{90} \cdot \sqrt{50} W$$

$$Z_{uk} = Z_i + R$$

$$= 4 + j3 + 5$$

$$= 9 + j3$$

2. slučaj: sve isto; umjesto $\square R$ je Z

$$Z_{uk} = \sqrt{9^2 + 3^2} = \sqrt{90}$$

$$Z = Z_i^* = 4 - j3 \Omega$$

$$I = \frac{U}{Z_{uk}} = \frac{10}{8}$$

$$I = \frac{U}{Z} = \frac{10}{\sqrt{90}}$$

$$Z_{uk} = Z + Z_i$$

$$= 8 \Omega$$

$$P_z = I^2 \cdot \operatorname{Re}\{Z\} = \frac{100}{64} \cdot 4 W$$

$$Q = I^2 \cdot \operatorname{Im}\{Z\} = \frac{100}{64} \cdot (-3) \text{ VAR}$$

$$\dot{S} = P + jQ$$


$$S_z = \sqrt{P_z^2 + Q_z^2}$$

$$U_i = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$I_h = 4,5 \text{ A}$$

$$\cos \varphi = 0,866$$

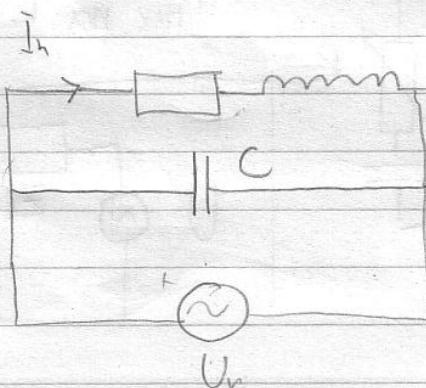

$$S = U_h \cdot I_h = 990 \text{ VA}$$

$$P = S \cdot \cos \varphi = 857 \text{ W}$$


$$Q = \sqrt{S^2 - P^2} = 496 \text{ VAr}$$

sa C

$$P = S' \cdot \cos \varphi \Rightarrow S' = 902 \text{ VA}$$

$$Q' = \sqrt{S'^2 - P^2}$$

$$= 281 \text{ VAr}$$

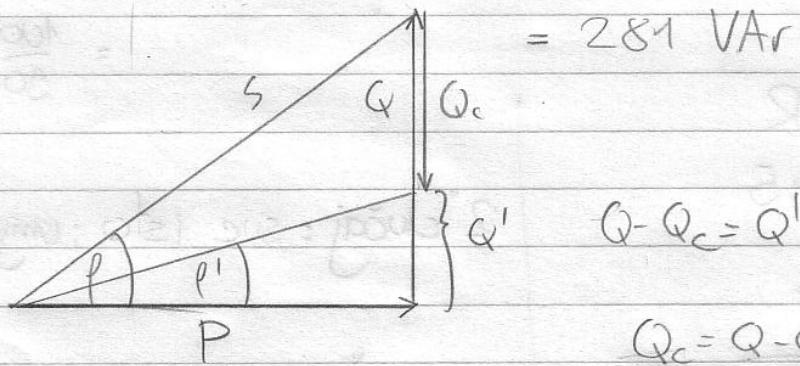

$$Q_c = Q - Q'$$

$$= 215 \text{ VAr}$$

$$\cos \varphi = \frac{P}{S} = \frac{P}{\sqrt{P^2 + Q^2}}$$

$$\cos \varphi \rightarrow \square \parallel$$

$$= U \cdot I_c = \frac{U_n^2}{X_C}$$

$$\frac{1}{w_C} = X_C = \frac{U_n^2}{Q_c}$$



$$\cos \varphi = 0,5$$

$$U_c = U_k$$

$$\cos \varphi = \frac{P}{\sqrt{P^2 + Q^2}}$$

$$S = U(i)^* = U \cdot I \cdot L \varphi$$

$$= \frac{U^2}{Z} \cos \varphi + j \frac{U^2}{Z} \sin \varphi$$

14.

ZADATAK SA
PROŠLOG GODIŠNJE
MEĐUISPIT


II. NAČIN ZA RJEŠAVANJE (prefvaranje paralele u seriju)

$$Z_{uk} = \frac{-jR X_c}{R - jX_c} = \frac{R X_c^2 - j R^2 X_c}{R^2 + X_c^2}$$

$$= \left(\frac{R X_c^2}{R^2 + X_c^2} \right) - j \left(\frac{R^2 X_c}{R^2 + X_c^2} \right)$$

$\downarrow \quad \downarrow$


$R' \quad X'_c$

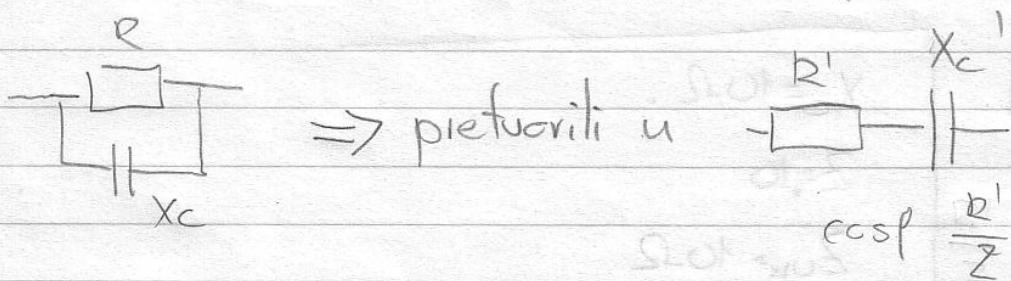

$$\phi = 60^\circ$$

$$\tan \phi = \frac{X'_c}{R'} = \frac{R^2 X_c}{R X_c^2} = \frac{R}{X_c}$$
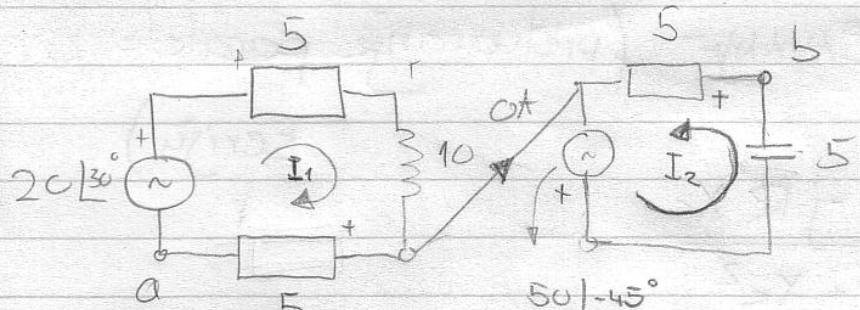
$$\tan \phi' = \frac{X_c}{R} \Rightarrow \phi' \\ \Rightarrow \cos \phi'$$




$$U_{ab} = -5 \cdot \dot{I}_2 - 5 \cdot \dot{I}_1$$

$$U_{ab} = |-5 \dot{I}_2 - 5 \dot{I}_1|$$

$$U_{ab} = ?$$

VII 1-14

$$I = 10 \text{ A}$$

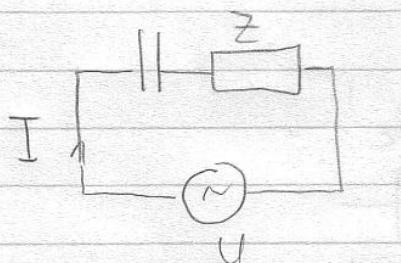

$$U_c = U_2 = U = 100 \text{ V}$$

$$X_c = 10 \Omega$$

$$Z = 10$$


$$Z_{\text{unk}} = 10 \Omega$$

$$Z = R + jX$$

$$Z_{\text{unk}} = R + jX - jX_c$$

$$Z = 10 = \sqrt{R^2 + X^2}$$
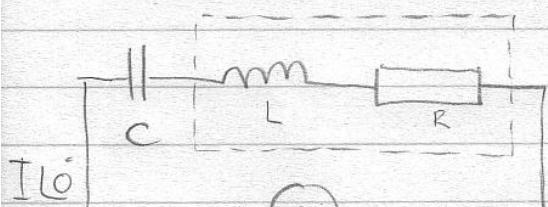
$$Z_{\text{unk}} = 10 = \sqrt{R^2 + (X-10)^2}$$



$$U = 120 \text{ V}$$

$$U = U_R + jU_L - jU_C$$

$$= U_R$$


$$U_C = 160 \text{ V}$$


$$X_L = X_C$$

$$U_R = 120 \text{ V}$$

$$U_L = U_C = 160$$

$$U_{\text{sr}} = \sqrt{U_R^2 + U_L^2}$$

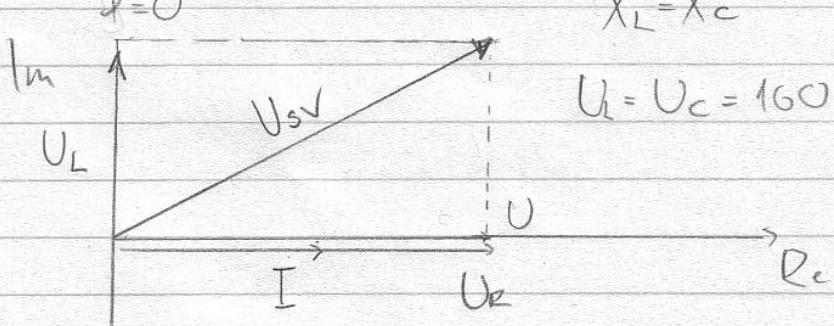

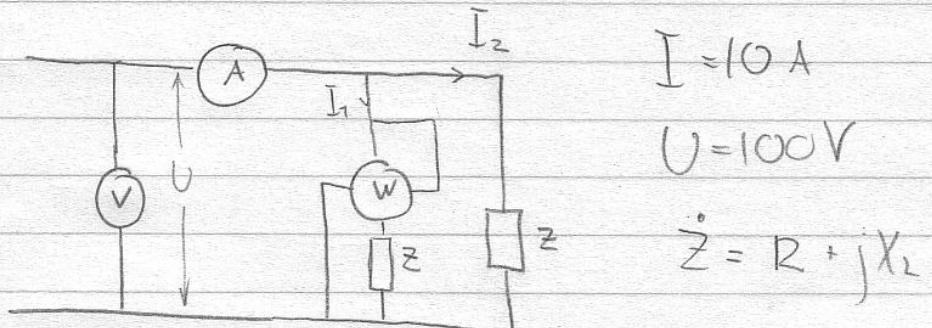

$$I = 10 \text{ A}$$

$$U = 100 \text{ V}$$

$$\dot{Z} = R + jX_L$$

$$R = \frac{1}{4} Z$$

$$I_1 = 5 \text{ A}$$


$$P = U \cdot I_1 \cdot \cos \varphi$$

$$Z_{\text{uk}} = \frac{Z}{2} = 10 \Omega$$

$$Z = 20 \Omega$$

$$R = 5 \Omega$$

$$X = \sqrt{Z^2 - R^2}$$

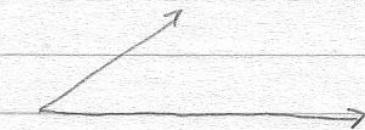

$$P = I_1^2 \cdot R = 125 \text{ W}$$