
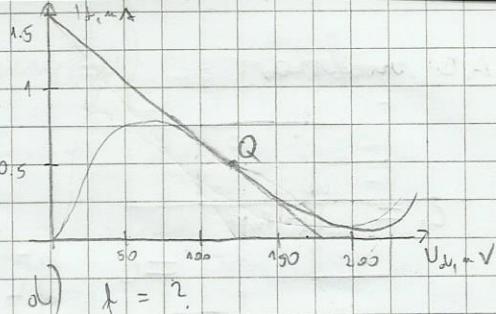


Zadání:

$$I_{dL} = 0.5 \text{ mA}$$

$$U_{dL} = 120 \text{ mV}$$

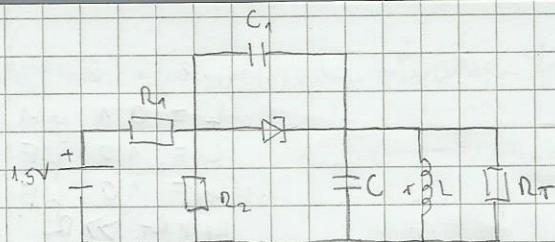

- a) $r_{ab} = ?$ b) jehozaříka proudu c) $f_{qj} = ?$ d) $\beta = ?$


$$\begin{aligned} T_1(0, 1.5) \\ T_2(120, 0.5) \end{aligned}$$

$$y - 1.5 = \frac{0.5 - 1.5}{120 - 0} (x - 0)$$

$$y - 1.5 = -\frac{1}{120} x \quad \frac{x = U}{y = I} \Rightarrow I = -\frac{1}{120} U + 1.5 \text{ [mA]}$$

$$g_d = -\frac{1}{120} \Rightarrow \underline{\underline{r_{ab} = -120 \Omega}}$$

D'C analýza: $(Z_L = 0, Z_C = \infty)$

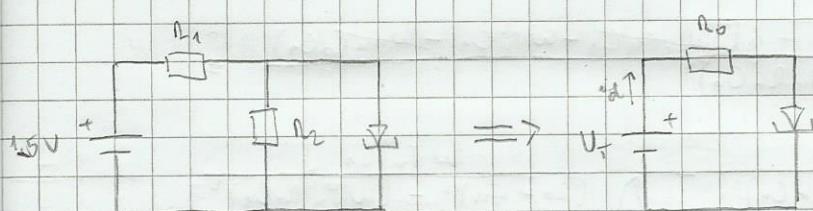

$$U_T = 1.5 \cdot \frac{R_2}{R_1 + R_2}$$

$$R_o = R_1 \parallel R_2$$

$$U_T = i_{dL} \cdot R_o + U_d$$

* v pravém re obvodu užíváme: $R_o = \frac{1}{g_d} |I_{dL}|$

$$R_o = 40 \Omega$$

$$1.5 \cdot \frac{R_2}{R_1 + R_2} = 40 \cdot i_{dL} + U_d \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{40 i_{dL} + U_d}{1.5}$$

$$\frac{R_1 R_2}{R_1 + R_2} = 40 \Rightarrow R_1 = 40 \cdot \frac{R_1 + R_2}{R_2}$$


$$\frac{R_2}{R_1 + R_2} = \frac{40 \cdot 0.5 \cdot 10^{-3} + 120 \cdot 10^{-3}}{1.5} = \frac{7}{45}$$

$$R_1 = \frac{40}{\frac{7}{45}} = \frac{3000}{7} = 428.57 \Omega$$

$$7.5 R_1 = 7 R_1 + 7 R_2$$

$$6.8 R_2 = 7 R_1 \Rightarrow R_2 = \frac{7}{68} R_1 = \frac{750}{17} = 44.12 \Omega$$

AC analýza:

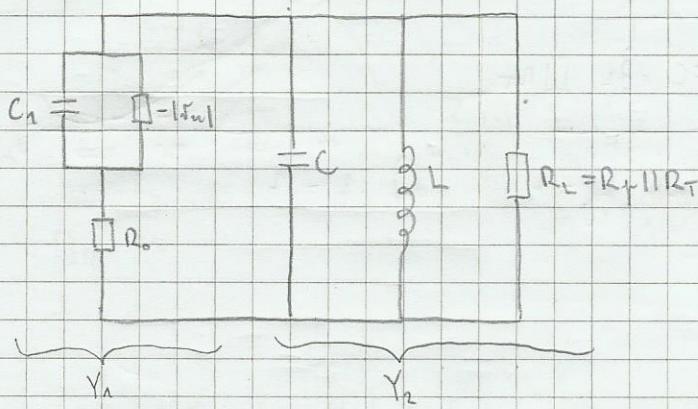

$$\begin{aligned}
 L &= 0.1 \mu H = 10^{-3} H \\
 C &= 10 \mu F = 10^{-11} F \\
 C_1 &= 10 \mu F = 10^{-11} F \\
 R_o \parallel R_L &\Rightarrow R_o, R_L \gg R_o \\
 \omega &= 120 \text{ rad/s} \\
 R_o &= 40 \Omega
 \end{aligned}$$

$$Z_1 = R_o + \omega \parallel \frac{1}{j\omega C_1} = R_o + \frac{\frac{j\omega}{2C_1}}{\omega + \frac{1}{j\omega C_1}} = R_o + \frac{j\omega}{1 + j\omega C_1}$$

$$Y_1 = \frac{1}{R_o + \frac{j\omega}{1 + j\omega C_1}} = \frac{1 + j\omega C_1}{R_o + j\omega R_o C_1 + j\omega} = \frac{1 + j\omega R_o C_1}{(R_o + j\omega) + j\omega R_o C_1}$$

$$\begin{aligned}
 \omega &= j\omega \Rightarrow Y_1 = \frac{1 + j\omega R_o C_1}{(R_o + j\omega) + j\omega R_o C_1} \cdot \frac{(R_o + j\omega) - j\omega R_o C_1}{(R_o + j\omega) - j\omega R_o C_1} = \\
 &= \frac{R_o + j\omega + \omega^2 R_o^2 C_1^2 R_o}{(R_o + j\omega)^2 + (\omega R_o R_o C_1)^2} + j \frac{\omega R_o^2 C_1}{(R_o + j\omega)^2 + (\omega R_o R_o C_1)^2}
 \end{aligned}$$

$$Y_2 = j\omega C + \frac{1}{R_L} + \frac{1}{j\omega L} \stackrel{\omega = j\omega}{=} Y_2 = j\omega C + \frac{1}{R_L} - j\frac{1}{\omega L}$$

$$Y_2 = \frac{1}{R_L} + j \left(\omega C - \frac{1}{\omega L} \right)$$

$$Y_{wh} = Y_1 + Y_2$$

$$w^2 = \frac{R_o + j\omega + \omega^2 R_o^2 R_o C_1^2}{(R_o + j\omega)^2 + (\omega R_o R_o C_1)^2} + \frac{1}{R_L} + j \left[\frac{\omega R_o^2 C_1}{(R_o + j\omega)^2 + (\omega R_o R_o C_1)^2} + \omega C - \frac{1}{\omega L} \right]$$

$$\operatorname{Re}\{Y_{wh}\} = 0 \quad (\text{výrobek nemopolovin; na pramalovate gravitacne fyzik.})$$

$$(R_o + j\omega) R_L + \omega^2 R_o^2 R_L C_1^2 + (R_o + j\omega)^2 + (\omega R_o R_o C_1)^2 = 0$$

$$w^2 = \frac{-(R_o + j\omega)^2 - (R_o + j\omega) R_L}{R_o^2 R_L C_1^2 + R_o^2 R_L C_1^2} = - \frac{(R_o + j\omega)(R_L + R_o + j\omega)}{R_o^2 C_1^2 R_L (R_L + R_o)}$$

$$w = \frac{1}{\omega C_1} \sqrt{\frac{(R_o + j\omega)(R_L + R_o + j\omega)}{-R_o(R_L + R_o)}} \approx \frac{1}{\omega C_1} \sqrt{\frac{(R_o + j\omega) \cdot R_L}{-R_o \cdot R_L}} = \frac{1}{\omega C_1} \sqrt{\frac{R_o + j\omega}{-R_o}}$$

$$w_g = \frac{1}{120 \cdot 10^{-11}} \cdot \sqrt{\frac{40 - 120}{-40}} = 1.1785 \cdot 10^9 \Rightarrow f_g = \frac{w}{2\pi}$$

$$f_g = 187.56 \text{ MHz}$$

$\Im m \{ Y_{\text{inh}} \} = 0$ (zu gewählten Strome freienweg)

$$\frac{\omega \sqrt{n^2 C_1}}{(R_o + \sqrt{n})^2 + (\omega \sqrt{n} R_o C_1)^2} = \frac{1 - \omega^2 L C}{WL}$$

$$\omega^2 \sqrt{n^2 L C_1} = [(R_o + \sqrt{n})^2 + \omega^2 \sqrt{n} R_o^2 C_1^2] (1 - \omega^2 L C)$$

$$*\omega^2 = \frac{1}{\sqrt{n^2 C_1}} \frac{R_o + \sqrt{n}}{-R_o} \cdot R_o^2 \sqrt{n} C_1^2$$

$$\omega^2 \sqrt{n} R_o^2 C_1^2 = -R_o (R_o + \sqrt{n})$$

$$\omega^2 \sqrt{n^2 L C_1} + [\omega^2 L C - 1] [(R_o + \sqrt{n})^2 - R_o (R_o + \sqrt{n})] = 0$$

$$\omega^2 \sqrt{n^2 L C_1} + (\omega^2 L C - 1) (R_o + \sqrt{n}) (R_o + \sqrt{n} - R_o) = 0$$

$$\omega^2 \sqrt{n^2 L C_1} + (\omega^2 L C - 1) (R_o \sqrt{n} + \sqrt{n}) = 0$$

$$\omega^2 \sqrt{n^2 L C_1} + \omega^2 R_o \sqrt{n} L C + \omega^2 \sqrt{n^2 L C} - R_o \sqrt{n} - \sqrt{n} = 0$$


$$\omega^2 = \frac{\sqrt{n} (R_o + \sqrt{n})}{\sqrt{n^2 L C_1} + \sqrt{n} L C (R_o + \sqrt{n})} = \frac{R_o + \sqrt{n}}{\sqrt{n} L C_1 + L C (R_o + \sqrt{n})}$$

$$\omega = 755.93 \cdot 10^6 \Rightarrow f = \frac{\omega}{2\pi}$$

$$f = 120.31 \text{ MHz}$$

2.

* h-parametris:

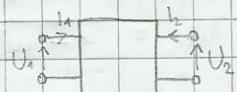

$$U_1 = h_{11} I_1 + h_{12} U_2$$

$$I_2 = h_{21} I_1 + h_{22} U_2$$


$$h_{11} = \left. \frac{U_1}{I_1} \right|_{U_2=0} [\Omega]$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{U_2=0} [\Omega] \Rightarrow h_{21}$$

$$h_{12} = \left. \frac{U_1}{U_2} \right|_{I_1=0} [\Omega]$$

$$h_{22} = \left. \frac{I_2}{U_2} \right|_{I_1=0} [\Omega]$$

* Transistor:

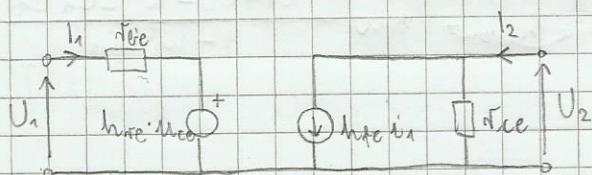


$$h_{11} = h_{11e} = h_{11e}$$

$$h_{12} = h_{12e}$$

$$h_{21} = h_{21e}$$

$$h_{22} = \left. \frac{I_2}{U_2} \right|_{I_1=0}$$

* Π -Gittermodell:

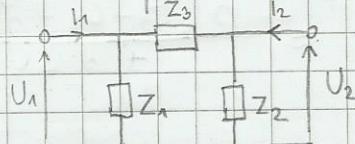

$$h_{11} = Z_1 \parallel Z_3$$

$$Z_1$$

$$h_{12} = Z_1 + Z_3$$

$$-Z_1$$

$$h_{21} = \frac{-Z_1}{Z_1 + Z_2 + Z_3}$$

$$h_{22} = \frac{Z_1 + Z_2 + Z_3}{Z_2 (Z_1 + Z_3)}$$

$$\omega_0 = 1 \text{ rad/s}$$

$$1/f_{rc} = 2.5 \cdot 10^{-4} \text{ s}$$


$$f_{rc} = 100$$

$$L = 40 \text{ nH}$$


$$f = 200 \text{ MHz}$$

Colpitts oscillator
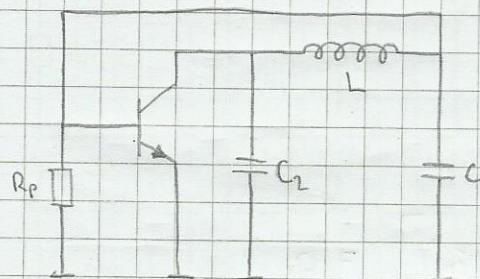
$$f_s = ? \quad \text{mit } \omega_0 \text{ nanopole} = ? \quad \frac{C_2}{C_1} = ? \quad f_{rc, \min} = ?$$


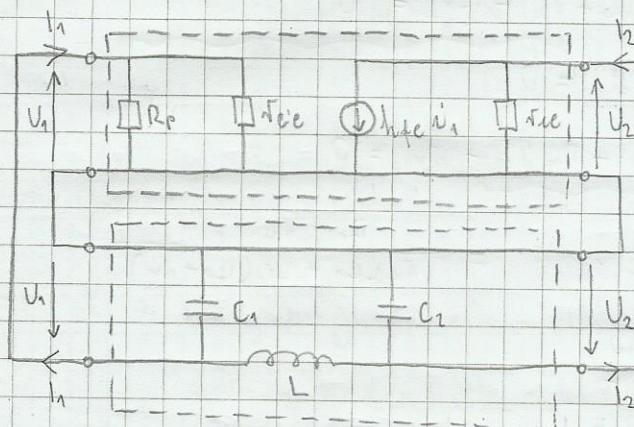
$$R_p = R_1 \parallel R_2 \parallel R_C$$



$$Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_1}$$

$$Z_L = j\omega L$$

$$h_{11}^1 = \frac{\frac{1}{j\omega C_1} \parallel j\omega L}{\frac{1}{j\omega C_1} + j\omega L} = \frac{\frac{j\omega L}{j\omega C_1}}{\frac{1}{j\omega C_1} + j\omega L} = \frac{j\omega L}{1 + j^2 \omega^2 C_1 L} = \frac{j\omega L}{1 + j^2 \omega^2 L C_1} \Rightarrow h_{11}^1 = \frac{j\omega L}{1 - \omega^2 L C_1}$$

$$h_{12}^1 = \frac{\frac{1}{j\omega C_1}}{\frac{1}{j\omega C_1} + j\omega L} = \frac{\frac{j\omega L}{j\omega C_1}}{\frac{1}{j\omega C_1} + j\omega L} = \frac{j\omega L}{1 + j^2 \omega^2 L C_1} \Rightarrow h_{12}^1 = \frac{1}{1 - \omega^2 L C_1}$$

$$h_{21}^1 = -\frac{1}{1 - \omega^2 L C_1}$$

$$h_{22}^1 = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L}{\frac{1}{j\omega C_1} + \left(\frac{1}{j\omega C_1} + j\omega L\right)} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j^2 \omega^2 L C_1 C_2}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_1} + j\omega L} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j^2 \omega^2 L C_1 C_2}{2 \frac{1}{j\omega C_1} + j\omega L} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j^2 \omega^2 L C_1 C_2}{\frac{2}{j\omega C_1} + j\omega L} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j^2 \omega^2 L C_1 C_2}{1 + j^2 \omega^2 L C_1} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j^2 \omega^2 L C_1 C_2}{j^2 \omega^2 L C_1}$$

$$= \frac{j(\omega C_1 + \omega C_2 + j^2 \omega^2 L C_1 C_2)}{1 + j^2 \omega^2 L C_1} \Rightarrow h_{22}^1 = j\omega \frac{\omega C_1 + \omega C_2 - \omega^2 L C_1 C_2}{1 - \omega^2 L C_1}$$

Transistor: $u_1 = h_{11} i_1 + h_{12} u_2 \quad (1)$

$$i_2 = h_{21} i_1 + h_{22} u_2 \quad (2)$$

π -cutterpol: $u_1 = -h_{21} i_1 + h_{22} u_2 \quad (3)$

$$-i_2 = -h_{21}^1 i_1 + h_{22}^1 u_2 \quad (4)$$

$$\textcircled{1} - \textcircled{3}: (h_{11} + h_{11}) u_1 + (h_{12} + h_{12}) u_2 = 0$$

$$\textcircled{2} + \textcircled{4}: (h_{21} - h_{21}) u_1 + (h_{22} + h_{22}) u_2 = 0$$

~~Kreisgelenk rechts~~ $\begin{array}{l} u_1 = 0 \\ u_2 = 0 \end{array}$

~~rechteckiges Rechteck~~: $\Delta = 0$

$$\begin{vmatrix} h_{11} + h_{11} & h_{12} - h_{12} \\ h_{21} - h_{21} & h_{22} + h_{22} \end{vmatrix} = 0$$

$$(h_{11} + h_{11})(h_{22} + h_{22}) - (h_{11} - h_{11})(h_{21} - h_{21}) = 0$$

$$\left(h_{11} + \frac{jwL}{1-w^2Lc_1} \right) \left(h_{22} + \frac{c_1+c_2-w^2Lc_1c_2}{1-w^2Lc_1} \right) - \left(h_{11} - \frac{1}{1-w^2Lc_1} \right) \left(h_{21} + \frac{1}{1-w^2Lc_1} \right) = 0$$

$$\alpha = 1 - w^2 L c_1$$

$$\frac{c_1 + c_2 - \alpha}{h_{11}h_{22} + jwLh_{11}} + h_{22} \frac{jwL}{\alpha} - \frac{w^2L[c_1 + c_2 - \alpha]}{\alpha^2} - h_{11}h_{21} - \frac{h_{21}}{\alpha} + \frac{h_{21}}{\alpha} + \frac{1}{\alpha} = 0$$

$$\alpha^2 h_{11}h_{22} + jwLh_{11}\alpha[c_1 + \alpha c_2] + jwLh_{22}\alpha - w^2L[c_1 + \alpha c_2] - \alpha^2 h_{11}h_{21} - \alpha h_{12} + \alpha h_{21} + 1 = 0$$

$$\Im\{ "inom" \} = 0$$

$$wLh_{11}\alpha[c_1 + \alpha c_2] + wLh_{22}\alpha = 0 \quad | : w\alpha$$

$$h_{11}(c_1 + \alpha c_2) + Lh_{22} = 0$$

$$h_{11}c_1 + \alpha h_{11}c_2 + Lh_{22} = 0$$

$$h_{11}c_1 + (1 - w^2Lc_1)h_{11}c_2 + h_{22}L = 0$$

$$h_{11}c_1 + h_{11}c_2 - w^2Lc_1c_2h_{11} + h_{22}L = 0$$

$$w^2Lc_1c_2h_{11} = h_{11}(c_1 + c_2) + h_{22}L \quad | : Lc_1c_2h_{11}$$

$$w^2 = \frac{c_1 + c_2}{Lc_1c_2} + \frac{h_{22}}{h_{11}c_1c_2}, \quad C_{eq} = \frac{c_1c_2}{c_1 + c_2}$$

$$w^2 = \underbrace{\frac{1}{Lc_{eq}}}_{w_e^2} + \underbrace{\frac{h_{22}}{h_{11}c_1c_2}}_{\text{Koeffizientenfaktor}}$$

$$\Re\{ "inom" \} = 0$$

$$\alpha^2 h_{11}h_{22} - w^2L(c_1 + \alpha c_2) - \alpha^2 h_{11}h_{21} - \alpha(h_{11} - h_{21}) + 1 = 0$$

$$\underbrace{\alpha^2(h_{11}h_{22} - h_{11}h_{21})}_{\Delta h} - \alpha(h_{12} - h_{21}) + 1 - w^2L \cdot (c_1 + \alpha c_2) = 0$$

$$\alpha = 1 - w_e^2 L c_1 = 1 - \frac{1}{Lc_{eq}} L c_1 = 1 - \frac{c_1}{c_1c_2} = 1 - \frac{c_1 + c_2}{c_1} = 1 - \frac{c_1}{c_{eq}} \neq 1$$

$$a = -\frac{c_1}{c_2} \quad c_1 = c_2 = 0$$

$$a^2 \Delta h + a(h_{21} - h_{22}) + 1 - \underbrace{w^2 L}_{(c_1 - c_1)} = 0$$

$$a^2 \Delta h + a(h_{21} - h_{22}) + 1 = 0$$

$$\frac{c_2}{c_1} = n = -\frac{1}{a}$$

$$\frac{1}{n^2} \Delta h - \frac{1}{n} (h_{21} - h_{22}) + 1 = 0 \quad | \cdot n^2$$

$$n^2 - n(h_{21} - h_{22}) + \Delta h = 0, \quad h_{22} \approx 0$$

$$n^2 - h_{21} n + \Delta h = 0$$

Vietnevne formule:

$$ax^2 + bx + c = 0$$

$$\left. \begin{array}{l} x_1 + x_2 = -\frac{b}{a} \\ x_1 \cdot x_2 = \frac{c}{a} \end{array} \right\} \quad \left. \begin{array}{l} n_1 + n_2 = \frac{h_{21}}{1} = h_{21} \\ n_1 \cdot n_2 = \frac{\Delta h}{1} = \Delta h \end{array} \right.$$

Detektionsfaktor: $n_1 \gg n_2 \Rightarrow n_1 \approx h_{21}$

$$h_{21} \cdot n_2 = \Delta h \quad | : h_{21}$$

$$n_2 = \frac{\Delta h}{h_{21}}$$

$$\frac{\Delta h}{h_{21}} < n < h_{21}$$

$$h_{21} = h_{FE} = 100$$

$$\Delta h = h_{21} n_2 - \underbrace{h_{21} h_{21}}_{\approx 0} = h_{21} n_2 = \left| \begin{array}{l} h_{21} = 100 \\ h_{21} = 100 \cdot 10^{-4} = 2.5 \cdot 10^{-4} \end{array} \right| = 10^2 \cdot 2.5 \cdot 10^{-4} = 0.25$$

$$\frac{\Delta h}{h_{21}} = 0.0025$$

$$n = \frac{c_2}{c_1} \Rightarrow 0.0025 < \frac{c_2}{c_1} < 100$$

c) $\frac{c_2}{c_1} = 1, \quad h_{FE, \min} = ?$

$$\frac{c_2}{c_1} = n = 1$$

$$n^2 - h_{21} n + \Delta h = 0$$


$$1 - h_{21} + 0.25 = 0 \Rightarrow h_{21} = h_{FE, \min} = 1.25$$

$$\begin{aligned}
 C_1 &= 91 \mu\text{F} & h_{11} &= 15.2 \Omega \\
 C_2 &= 43 \mu\text{F} & h_{12} &= -0.969 \\
 L &= 0.11 \mu\text{H} & h_{21} &= 0.0672 \\
 C_3 &= 0.1 \mu\text{F} & h_{22} &= 2.66 \text{ mS} \\
 f &= 1 \text{ Hz} & \text{magnetoohm} &= 2
 \end{aligned}$$

AC analiza:

$C_2, C_3 \rightarrow$ hantový mož

zavojenka Pr. \rightarrow prameň hrot

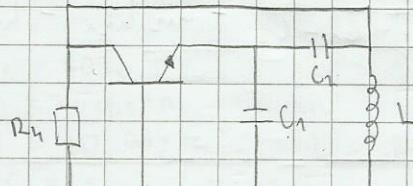


Colpitts oscillator

$$\omega_0 = \frac{1}{\sqrt{LC}} = 15.2 \text{ rad/s}$$

$$h_{11} = h_{12}$$


$$h_{21} = h_{22}$$

$$h_{22} = h_0$$

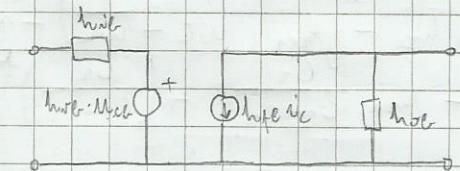

lineárna závislosť

není na mali signál:

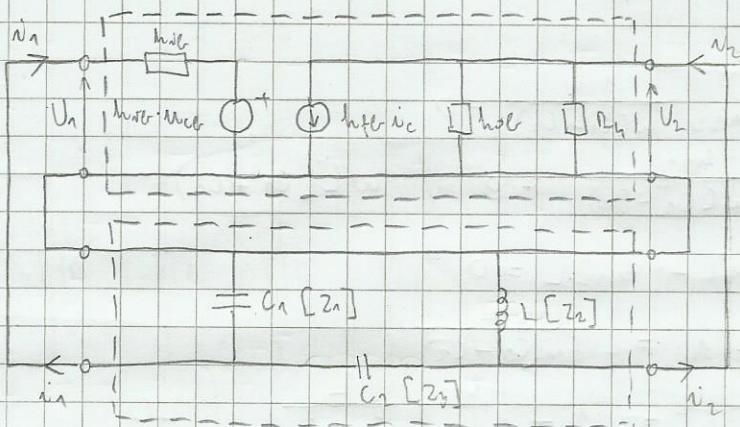

$$Z_1 = \frac{1}{j\omega C_1} \Rightarrow Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = j\omega L \Rightarrow Z_2 = j\omega L$$

$$Z_3 = \frac{1}{j\omega C_2} \Rightarrow Z_3 = \frac{1}{j\omega C_2}$$

Th - Štefanopol:

$$h_{11} = Z_1 // Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{\frac{1}{j\omega C_1} \cdot \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{\frac{j\omega C_1 j\omega C_2}{j\omega C_1 j\omega C_2}}{\frac{j\omega C_1 + j\omega C_2}{j\omega C_1 j\omega C_2}} = \frac{1}{j\omega(C_1 + C_2)}$$

$$h_{12} = \frac{Z_1}{Z_1 + Z_2} = \frac{h_{11}}{Z_2} = \frac{1}{j\omega(C_1 + C_2)} \cdot j\omega C_2 = \frac{C_2}{C_1 + C_2}$$

$$h_{21} = -h_{12} = -\frac{C_2}{C_1 + C_2}$$

$$h_{22} = \frac{Z_1 + Z_2 + Z_3}{Z_2(Z_1 + Z_2)} = \frac{\frac{1}{j\omega C_1} + j\omega L + \frac{1}{j\omega C_2}}{j\omega L \left(\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \right)} = \frac{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}}{j\omega L \left(\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \right)} + \frac{j\omega L}{j\omega L \left(\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \right)} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

$$= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_1 + j\omega C_2} = \frac{1}{j\omega C_1} + \frac{-j\omega C_1 C_2}{j\omega C_1(j\omega C_1 + j\omega C_2)} = \frac{1}{j\omega C_1} + \frac{-j\omega C_1 C_2}{j\omega C_1(j\omega C_1 + j\omega C_2)} = \frac{1}{j\omega C_1} + \frac{C_1 C_2}{j\omega C_1 + j\omega C_2}$$

transformácia:

$$\begin{aligned}
 \textcircled{1} \quad u_1 &= h_{11} i_1 + h_{12} u_2 \\
 \textcircled{2} \quad i_2 &= h_{21} i_1 + h_{22} u_2
 \end{aligned}$$

Th - Štefanopol:

$$\begin{aligned}
 \textcircled{3} \quad u_1 &= -h_{11} i_1 + h_{12} u_2 \\
 \textcircled{4} \quad -i_2 &= h_{21} i_1 + h_{22} u_2
 \end{aligned}$$

$$\textcircled{1} - \textcircled{3}: (h_{11} + h_{11}) i_1 + (h_{12} - h_{11}) u_2 = 0$$

$$\textcircled{2} + \textcircled{4}: (h_{21} - h_{21}) i_1 + (h_{22} + h_{21}) u_2 = 0$$

$$\Delta h = 0$$

$$(h_{11} + h_{12})(h_{21} + h_{22}) - (h_{12} + h_{21})(h_{11} + h_{22}) = 0$$

$$h_{11}h_{22} + h_{12}h_{12} + h_{11}h_{22} + h_{11}h_{12} - h_{12}h_{21} + h_{12}h_{11} + h_{11}h_{21} - h_{12}h_{11} = 0$$

$$h_{11}h_{22} + \frac{h_{11}}{\rho w L} + \text{Jwh}_{11}C + \frac{h_{22}}{\rho w (C_1+C_2)} + \frac{1}{\rho w (C_1+C_2)} \left(\frac{1}{\rho w L} + \rho w C \right) - h_{12}h_{21} - h_{12} \frac{C_2}{C_1+C_2} + h_{21} \frac{C_2}{C_1+C_2} + \frac{(C_2)}{(C_1+C_2)^2} = 0$$

$$h_{11}h_{22} + \rho h_{11} \left(wC - \frac{1}{wL} \right) + \rho h_{22} \frac{1}{w(C_1+C_2)} - w^2 L \frac{1}{C_1+C_2} - h_{12}h_{21} - h_{12} \frac{C_2}{C_1+C_2} + h_{21} \frac{C_2}{C_1+C_2} + \frac{(C_2)}{(C_1+C_2)^2} = 0$$

$$\Im \{ \text{ "niveau"} \} = 0$$

$$h_{11} \left(wC - \frac{1}{wL} \right) - h_{22} \frac{1}{w(C_1+C_2)} = 0$$

$$h_{11} \cdot \frac{w^2 LC - 1}{wL} - \frac{h_{22}}{w(C_1+C_2)} = 0 \quad | \cdot wL(C_1+C_2)$$

$$h_{11}(C_1+C_2)(w^2 LC - 1) - h_{22}L = 0$$

$$w^2 LC - 1 = \frac{h_{22}L}{h_{11}(C_1+C_2)}$$

$$LC w^2 = 1 + \frac{h_{22}}{h_{11}} \frac{L}{C_1+C_2} \quad | : LC$$

$$w^2 = \underbrace{\frac{1}{LC}}_{w_0} + \frac{h_{22}}{h_{11}} \cdot \frac{1}{C_1+C_2} \cdot \frac{C_1+C_2}{C_1 \cdot C_2} = \frac{1}{LC} + \frac{h_{22}}{h_{11}} \frac{1}{C_1 \cdot C_2}$$

$$w^2 = \frac{1}{0.11 \cdot 10^{-6} \cdot \frac{91 \cdot 47}{91+47} \cdot 10^{-12}} + \frac{2.66 \cdot 10^{-3}}{15.2} \cdot \frac{1}{91 \cdot 47 \cdot 10^{24}} = 3.56 \cdot 10^{17}$$

$$w = 2\pi f \Rightarrow f = 94,97 \text{ MHz}$$

- also interessante obere Frequenz Resonanz:

$$w = w_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.11 \cdot 10^{-6} \cdot \frac{91 \cdot 47}{91+47} \cdot 10^{-12}}} = 557.96 \cdot 10^6$$

$$f_0 = 88.8 \text{ MHz}$$

$$\Re \{ \text{ "niveau"} \} = 0$$

$$h_{11}h_{22} + \frac{C}{C_1+C_2} - \frac{1}{w^2 L(C_1+C_2)} - h_{12}h_{21} + (h_{21} - h_{12}) \frac{C_2}{C_1+C_2} + \left(\frac{C_2}{C_1+C_2} \right)^2 = 0$$

$$w = w_0 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{w^2 L(C_1+C_2)} = \frac{LC}{L(C_1+C_2)} = \frac{C}{C_1+C_2}$$


$$h_{11} + \frac{c_1}{c_1+c_2} - \frac{c_1}{c_1+c_2} - h_{21}h_{21} + \frac{c_2}{c_1+c_2} (h_{21}) - h_{21} \frac{c_2}{c_1+c_2} + \left(\frac{c_2}{c_1+c_2} \right)^2 = 0$$

$$h_{21} = \frac{h_{11}h_{22} - h_{21} \frac{c_2}{c_1+c_2} + \left(\frac{c_2}{c_1+c_2} \right)^2}{h_{12} - \frac{c_2}{c_1+c_2}} = \frac{18.2 \cdot 26.6 \cdot 10^3 - 0.0672 \cdot \frac{43}{91+43} + \left(\frac{43}{91+43} \right)^2}{0.0672 - \frac{43}{91+43}}$$

$$\left. \begin{array}{l} h_{21} = -0.48 \\ h_{12} = -0.969 \end{array} \right\} \quad | \text{hypel} > \text{Thail} \quad \Rightarrow \text{nicht monopolistische Nachfrage}$$


4. $r_{ce} = 1000 \Omega$ $R_C = 1000 \Omega$ RC-Schaltung
 $r_{ue} = 40000 \Omega$ $R_L = 1000 \Omega$
 $f = 20000 \text{ Hz}$ $R_o = 800 \Omega$
 $C = ?$ $i_{fe} = ?$

AC-Analyse:

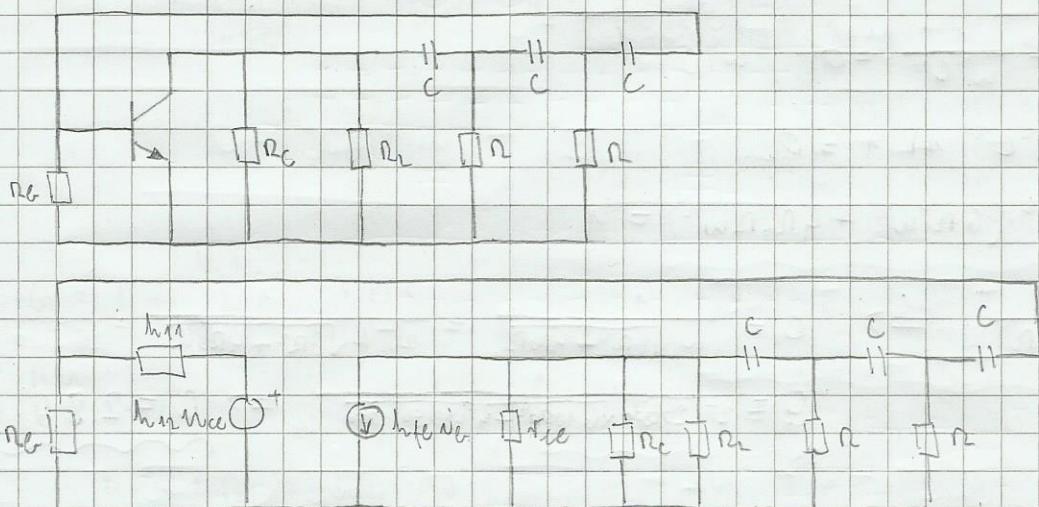

$$r_{ce} = R_C \parallel h_{21} = 1000 \Omega$$

$$h_{21} = h_{re} = 0$$

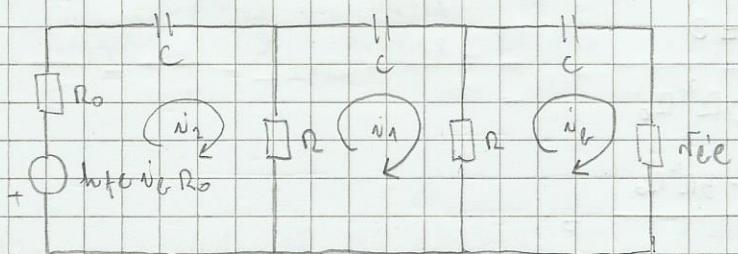

$$R_o = r_{ue} \parallel R_L \parallel R_o = 40000 \parallel 1000 \parallel 800$$

$$R_o = \frac{40000}{91} \approx 439.56 \Omega$$

$$\textcircled{1} \quad i_0 \left(R + r_{ce} + \frac{1}{j\omega C} \right) - i_1 R = 0$$

$$\textcircled{2} \quad i_1 \left(R + R + \frac{1}{j\omega C} \right) - i_0 R - i_2 R = 0$$

$$\textcircled{3} \quad i_2 \left(R_o + R + \frac{1}{j\omega C} \right) - i_1 R + i_{fe} R_o i_0 = 0$$

$$\begin{array}{ccccccc} i_0 & & i_1 & & i_2 & & \\ R + r_{ce} + \frac{1}{j\omega C} & & -R & & 0 & & \\ -R & & 2R + \frac{1}{j\omega C} & & -R & & = 0 \\ h_{fe} R_o & & -R & & R_o + R + \frac{1}{j\omega C} & & \end{array}$$

$$\begin{vmatrix}
 R + \frac{1}{j\omega C} & -R & R + \frac{1}{j\omega C} & -R \\
 h_{FE} R_0 & -R & -R & 2R + \frac{1}{j\omega C} \\
 \end{vmatrix} = 0$$

$$R \left[-R \left(R + \frac{1}{j\omega C} + \frac{1}{j\omega C} \right) + R h_{FE} R_0 \right] + \left(R_0 + R + \frac{1}{j\omega C} \right) \left[\left(2R + \frac{1}{j\omega C} \right) \left(R + \frac{1}{j\omega C} + \frac{1}{j\omega C} \right) - R^2 \right] = 0$$

$$-2R^3 - \frac{R^2}{j\omega C} + R^2 h_{FE} R_0 + \left(R_0 + R + \frac{1}{j\omega C} \right) \left(4R^2 + \frac{4R}{j\omega C} - \frac{1}{w^2 C^2} - R^2 \right) = 0$$

$$-2R^3 - \frac{R^2}{j\omega C} + R^2 h_{FE} R_0 + 3R_0 R^2 + \frac{4R_0 R}{j\omega C} - \frac{R_0}{w^2 C^2} + 3R^3 + \frac{4R^2}{j\omega C} - \frac{R}{w^2 C^2} + \frac{3R^2}{j\omega C} - \frac{4R}{w^2 C^2} + \frac{1}{j\omega C^3} = 0$$

$$R^3 + j \frac{R^2}{wC} (1 - 4 - 3) + R^2 R_0 (h_{FE} + 3) - j \frac{4R_0 R}{wC} - \frac{R_0 + R + 4R}{w^2 C^2} + j \frac{1}{w^2 C^3} = 0$$

$\Im\{ \text{"invar"} \} = 0$

$$-6 \frac{R^2}{wC} - 4 \frac{R_0 R}{wC} + \frac{1}{w^2 C^3} = 0 \quad | w^2 C^3$$

$$-6R^2 w^2 C^2 - 4R_0 R w^2 C^2 + 1 = 0$$

$$C^2 (6R^2 w^2 + 4R_0 R w^2) = 1$$

$$C = \frac{1}{w^2 (6R^2 + 4R_0 R)} \Rightarrow C = \frac{1}{w \sqrt{6R^2 + 4R_0 R}} = \frac{1}{2\pi f \sqrt{6R^2 + 4R_0 R}}$$

$$C = \frac{1}{2\pi \cdot 20000 \sqrt{6 \cdot 1000^2 + 4 \cdot 430.56 \cdot 1000}} \Rightarrow C = 2.86 \text{ nF}$$

$\Re\{ \text{"invar"} \} = 0$


$$R^3 + R^2 R_0 (h_{FE} + 3) - \frac{R_0 + 5R}{w^2 C^2} = 0$$

$$R^2 R_0 h_{FE} = \frac{5R + R_0}{w^2 C^2} - R^3 - 3R^2 R_0$$

$$h_{FE} = \frac{\frac{5R + R_0}{w^2 C^2} - R^3 - 3R^2 R_0}{R^2 R_0} = \dots$$

$$h_{FE} = 90.73$$
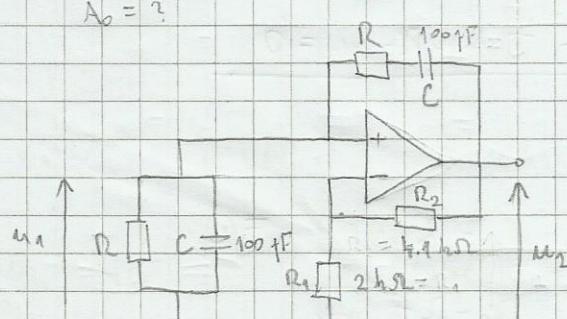
$$\begin{aligned}
 f &= 787.4 \text{ Hz} \\
 R &= ? \\
 A_b &= ?
 \end{aligned}$$



$$u_1 = u_2 \cdot \frac{\frac{1}{R_{11} + jwC}}{\frac{1}{R_{11}} + \left(R_2 + \frac{1}{jwC} \right)} = u_2 \cdot \frac{\frac{1}{R}}{\frac{1}{1+jwRC} + \frac{1+jwR_2}{jwC}}$$

$$\frac{u_2}{u_1} = \frac{\frac{R}{1+jwRC} + \frac{1+jwR_2}{jwC}}{\frac{R}{1+jwRC}} = 1 + \frac{\frac{1+jwR_2}{jwC}}{\frac{R}{1+jwRC}} =$$

$$= 1 + \frac{(1+jwR_2)^2}{jwR_2} = 1 + \frac{1 + 2jwR_2 - w^2R_2^2}{jwR_2} =$$

$$= 1 + \frac{1}{jwR_2} + 2 - \frac{wR_2}{j} = 3 - j \frac{1 - (wR_2)^2}{wR_2}$$

$$\Im\{ \frac{u_2}{u_1} \} = 0$$

$$\frac{1 - (wR_2)^2}{wR_2} = 0 \Rightarrow (wR_2)^2 = 1$$

$$wR_2 = 1 \Rightarrow R = \frac{1}{wC} = \frac{1}{2\pi f C} = \frac{1}{2\pi \cdot 48400 \cdot 1}$$

$$\underline{R = 2021.27 \Omega}$$

$$G_1 = 1 + \frac{4.1}{2} = 3.05$$

$$\frac{u_2}{u_1} = 3$$

$$u_2 = u_{12} = u_{ab} \cdot A_o$$


$$u_1 = u_{21} + u_{ab} \Rightarrow u_{ab} = u_1 - u_{21} = \frac{1}{3} u_2 - \frac{R_1}{R_1 + R_2} u_2 = \left(\frac{1}{3} - \frac{R_1}{R_1 + R_2} \right) u_2$$

$$u_2 = \left(\frac{1}{3} - \frac{R_1}{R_1 + R_2} \right) u_1 \cdot A_o \Rightarrow A_o = \frac{1}{\frac{1}{3} - \frac{R_1}{R_1 + R_2}} = \frac{1}{\frac{1}{3} - \frac{2}{4.1 + 2}}$$

$$\underline{A_o = 183}$$


6. Gyrator - Clappor oscillator

V_{DD}
P_{r.}

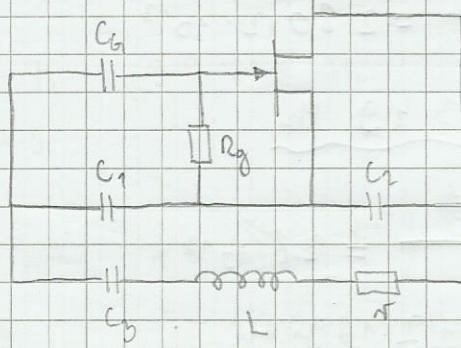

$$\begin{aligned}
 C_1 = C_2 &= 500 \mu F & r &= 15 \Omega \\
 C_3 &= 100 \mu F & r_d &= 5 \Omega \\
 C_g &= 0.1 \mu F & R_g &= 560 \Omega \\
 L &= 500 \mu H & f &= ? \\
 \end{aligned}$$

AC analysis:

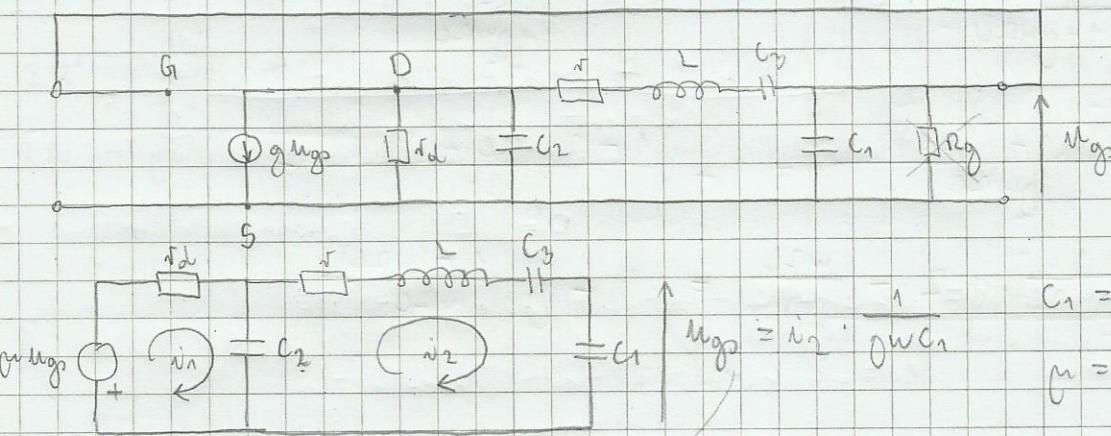

$C_g \rightarrow$ leeres Objekt

$R_g \rightarrow \infty$

$$C_1 = C_2 = C$$

$$\mu = g \cdot r_d$$

↳ Stromkreis

$$(1) i_1 \left(r_d + \frac{1}{jwC} \right) + \mu u_{gp} - i_2 \frac{1}{jwC} = 0$$

$$(2) i_2 \left(\frac{1}{jwC} + r + jwL + \frac{1}{jwC_3} + \frac{1}{jwC} \right) - i_1 \cdot \frac{1}{jwC} = 0$$

$$\begin{vmatrix}
 r_d + \frac{1}{jwC} & -\frac{1}{jwC} & \frac{\mu}{jwC} \\
 -\frac{1}{jwC} & \frac{1}{jwC} + r + jwL + \frac{1}{jwC_3} &
 \end{vmatrix} = 0$$

$$\left(r_d - j \frac{1}{wC} \right) \left(-j \frac{2}{wC} + r + jwL - j \frac{1}{wC_3} \right) - j \frac{1}{wC} \left(j \frac{1}{wC} - j \frac{\mu}{wC} \right) = 0$$

$$-j \frac{2r_d}{wC} + r r_d + jw r_d L - j \frac{r_d}{wC_3} - \frac{2}{w^2 C^2} + j \frac{r}{wC} + \frac{L}{C} - \frac{1}{w^2 C C_3} + \frac{1}{w^2 C^2} - \frac{\mu}{w^2 C^2} = 0$$

$$r r_d + \frac{1}{w^2 C^2} (-2 + 1 - \mu) + \frac{L}{C} - \frac{1}{w^2 C C_3} + j \left[\frac{2r_d}{wC} + w r_d L - \frac{r_d}{wC_3} - \frac{r}{wC} \right] = 0$$

$$\Im \{ \text{unreal} \} = 0$$

$$-\frac{2r_d}{wC} + w r_d L - \frac{r_d}{wC_3} - \frac{r}{wC} = 0 \quad | \cdot w$$

$$-2 \frac{r_d}{C} + w^2 r_d L - \frac{r_d}{C_3} - \frac{r}{C} = 0$$

$$w^2 = \frac{\frac{r_d}{C_3} + \frac{r}{C} + 2 \frac{r_d}{C L}}{\frac{r_d}{C_3} + 2 \frac{r_d}{C}} = 2.8012 \cdot 10^{13}$$

$$w = 2\pi f \Rightarrow f = 842349 \text{ Hz}$$

$$\frac{\frac{r_d}{C_3} + 2 \frac{r_d}{C}}{\frac{r_d}{C_3} + 2 \frac{r_d}{C}} = 2.8 \cdot 10^{13}$$

$$\text{also } g \cdot r_d = 0 \Rightarrow w^2 = \frac{r_d}{C L} = 2.8 \cdot 10^{13}$$

$$f = 842169 \text{ Hz}$$

$$\operatorname{Re} \{ " \text{resonanz"} \} = 0$$

$$\sqrt{\omega_0^2 + \frac{1}{w^2 C_x^2}} (-1 - j\mu) + \frac{L}{C} - \frac{1}{w^2 C_0 C_x} = 0$$

$$\sqrt{\omega_0^2} - \frac{1}{w^2 C_x^2} - \frac{\mu}{w^2 C_x^2} + \frac{L}{C} - \frac{1}{w^2 C_0 C_x} = 0 \quad | \cdot w^2 C^2$$

$$w^2 \sqrt{\omega_0^2} C^2 - 1 - \mu + w^2 L C - \frac{C}{C_0} = 0$$


$$\mu = w^2 \sqrt{\omega_0^2} C^2 + w^2 L C - \frac{C}{C_0} - 1 = 2.80 \cdot 12 \cdot 10^{13} \cdot 15 \cdot 5000 \cdot (800 \cdot 10^{-12})^2 + 2.80 \cdot 12 \cdot 10^{13} \cdot 500 \cdot 10^{-6} \cdot 800 \cdot 10^{-12}$$

$$\mu = 1.528$$

$$w_0 \cdot \tau = 0 \Rightarrow \omega = 100 \Rightarrow g = \frac{\mu}{\omega_0} = \frac{1}{5000}$$

$$g = 0.2 \text{ mS}$$

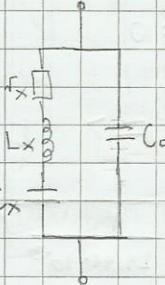7. $C_0 = 0.3 \text{ } \mu\text{F}$
 $C_x = 0.003 \text{ } \mu\text{F}$
 $L_x = 21.11 \text{ mH}$
 $Q = 20000$
 $f_s = ? \quad f_p = ? \quad \tau_x = ?$



$$\begin{aligned} Z_x &= \frac{\left(\tau_x + j\omega L_x + \frac{1}{j\omega C_x} \right) \cdot \frac{1}{j\omega C_0}}{\tau_x + j\omega L_x + \frac{1}{j\omega C_x} + \frac{1}{j\omega C_0}} = \tau_x \approx 0 \\ &= \frac{\frac{L_x}{C_0} - \frac{1}{j\omega C_x C_0}}{-\omega^2 L_x C_x C_0 + C_x + C_0} = \frac{\frac{w^2 L_x C_x - 1}{j\omega C_x C_0}}{C_x + C_0 - \frac{w^2 L_x C_x C_0}{j\omega C_x C_0}} \\ &= \frac{1 - \frac{w^2 L_x C_x}{\omega (w^2 L_x C_x C_0 - C_x - C_0)}}{0} \end{aligned}$$

* rechteckiger Verstärkerzustand:

$$Z_x = 0$$

$$1 - \frac{w^2 L_x C_x}{\omega} = 0$$

$$\omega_s = \frac{1}{\sqrt{L_x C_x}}$$

$$f_s = \frac{1}{2\pi \sqrt{L_x C_x}} = \frac{1}{2\pi \sqrt{0.0211 \cdot 3 \cdot 10^{-15}}} \text{ Hz}$$

$$f_s = 19999327.29 \text{ Hz}$$

$$\Delta f = f_p - f_s = 99748 \text{ Hz}$$

$$\frac{f_p}{f_s} = 1.005$$

$$Q = \frac{\tau_x}{\omega_s} \Rightarrow \omega = \frac{\omega_s}{Q} = \frac{2\pi f_s L}{Q} = \frac{2\pi \cdot 19999327.29 \cdot 21.11 \cdot 10^{-3}}{20000}$$

$$\tau_x = 132.63 \text{ s}$$

* paralleler Resonanzzustand:

$$Z_x \rightarrow \infty \quad (Y_x = 0)$$

$$\omega^2 L_x C_x C_0 - C_x - C_0 = 0$$

$$w_p = \sqrt{\frac{C_x + C_0}{L_x C_x C_0}}$$

$$f_p = \frac{1}{2\pi} \sqrt{\frac{1}{L_x} \left(\frac{1}{C_0} + \frac{1}{C_x} \right)}$$

$$f_p = 20999075.17 \text{ Hz}$$

C_s

\underline{Z}_x

$$Z_{wh} = Z_{Cs} + Z_x = \frac{1}{j\omega C_s} + Z_x$$

$$f_s = ? \quad \text{mit } C_s = 0.3 \mu F \quad \text{oder } C_s = 10 \mu F$$

$$\begin{aligned} Z_{wh} &= \frac{1}{j\omega C_s} + \frac{1 - \omega^2 L_x C_x}{j\omega (w^2 L_x C_x C_o - C_x - C_o)} = -\frac{j(w^2 L_x C_x C_o - C_x - C_o) + jC_s + j\omega^2 L_x C_x C_s}{\omega C_s (w^2 L_x C_x C_o - C_x - C_o)} \\ &= \frac{j(C_s(1 + \omega^2 L_x C_x) + C_x + C_o - \omega^2 L_x C_x C_o)}{\omega C_s (w^2 L_x C_x C_o - C_x - C_o)} \end{aligned}$$

* Resonanzfrequenz: $Z_{wh} = 0$

$$C_s(1 - \omega^2 L_x C_x) + C_x + C_o - \omega^2 L_x C_x C_o = 0$$

$$C_s - \omega^2 L_x C_x C_s + C_x + C_o - \omega^2 L_x C_x C_o = 0$$

$$\omega^2 = \frac{C_s + C_x + C_o}{L_x C_x C_s + L_x C_x C_o} \Rightarrow f = \frac{1}{2\pi} \sqrt{\frac{C_s + C_x + C_o}{L_x C_x (C_s + C_o)}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L_x} \left(\frac{1}{C_x} + \frac{1}{C_s + C_o} \right)} = \frac{1}{2\pi} \sqrt{\frac{1}{21.11 \cdot 10^{-3}} \left(\frac{1}{0.003 \cdot 10^{-12}} + \frac{1}{0.3 \cdot 10^{-12} + C_o} \right)}$$

$$f(C_s = 0.3 \mu F) = 20.049 \text{ Hz}$$

$$f(C_s = 10 \mu F) = 20.002 \text{ Hz}$$