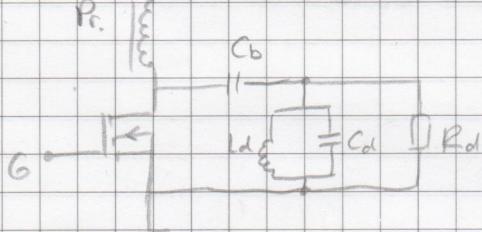
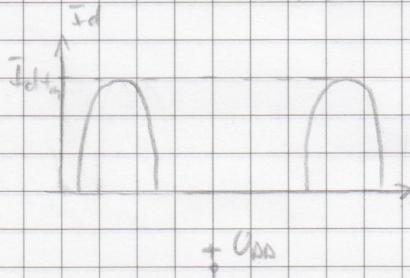


8.

PTF 10136

klasa C

 $f = 1 \text{ MHz}$ 

$$\cos \theta = \frac{U_p - U_{G0}}{U_{Gm}} = \frac{1 - (-1)}{5.85} = 0.302$$

$$\theta = 70^\circ$$

$$h_u = \frac{U_{dm}}{U_{dA}} = \frac{U_{D0} - U_{dm\min}}{U_{D0}} = \frac{28 - 4}{28} = 0.857$$

$$f_0(\theta) = 0.252 \rightarrow \text{istosuširina komp.}$$

$$f_1(\theta) = 0.436 \rightarrow 1. \text{ harmonik}$$

$$P_{od} = U_{D0} \cdot I_{od} = U_{D0} \cdot I_{d(t)m} \cdot f_0(\theta) = 28 \cdot 1.1 \cdot 0.252 = 7.76 \text{ W}$$

$$P_k = \frac{U_{dm}}{2} \cdot I_{dm} = \frac{(U_{D0} - U_{dm\min})}{2} I_{d(t)m} f_1(\theta) = \frac{(28 - 4)}{2} \cdot 1.1 \cdot 0.436$$

$$P_k = 5.75 \text{ W}$$

$$R_d = \frac{U_{dm}}{I_{dm}} = \frac{U_{D0} - U_{dm\min}}{I_{d(t)m} \cdot f_1(\theta)} = \frac{28 - 4}{1.1 \cdot 0.436} = 50 \Omega$$

$$Q = \frac{R_d}{2\pi f L_d} \Rightarrow L_d = \frac{R_d}{2\pi f Q} = \frac{50}{2\pi \cdot 10^6 \cdot 12} = 0.663 \mu H$$

$$C_{dl} = \frac{1}{(2\pi f)^2 L_d} = 38.2 \text{ nF}$$

$$L = \frac{f_1(\theta)}{2f_0(\theta)} \quad \text{za } h_u = 1$$

$$L = \frac{f_1(\theta)}{2f_0(\theta)} \cdot h_u \quad \text{za } h_u < 1$$


$$\begin{aligned} \theta &\downarrow \eta & \uparrow \\ \theta = 0 &\Rightarrow \eta = 0 \end{aligned}$$

Pojedinka snage

- cilj - sito manja dissipacija (> 2)

- 4 kW

- krajnji od 0.5 MW

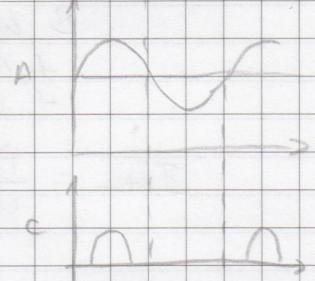

9.

Klasa B

 V_{oss}

$$U_{DD\ max} = \frac{V_{oss}}{2} = 14V$$

$$U_{DD} = U_{DD\ max} \cdot 0.8 = 11.2V$$

$$P_{DD} = P_u + P_d = P_{DD} \cdot \eta + P_d =$$

$$P_{DD} = \frac{P_d}{1-\eta} = \frac{0.8 \cdot P_d}{1-\eta} = \frac{0.8 \cdot 25}{1-0.6} = 50W$$

$$P_u = P_{DD} \eta = 30W$$

$$P_{DD} = U_{DD} \cdot I_{DD} = U_{DD} I_{DD\ min} f_0(\theta)$$

B klasa $\theta = 90^\circ$

$$f_0(90^\circ) = 0.318$$

$$f_1(90^\circ) = 0.5$$

$$I_{DD\ min} = \frac{P_{DD}}{U_{DD} f_0(\theta)} = \frac{50}{11.2 \cdot 0.318} = 14.03A$$

$$P_u = \frac{U_{DD} I_{DD}}{2} = \frac{U_{DD} I_{DD\ min} f_1(\theta)}{2}$$

$$U_{DD} = \frac{2 P_u}{I_{DD\ min} f_1(\theta)} = \frac{2 \cdot 30}{14.03 \cdot 0.5} = 8.55V$$

$$U_{DD\ min} = U_{DD} - U_{DD\ max} = 11.2 - 8.55 = 2.65V$$

Dodatek niskom zadaťku

(10.)

$$K = K_{SK} + K_{KH} + K_{HO} = 0.5 + 0.2 + 0.8 = 1.5 \text{ } ^\circ\text{C/W}$$

$$P_{dT} = \frac{T_s - T_0}{K} = \frac{130 - 50}{1.5} = 53.33 \text{ W}$$

$$P_{DD} = P_K + P_d = P_K + P_{dT}$$


$$\frac{P_K}{2} = P_K + P_{dT}$$

$$P_K = P_{dT} \cdot \frac{2}{1-2} = 53.33 \cdot \frac{0.75}{0.25} = 160 \text{ W}$$

(11.)

klasa C

je, A

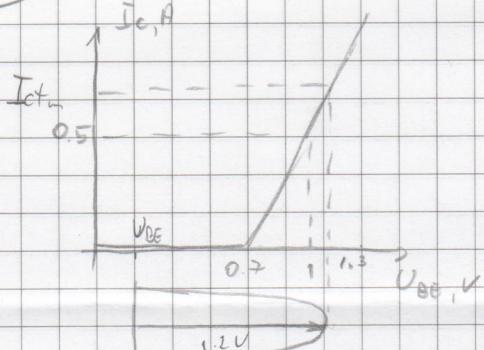

$$I_C = \frac{5}{3} (V_{BE} - 0.7) \text{ za } V_{BE} > 0.7 \text{ V}$$

$$I_{C(t_m)} = \frac{5}{3} (1.3 - 0.7) = \frac{5}{3} \cdot 0.6 = 1 \text{ A}$$

$$\cos \theta = \frac{V_{BEz} - V_{BB}}{V_{BEz}} = \frac{0.7 - 0.1}{1.2} = 0.5$$

$$\theta = 60^\circ$$

$$I_{Cs} = I_{C(t_m)} f_0(\theta) = 1 \cdot 0.218 = 0.218 \text{ A}$$

$$\eta = \frac{P_K}{P_{CC}} = \frac{\frac{V_{CC} \cdot I_{Cs}}{2} - \frac{(V_{CC} - V_S) I_{C(t_m)} f_1(\theta)}{2} - \frac{27 \cdot 1 \cdot 0.391}{2}}{P_{CC}}$$

$$P_{CC} = V_{CC} \cdot I_{Cs} = 27 \cdot 0.218 = 6,104 \text{ W}$$

$$P_K = 5.278 \text{ W}$$

$$\eta = \frac{5.278}{6,104} = 86.47\%$$

$$G = 10 \log \frac{P_K}{P_{K2}} = 10 \log \frac{5.278}{0.5} = 10.23 \text{ dB}$$

$$R_o = \frac{V_{CC}}{I_{Cs}} = \frac{27}{0.391} = 69 \text{ k}\Omega$$

$$P_d = P_{CC} - P_K = 6,104 - 5.278 = 0.825 \text{ W}$$

$$P_{dT} = P_d + P_{K2} = 1.325 \text{ W}$$

$$K = \frac{T_s - T_0}{P_{dT}} = \frac{130 - 50}{1.325} = 90.53 \text{ } ^\circ\text{C/W}$$

$$K_{HO} = K - K_{Si} - K_{KH} = 90.53 - 15 - 6 = 69.53 \text{ } ^\circ\text{C/W}$$

(12)

$$f_3(\Theta)_{max} = 0.185$$

$$\Theta = 40^\circ$$

$$P_{k3} = \frac{U_{ce} \cdot I_{c3m}}{2} = \frac{U_{ce} \cdot I_{ctm} \cdot f_3(\Theta)}{2}$$

$$I_{ctm} = \frac{2 \cdot P_{k3}}{U_{cm} f_3(\Theta)} = \frac{2 \cdot 1}{(12 - 2) \cdot 0.185} = 1.081 \text{ A}$$

$$P_{cc} = U_{cc} \cdot I_{cs} = U_{cc} \cdot I_{ctm} \cdot f_0(\Theta) = 12 \cdot 1.081 \cdot 0.147 = 1.9 \text{ W}$$

$$\eta = \frac{P_{cc}}{P_{k3}} = 52.43\%$$

(13)

$$\eta = 0.865$$

$$U_{cs} = 0 \Rightarrow h_u = 1$$

$$\eta = \frac{1}{2} h_u h_i$$

$$h_i = 2 \eta = 1.73 \Rightarrow \Theta = 70^\circ$$

$$h_i = \frac{f_1(\Theta)}{f_0(\Theta)}$$

$$P_{k3} = \frac{U_{cm} \cdot I_{cm}}{2} = \frac{U_{cm} \cdot I_{ctm} \cdot f_1(\Theta)}{2}$$

$$I_{ctm} = \frac{2 \cdot P_{k3}}{U_{cm} f_1(\Theta)} = \frac{2 \cdot 8}{12 \cdot 0.436} = 3.06 \text{ A}$$

$$I_{cs} = I_{ctm} \cdot f_0(\Theta) \\ = 3.06 \cdot 0.252 = 0.77 \text{ A}$$

$$U_N = U_{cc} + U_{cm} = 2 \cdot U_{cc} = 24 \text{ V} < \underline{U_{cbo}} = 30 \text{ V} \quad \checkmark$$

$$U_M = U_{cc} - U_{cm} \cos \Theta = 7.896 < \underline{U_{CEO}}_{(50\%)} = 20 \text{ V} \quad \checkmark$$

$$I_{ctm} = 3.06 \text{ A} < I_{cmax} = 3.5 \text{ A} \quad \checkmark$$

Ponoviti, pogledati

U_{cbo} !!!

U_{CEO}

I_{cmax}

14.

$$R = 10 \Omega$$


$$L, C_1 = ?$$

$$f_d = 160 \text{ kHz} = \frac{1}{2\pi R C_1} \Rightarrow C_1 = \frac{1}{2\pi f_d R} = \frac{1}{2\pi \cdot 160 \cdot 10^3 \cdot 10} = 99.47 \text{nF}$$

$$f_g = \frac{R}{2\pi L} \Rightarrow L = \frac{R}{2\pi f_g} = \frac{10}{2\pi \cdot 32 \cdot 10^6} = 44.2 \text{nH}$$


	f_d	f_g
C_2	3014Ω	13.4Ω
L	0.04Ω	10Ω

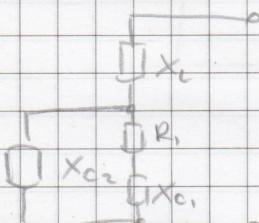C_2 - služi za povećanje opterećnog otpora



$$f_c = 132 \text{ MHz}$$

$$X_{C_1} = 0.012 \Omega \approx 0$$

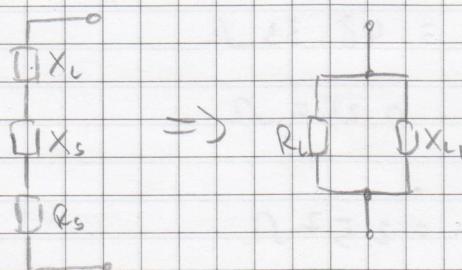

$$f_1 = 132 \text{ MHz}$$

$$X_{C2} = \frac{1}{2\pi f_1 C_2} = 3.65 \Omega$$

$$X_L = 2\pi f_1 L = 36.66 \Omega$$

$$R_s = \frac{R X_{C2}^2}{R^2 + X_{C2}^2} = 1.17 \Omega$$


$$X_s = \frac{R^2 X_{C2}}{R^2 + X_{C2}^2} = 3.22 \Omega$$

$$X_{S1} = X_L - X_s = 36.66 - 3.22 = 33.44 \Omega$$

$$R_u = \frac{X_{S1}^2 + R_s^2}{R_s} = 950.84 \Omega$$

$$X_{L1} = \frac{X_{S1}^2 + R_s^2}{X_{S1}} = 43.48 \Omega$$

bez C_2

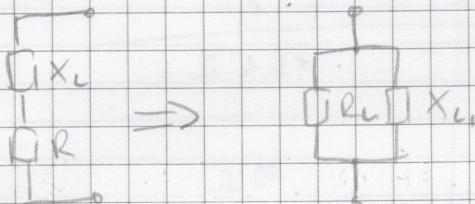

$$R_L = \frac{X_L^2 + R^2}{R} = 144 \Omega$$

$$X_{L1} = \frac{X_L^2 + R^2}{X_L} = 39.59 \Omega$$

$$f_2 = 174 \text{ MHz}$$

$$X_{C2} = \frac{1}{2\pi f_2 C_2} = 2.77 \Omega$$

$$X_L = 2\pi f_2 L = 48.33 \Omega$$

$$R_s = \frac{R X_{C2}^2}{R^2 + X_{C2}^2} = 0.257 \Omega$$

$$X_s = \frac{R^2 X_{C2}}{R^2 + X_{C2}^2} = 2.57 \Omega$$

$$X_{S_1} = X_L - X_S = 45.75 \Omega$$

$$R_L = \frac{R_S^2 + X_{S_1}^2}{R_S} = 8135 \Omega$$

$$X_{L_1} = \frac{R_S^2 + X_{S_1}^2}{X_S} =$$

bbez C_2 za f_2

$$R_L = \frac{R^2 + X_C^2}{R}$$

$$X_{L_1} = \frac{R^2 + X_C^2}{X_C} =$$

-neček. doč. uva
test (sačin za
pružir už predavanje)

(15)

II - čitverogon

$$X_L = \frac{R}{1+Q^2} \left(Q + \sqrt{\frac{r_a}{R}} (1+Q^2) - 1 \right)$$

Q^2 zákonarivo !

$$\frac{r_a}{R} = \frac{8}{50} = \frac{4}{25} \quad Q > 10$$

$$X_L \approx \frac{R}{Q^2} (Q + \sqrt{\frac{r_a}{R}} Q^2) = \frac{R}{Q} (1 + \sqrt{\frac{r_a}{R}})$$

$$Q \approx \frac{R}{X_L} (1 + \sqrt{\frac{r_a}{R}}) \approx \frac{70}{X_L}$$

(a)

$$f_d = 980 \text{ kHz}$$

$$X_L' = 2\pi f_d L = 7 \Omega$$

$$Q' = \frac{70}{X_L'} = 10$$

$$X_2' = \frac{r_a}{\sqrt{\frac{r_a}{R} (1+Q'^2)} - 1} = 2.05 \Omega \Rightarrow C_2' = \frac{1}{2\pi f_d X_2'} = 79 \text{ nF}$$

$$X_1' = \frac{R}{Q'} = \frac{50}{10} = 5 \Omega \Rightarrow C_1' = \frac{1}{2\pi f_d X_1'} = 32.5 \text{ nF}$$

$$(b) f_g = 1400 \text{ MHz}$$

$$X_L'' = 10 \Omega \Rightarrow Q'' = 7$$

$$X_1'' = \frac{r_a}{\sqrt{\frac{r_a}{R} (1+Q^2) - 1}} = 3 \Omega \quad C_2'' = 37.6 \text{ nF}$$

$$X_1'' = \frac{R}{Q''} = \frac{50}{7} = 7.14 \Omega \quad C_1'' = 15.91 \text{ nF}$$

$$\begin{aligned} 15.91 &< C_1 < 32.48 \text{ nF} \\ 37.6 &< C_2 < 79.04 \text{ nF} \end{aligned}$$

(16.)

$$f = 3 \text{ MHz}$$

$$X_C = 0.53 \Omega$$

$$X_{C_1} = 471.23 \Omega$$

$$X_C = 10 \Omega$$

$$X_S = 13.26 \Omega$$

$$r_I' = \frac{r_I^2 + X_S^2}{r_I} = 48 \Omega = R_C$$

$$X_S' = \frac{r_I^2 + X_S^2}{X_S} = 14.47 \Omega$$

$$X_o + X_p + X_S' = X_L$$

$$C_S = \frac{1}{2\pi f X_S} = 3.66 \text{ nF}$$

$$X_L = X_{Cuk} = \frac{1}{\omega C_{Cuk}} \Rightarrow C_{Cuk} = \frac{1}{\omega X_L} = 5.3 \text{ nF}$$

$$C_P = C_{Cuk} - C_o - C_S' = 5.3 - 0.03 - 3.66 = 1.6 \text{ nF}$$

$$P_k = \frac{(U_{CC} - U_b)^2}{2 R_C} = \frac{(9 - 2)^2}{2 \cdot 148} = 0.51 \text{ W}$$

$$\cos \Theta = \frac{U_n - U_{BB}}{U_{beam}} = \frac{0.6 - 0}{2.02} = 0.297 \quad U_n = 0.6V$$

$$U_{BB} = 0$$

$$\Rightarrow \Theta = 72.72^\circ$$

$$P_{uz2} = \frac{U_{beam}}{2 r_i} \Rightarrow U_{beam} = \sqrt{2 P_{uz2} r_i} = \sqrt{2 \cdot 0.51 \cdot 4} = 2.02 \text{ V}$$