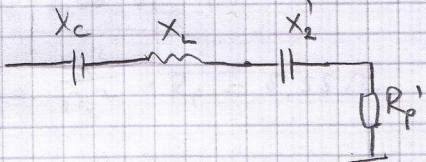


3. MI

23



$$U_S = 1,2 \text{ V}$$

$$X_1 = \frac{1}{2\pi f C_1} = 102 \text{ } \Omega$$

$$X_2 = \frac{1}{2\pi f C_2} = 26,5 \text{ } \Omega$$

$$R_p' = \frac{R_p X_2^2}{R_p^2 + X_2^2} = 11 \text{ } \Omega$$

$$X_2' = \frac{R_p^2 \cdot X_2}{R_p^2 + X_2^2} = 20,7 \text{ } \Omega$$

$$X_L = X_1 + X_2' = 122,7 \text{ } \Omega \Rightarrow L = \frac{X_L}{2\pi f} = 32,55 \mu\text{H}$$

$$U_{CCM} = \frac{2}{\pi} (U_{CC} - 2U_S) = 9,93 \text{ V}$$

$$P_K = \frac{U_{CCM}^2}{2R_p'} = \frac{9,93^2}{2 \cdot 11} = 9,48 \text{ W}$$

$$I_{CC} = \frac{2}{\pi R_p} (U_{CC} - 2U_S) = 287 \text{ mA}$$

$$P_{CC} = U_{CC} I_{CC} = 5,17 \text{ W}$$

$$\eta = \frac{P_K}{P_{CC}} = 86,6 \Rightarrow$$

$$P_K = \frac{U_{CCM}^2}{2R_p}$$

$$U_{CCM} = \sqrt{2P_K \cdot R_p} = 21,2 \text{ V}$$

$$P_C = P_{CC} - P_K = 0,69 \text{ W}$$

$$P_{C1} = P_{C2} = \frac{P_C}{2} = 0,35 \text{ W}$$

$$(24) \quad P_K = \frac{(U_{cc} - U_s)^2}{2R_c} \quad U_{cm} = U_{cc} - U_s$$

$$R_c = \frac{U_{cm}^2}{2P_K} = 84,5 \Omega$$

$$U_{cm\max} = U_{cc} + U_{cm} = 28 \text{ V}$$

$$I_{cm} = \sqrt{\frac{2P_K}{R_c}} = 0,154 \text{ A}$$

$$I_{cm} = I_{ctm} \cdot f_0(\Theta) \Rightarrow I_{ctm} = \frac{I_{cm}}{f_0(\Theta)} = 0,308 \text{ A}$$

$$P_{cc} = U_{cc} \cdot I_{cs} = U_{cc} \cdot I_{ctm} \cdot f_0(\Theta) = 2,31 \text{ W}$$

$$\eta = \frac{P_K}{P_{cc}} = 43,3 \%$$

$$25) P_k = 100 \text{ W}$$

$$R_p = 50 \Omega$$

$$m_1 : m_3 = 1 : 3$$

$$U_s = 2,65 \text{ V}$$

$$R_c = \frac{n_1^2}{n_2^2} \cdot R_p = 5,55 \Omega$$

$$P_k = \frac{U_{cm}^2}{2R_c} \Rightarrow U_{cm} = \sqrt{2P_k R_c} = 33,33 \text{ V}$$

$$U_{cc} = U_{cm} + U_s = 36 \text{ V}$$

$$U_{cm\max} = U_{cc} + U_{cm} = 69,33 \text{ V}$$

$$I_{cm} = \sqrt{\frac{2P_k}{R_c}} = 6 \text{ A}$$

$$I_{ctm} = \frac{I_{cm}}{f_1(\infty)} = \frac{6}{9,5} = 12 \text{ A}$$

$$P_{cc} = U_{cc} \cdot I_{cs} = U_{cc} I_{ctm} \cdot f_0(0) = 36 \cdot 12 \cdot 0,318$$

$$P_{cc} = 137,37 \text{ W}$$

$$\eta = \frac{P_k}{P_{cc}} = 72,8 \%$$

(26)

$$P_K = 300 \text{ W}$$

$$f = 13,56 \text{ MHz}$$

$$U_{DD} = 75 \text{ V}$$

$$r_{DS(w)} = 0,085 \Omega$$

$$C_0 = 500 \text{ pF}$$

$$P_K = \frac{2}{\pi^2} \frac{R_p U_{DD}^2}{(R_p + r_{DS(w)})^2} \Rightarrow R_p = \frac{2}{\pi^2} \frac{U_{DD}^2}{P_K} = 3,8 \Omega$$

$$I_{DTRM} = \frac{2U_{DD}}{\pi R_p} = 12,56 \text{ A}$$

$$P_{d1} = P_{d2} = P_d / 2$$

$$P_d = P_{DD} - P_K + P_{d+} \rightarrow \text{gubitai na dotokuu (2bog } C_0)$$

$$P_d = \frac{2}{\pi^2} \frac{U_{DD}^2}{(R_p + r_{DS(w)})^2} + 4C_0 U_{DD}^2 \cdot f$$

$$P_d = 158,97 \text{ W}$$

$$P_{d1} = P_{d2} = 79,48 \text{ W}$$

$$\eta = \frac{P_K}{P_{DD}} = \frac{P_K}{P_K + P_d} = 65,36 \%$$

$$f' = 1,3 \text{ MHz}$$

$$P_d' = 21 \text{ W}$$

$$\eta' = \frac{P_K}{P_K + P_d'} = 93,45 \%$$

27.

$$P_k = 28,6 \text{ dBm} = 0,724 \text{ W}$$

$$G = 9 \text{ dB} = 7,94$$

$$\text{PAE} = 75,6 \text{ \%}$$

$$\text{PAE} = \frac{P_p - P_{uc}}{P_0} = \frac{P_k}{P_{cc}} \left(1 - \frac{1}{G}\right)$$

$$P_{cc} = \frac{P_k}{\text{PAE}} \left(1 - \frac{1}{G}\right) = \frac{0,724}{0,756} \left(1 - \frac{1}{7,94}\right) = 0,837 \text{ W}$$

$$P_{uz} = P_k - G = 28,6 - 9 = 19,6 \text{ dBm} = 0,812 \text{ mW}$$

$$\eta = \frac{P_k}{P_{cc}} = \frac{0,724}{0,837} = 86,5 \text{ \%}$$

28

$$P_K = \frac{8}{\pi^2} \frac{R_p \cdot U_{DD}^2}{(R_p + (Z_{DS(w)})^2)} \rightarrow \text{nije zadano} \Rightarrow = 0$$

$$P_K \approx \frac{8}{\pi^2} \frac{U_{DD}^2}{R_p}$$

$$U_{DD} = \sqrt{\frac{\pi^2}{8} P_K R_p} = 78,53 \text{ V}$$

$$U_{d,m} = 2U_{DD} = 157 \text{ V} \geq U_{loss} -$$

$$I_{d,m} = I_{R,m} = \frac{4U_{DD}}{\pi R_p} = 2 \text{ A} < I_{D,max} \checkmark$$

(23) Klasa D \rightarrow oba pojedyncze fale how sklepka

$$P_c = \frac{1}{2} I_{cc}^2 \cdot R_p = (U_{cc} - U_s) \cdot I_{cc}$$

$$I_{cc} = \frac{P_c}{U_{cc} - U_s} = 1,25 \text{ A}$$

$$I_{cc} = 0,577 \frac{U_{cc} - U_s}{R_p} \Rightarrow R_p = 0,577 \frac{U_{cc} - U_s}{I_{cc}} = 7,38 \text{ } \Omega$$


$$\frac{1}{X_C1} = \omega C_1 = \frac{0,184}{R_p} \Rightarrow C_1 = \frac{0,184}{2\pi f R_p} = 56,6 \text{ pF}$$

$$f' = 2f = 140 \text{ MHz}$$

$$f = 70 \text{ MHz}$$

$$X_C2 = X_L2$$

$$X_C2 = 4X_L2$$

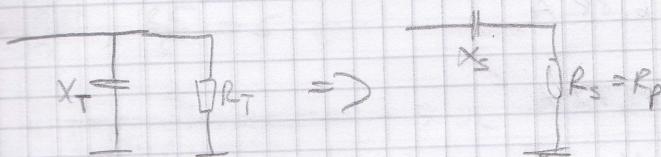

$$X_T = -X_C2 + X_C1 = -3X_L2$$

$$X_S = \frac{R_T^2 \cdot X_T}{R_T^2 + X_T^2}$$

$$R_p = \frac{R_T X_T^2}{R_T^2 + X_T^2}$$

$$X_T^2 \cdot R_S + R_p R_T^2 = R_T X_T^2 \Rightarrow X_T = \sqrt{\frac{R_p \cdot R_T^2}{R_T + R_p}} = 20,8 \text{ } \Omega$$

$$|X_T| = 13X_L2 \Rightarrow X_L = 6,93 \text{ } \Omega \Rightarrow L_2 = 15,77 \text{ mH}$$

$$|X_C2| = 14X_L2 = 27,74 \Rightarrow C_2 = 82 \text{ pF}$$

$$X_S = 1,73 \text{ } \Omega$$

$$X_C1 = \frac{1}{X_L X_S} \parallel R_p \Rightarrow \omega L \cdot \frac{1}{\omega C_2} = 1,152 R_p$$

$$L = \frac{1,152 R_p + X_S}{\omega} = 59,64 \text{ mH}$$

$$P_c = U_s \cdot I_{cc} = 2,5 \text{ W}$$

$$\eta = \frac{P_c}{P_c + P_{diss}} = 88,89 \%$$

$$I_{ctm} = 2,862 I_{cc} = 3,577 \text{ A}$$

$$U_{cmax} = U_s + 1,134 \cdot \pi (U_{cc} - U_s) = 59 \text{ V}$$

(30)

$$\gamma = \frac{R_p}{R_p + 1,365 \cdot f_{DS}(w)} \Rightarrow f_{DS}(w) = \frac{\frac{R_p}{\gamma} - R_p}{1,365} = 0,2 \text{ Hz}$$

$$wC_1 = \frac{0,184}{R_p} \rightarrow C_1 = \frac{0,184}{2\pi f R_p} = 0,697 \mu F$$

$$C_p = C_1 - C_{DSS} = 572 \text{ pF}$$

$$wL_s = \frac{1}{\omega C_1} = 1,152 R_p \Rightarrow L_s = \frac{1,152 R_p}{\omega} = 10 \text{ mH}$$

$$I_{DD} = 0,577 \frac{U_{DD}}{R_p}$$

$$P_K = 0,577 \frac{R_p U_{DD}^2}{(R_p + f_{DS}(w))^2} \Rightarrow U_{DD} = \sqrt{\frac{P_K (R_p + f_{DS}(w))^2}{0,577 R_p}} \approx 18,5 \text{ V}$$

$$I_{DD} = 0,577 \frac{U_{DD}}{R_p} = 6,88 \text{ A}$$


$$I_{DTM} = 2,862 I_{DD} = 19,71 \text{ A}$$

$$U_{Dmax} = 1,13 C_1 \cdot \pi \frac{U_{DD} \cdot R_p}{R_p + f_{DS}(w)} = 58,37 \text{ V}$$

$$\textcircled{1} \quad P_c = \frac{8}{\pi^2 R_c} (U_{cc} - U_s)^2$$

$$R_c = \frac{8}{\pi^2 R_c} (U_{cc} - U_s)^2 \approx 100 \Omega$$
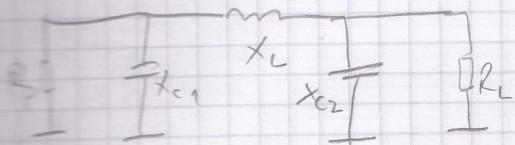
$$R_c = \frac{Z_0^2}{R_p} \Rightarrow R_p = \frac{Z_0^2}{R_c} = 25 \Omega$$



I CONVERGENCE

$$Y_{cc} = 5 \Omega$$

$$Q = \frac{R_p}{X_{C1}} = \frac{25}{5} = 5$$

$$X_{C2} = \frac{R_c}{\sqrt{\frac{R_c}{R_p} (1+Q^2) - 1}} = 7 \Omega \Rightarrow C_2 = 2,52 \text{ nF}$$

$$X_L = \frac{R_p}{1+Q^2} \left(Q + \sqrt{\frac{R_c}{R_p} (1+Q^2) - 1} \right) = 11,67 \Omega \Rightarrow L = 206 \text{ nH}$$

$$U_{ceVmin} = 2(U_{cc} - U_s) = 62 \text{ V}$$

$$I_{cm} = 2 I_{1m} = \frac{8}{\pi R_c} (U_{cc} - U_s) = 0,764 \text{ A}$$

$$\eta = \frac{P_c}{P_K + P_d} \quad P_d = P_c + P_{at}$$

$$P_d = \frac{8}{\pi^2 R_c} (U_{cc} - U_s) U_s + 2 C_0 f (U_{cc} - U_s)^2 = 0,486 + 0,324 = 0,81 \text{ W}$$

$$\eta = \frac{73}{73 + 0,81} = 90\%$$

$$P_k = \frac{8U_{DD}^2}{\pi^2} \cdot \frac{R_d}{(R_d + 2f_{DSS}(u))^2} = 6,859 \text{ W}$$

$$U_{dmax} = 2U_{DD} = 64 \text{ V}$$

$$I_{dtm} = 2I_{dmax} = \frac{8U_{DD}}{\pi} \cdot \frac{1}{R_d + 2f_{DSS}(u)} = 0,74 \text{ A}$$

$$\eta = \frac{P_{kern}}{P_k + P_d}$$

$$P_d = 0,686 + 0,368 = 1,05 \text{ W}$$

$$= P_D + P_{D+} = \frac{8U_{DD}^2}{\pi^2} \cdot \frac{2f_{DSS}(u)}{(R_d + 2f_{DSS}(u))^2} + 2C_{DSS} f U_{DD}^2$$

$$\eta = \frac{6,86}{6,86 + 1,05} = 86,6 \%$$