

# TIPOVI FILTARA

## 1) NISKOPROPUSNI (NP)

opća prijenosna karakteristika NP 1. reda

$$H(s) = K \cdot \frac{\omega_0}{s + \omega_0}$$

- II - II - NP 2. reda

$$H(s) = K \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

$\omega_p$  - frekv. polova

$$\omega_{p,1,2} = \sqrt{\omega_p^2 + j^2 Q_p}$$

$Q_p$  - faktor kvalitete

$$Q_p = -\frac{\omega_p}{2\sqrt{\omega_p}}$$

## 2) VISOKOPROPUSNI FILTAR (VP)

VP 1. reda,

$$H(s) = \frac{K \cdot s}{s + \omega_0}$$

$$Q_p = -\frac{\omega_p}{2\sqrt{\omega_p}}$$

2. reda

$$H(s) = K \frac{s^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

### 3. POJASNI PROPOST

$$H(s) = \frac{s - \frac{\omega_p}{Q_p}}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

$$\omega_{g,d} = \omega_p \sqrt{1 + \frac{1}{4Q_p^2}} = \frac{\omega_p}{2Q_p}$$

$$B = \omega_g - \omega_d = \frac{\omega_p}{Q_p}$$

$$\omega_p^2 = \omega_d \omega_p$$

$\omega_p = \omega_c \rightarrow$  centralna freku. filtra

$Q \geq 10 \rightarrow$  uski pojas

$$\omega_{g,d} \approx \omega_p \pm \frac{\omega_p}{2Q_p} = \omega_p \pm \frac{1}{2} B$$


### 4. POJASNA ZRANA

$$H(s) = \frac{s^2 + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

# ČETVEROPOLI

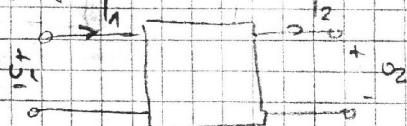1) STRUJNE JEDNADŽBE 4-POLA  $\Rightarrow$  Y - parametri

$$\begin{cases} I_1 = y_{11}U_1 - y_{12}U_2 \\ I_2 = y_{21}U_1 - y_{22}U_2 \end{cases}$$



-ako je  $I_2$  u drugom smjeru

$$\begin{array}{|c|c|} \hline y_{11} = \frac{I_1}{U_1} & y_{21} = \frac{I_2}{U_1} \\ \hline U_2=0 & U_2=0 \\ \hline \end{array}$$

$$y_{12} = \frac{I_1}{U_2} \quad y_{22} = -\frac{I_2}{U_2}$$

$$I_1 = y_{11}U_1 + y_{12}U_2$$

$$I_2 = y_{21}U_1 + y_{22}U_2$$

-ako je 4-pol recipročan  $\boxed{y_{12} = y_{21}}$

$$[y] = \begin{bmatrix} y_{11} & -y_{12} \\ y_{21} & -y_{22} \end{bmatrix}$$

2) NAPONSKIE JEDNADŽBE 4-POLA  $\Rightarrow$  Z - parametri

$$U_1 = I_1 Z_{11} - I_2 Z_{12}$$

$$U_2 = I_1 Z_{21} - I_2 Z_{22}$$

$$Z_{21} = Z_{12}$$

ugjet recipročnosti

$$[z] = \begin{bmatrix} z_{11} & -z_{12} \\ z_{21} & -z_{22} \end{bmatrix}$$

$$[z] = [y]^{-1}$$

$$z_{11} = \frac{U_1}{I_1} \Big|_{I_2=0}$$

$$z_{12} = -\frac{U_1}{I_2} \Big|_{I_1=0}$$

$$z_{21} = \frac{U_2}{I_1} \Big|_{I_2=0}$$

$$z_{22} = -\frac{U_2}{I_2} \Big|_{I_1=0}$$

3) PRIJENOSNE JEDNADŽBE  $\Rightarrow$  a - parametri

$$U_1 = AU_2 + BI_2$$

$$I_1 = CU_2 + DI_2$$

$$[a] = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$A = \frac{U_1}{U_2} \Big|_{I_2=0}$$

$$C = \frac{I_1}{U_2} \Big|_{I_2=0}$$

$$B = \frac{I_1}{U_2} \Big|_{U_2=0}$$

$$D = \frac{I_1}{U_2} \Big|_{U_2=0}$$

$$\text{uvjet recipročnosti: } AD - BC = 1$$

$$\text{prijevrat } U_2 + I_2 \rightarrow U_1 + I_1$$

pa je

$$U_2 = D U_1 - B I_1$$

$$-I_2 = C U_1 - A I_1$$

(4) HIBRIDNE JEDNADŽBE  $\Rightarrow$  h parametri

$$\boxed{\begin{aligned} U_1 &= h_{11} I_1 + h_{12} U_2 \\ I_2 &= h_{21} I_1 + h_{22} U_2 \end{aligned}}$$

$$[h] = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$


- ako imamo  $U_1$  i  $I_2 \Rightarrow U_2 = ?$ ;  $I_1 = ?$

$$\boxed{\begin{aligned} I_1 &= g_{11} U_1 + g_{12} I_2 \\ U_2 &= g_{21} U_1 + g_{22} I_2 \end{aligned}}$$

hibridne g jeckn.

PRIJENOŠNE FUNKCIJE z-parametri

- prijenosna funkcija struje

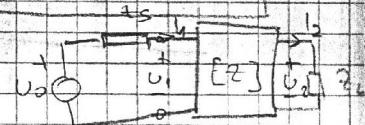

$$H_i(s) = \frac{I_2}{I_1} = \frac{z_{21}}{z_L + z_{22}}$$

- naponska prij.  $H_U(s) = \frac{U_2}{U_1} = \frac{z_L z_{21}}{z_{11}(z_{22} + z_L) - z_{12} z_{21}} = \frac{z_L z_{21}}{z_2 + z_{11} z_L}$

$$H_u(s) = \frac{U_2}{U_1} = \frac{z_L z_{21}}{(z_{11} + z_L)(z_{22} + z_L) - z_{12} z_{21}}$$

$$\Delta z = z_{11} z_{22} - z_{12} z_L$$

PRIJENOŠNE FUNKCIJE y-parametri

$$H_u(s) = \frac{y_{21}}{Y_L + y_{22}}$$

- ista slika

$$H_i = \frac{Y_L y_{21}}{y_{11}(y_{22} + Y_L) - y_{12} y_{21}}$$

# PRJEVODSNE FJE AČ parametrima


$$H_1(s) = \frac{U_1}{U_1} = \frac{Z_L}{AZ_L + B}$$

iste skica


$$H_1 = \frac{I_2}{I_1} = \frac{1}{CZ_L + D}$$

$$H(s) = \frac{U_2}{U_1} = \frac{Z_L}{AZ_L + B + Z_s(CZ_L + D)}$$
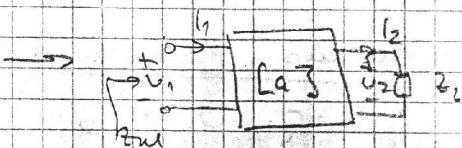
$$Z_{ul_1} = \frac{U_1}{I_1} = \frac{AZ_2 + B}{CZ_2 + D}$$


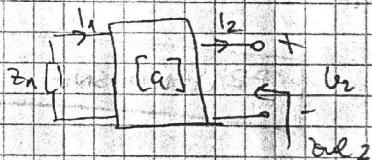
$$Z_{ul_2} = \frac{U_2}{I_2} = \frac{DZ_1 + B}{CZ_1 + A}$$




$$Z_{ul_1} = Z_{11} - \frac{Z_{12}}{Z_2 + Z_{22}}$$

$$Z_{ul_2} = -\frac{U_2}{I_2} = Z_{22} - \frac{Z_{12}Z_{21}}{Z_{11} + Z_1}$$

$$Y_{ul_1} = Y_{11} = \frac{Y_{12}Y_{21}}{Y_2 + Y_{22}}$$
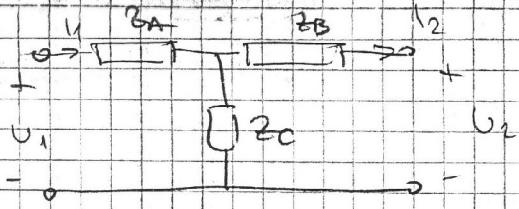
$$Y_{ul_2} = Y_{22} - \frac{Y_{12}Y_{21}}{Y_1 + Y_{22}}$$



$$Z_A = Z_{11} - Z_{12}$$

$$Z_B = Z_{22} - Z_{12}$$

$$Z_C = Z_{12} = Z_{21}$$

$\Rightarrow$  vrijedi za recipročni u-poli


$\rightarrow$  tako se radi o nereciprocnom u-polu

$$Z_{12} \neq Z_{21}$$


$$U_1 = I_1 Z_{11} - I_2 Z_{12}$$

$$U_2 = I_1 Z_{12} - (Z_{22} + I_1 (Z_{21} - Z_{12}))$$

(nap. troug)

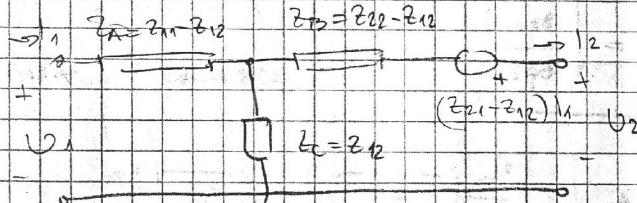

### EKVIVALENTNI u-POL U II-SPOJU

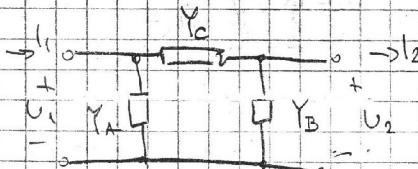


- za recipročni u-poli

$$Y_A = Y_{11} - Y_{12}$$

$$Y_B = Y_{22} - Y_{12}$$

$$Y_C = Y_{12} = Y_{21}$$

- nereciprocni (četverpolni)

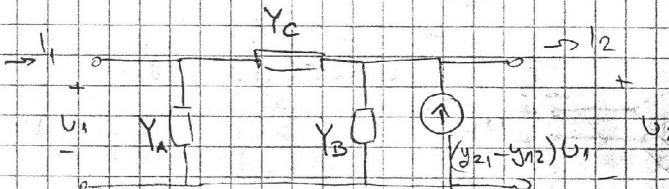


$$I_1 = Y_{11} U_1 - Y_{12} U_2$$

$$I_2 = Y_{12} U_1 - Y_{22} U_2 + (Y_{21} - Y_{12}) U_1$$

$$= h_{21} U_1$$

itvor

- also mijedi

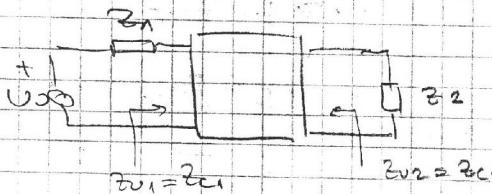

$$| \quad Z_{01} = Z_0 \quad ; \quad Z_02 = Z_0 \quad \Rightarrow \text{prilagoden je rezistor u par,}$$

$$Z_{C1} = \sqrt{\frac{Z_{p1} Z_{01}}{Y_{11}}} = \sqrt{\frac{Z_{11}}{Y_{11}}}$$

$Z_{p1}$  - na pravcu  $\rightarrow$  s vlasta sa 1,1


$$Z_{C2} = \sqrt{\frac{Z_{p2} Z_{02}}{Y_{22}}} = \sqrt{\frac{Z_{22}}{Y_{22}}}$$

$Z_{p2}$  - na kretanju  $\rightarrow$  s 2,2

$$| \quad t_h(g) = \sqrt{\frac{Z_{01}}{Z_{p1}}} = \sqrt{\frac{Z_{02}}{Z_{p2}}}$$


## POVEZIVANJE $h$ -POLA

### (1) SERIJA

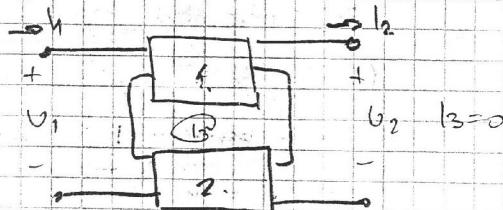


$$\{Z\} = \{Z\} + \{Z''\}$$

### (2) PARALELA

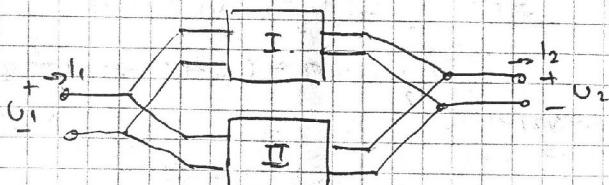


$$\{y\} = \{y'\} + \{y''\}$$

③ SERIJSKO - PARALELNI

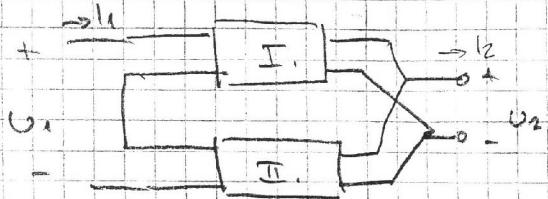


$$[h] = [h'] + [h'']$$

④ PARALELNO - SERIJSKI

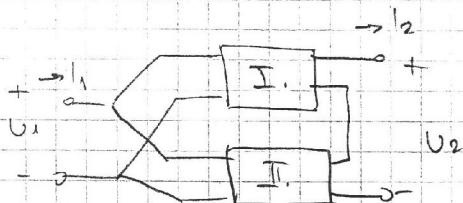

$$[g] = [g'] + [g'']$$

⑤ LANAC (VASKADA)

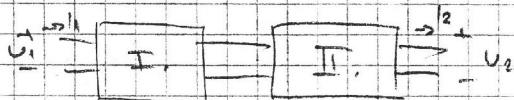

$$[a] = [a'] \cdot [a'']$$

SIMETRIČNI

ČETVEROPOLI

$y$ -parametri: 
$$\boxed{y_{11} = y_{22}}$$

$\beta$ -parametri: 
$$\boxed{\beta_{11} = \beta_{22}}$$

$a$ -parametri: 
$$\boxed{A = 0}$$

homogeni  $h$ : 
$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = -1$$

homogeni  $g$ : 
$$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} = 1$$

## LINIJE

$$ch jx = \cos k$$

$$sh jx = j \sin k$$

$\rightarrow$  faktor projekcije (propagacije)

$$S^e = \sqrt{(R+jL)(G+jC)}$$

$$Z_0 = \sqrt{\frac{R+jL}{G+jC}}$$

$\rightarrow$  karakter. Impedanca

$\rightarrow$  koef. refleksije na izlazu

$$\Gamma_2 = \frac{Z_2 - Z_0}{Z_2 + Z_0}$$

-11- na ulazu

$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

linija  $\Rightarrow$  simetričan 4-pol

$$f = \alpha + j\beta$$

$\rightarrow$  -11- faktor faze

$$N = \frac{w}{\beta}$$

$$\lambda = \frac{P}{\beta}$$

$$\lambda = \frac{2\pi}{\beta}$$

## 1. LINIJA BEZ GUBITAKA

$$R=0, G=0$$

$$Z_0 = \sqrt{\frac{L}{C}} = \text{kons.}$$

$$S^e = j\sqrt{LC}$$

$\rightarrow$  sinusna rotacija

$$S^e = j\omega LC = j\beta$$

## 2. LINIJA BEZ DISTORSIJE

$$\frac{R}{L} = \frac{G}{C} \Rightarrow \frac{R}{G} = \frac{L}{C} \Rightarrow RC = GL$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$g = \sqrt{RG} + j\sqrt{LC}$$

zadava podatka

$$g = \sqrt{RC} + j\omega\sqrt{LC}$$

$$L = R \sqrt{\frac{C}{L}} = \sqrt{RG} \quad \beta = \omega\sqrt{LC} \quad U(x) = U(0) \cdot e^{-\frac{x}{\lambda}} \cdot e^{-j\frac{\beta x}{2}}$$

$$f = \sqrt{RG} + j\sqrt{LC}$$

λ = β/β

## 3. RC-LINIJA

$$G=0 \quad L=0$$

$$Z_0 = \sqrt{\frac{R}{GC}}$$

$$g = \sqrt{\frac{\omega RC}{2}} + j\sqrt{\frac{\omega RC}{2}}$$

## 4. LINIJA S MALIM SUBICIMA

$$\omega L \gg R \quad \omega C \gg G$$

$$U(x) = U(0) e^{-\frac{R}{2}x}$$

$$\rightarrow \text{akao } j\omega C \quad Z_2 = Z_0 \Rightarrow Z_{UL} = Z_0 \rightarrow \text{prilagođenje!}$$

- linija zadržavajuća za  $Z_0$  → kao beskonačno dug (nema refleksije)

$$I(0)=0$$

$$\frac{d}{dx} I(x) = 0$$

$$U(0)=0$$

$$U(x) = U(0) \operatorname{ch}(gx) - Z_0 I(0) g \operatorname{sh}(gx)$$

$$I(x) = -\frac{U(0)}{Z_0} g \operatorname{sh}(gx) + I(0) \operatorname{ch}(gx)$$

$$-Z_0 \quad x=l$$

$$U(0) = U(l) \operatorname{ch}(gl) + Z_0 I(l) g \operatorname{sh}(gl)$$

$$I(0) = \frac{U(l)}{Z_0} g \operatorname{sh}(gl) + I(l) \operatorname{ch}(gl)$$

$$Z_{UL} = \frac{Z_0 \operatorname{ch}(gl) + Z_0 g I(l) \operatorname{sh}(gl)}{g \operatorname{sh}(gl) + \operatorname{ch}(gl)}$$

$$Z_{UL} = \frac{U(l) \operatorname{ch}(gl) + I(l) Z_0 g \operatorname{sh}(gl)}{I(l) g \operatorname{sh}(gl) + I(l) \operatorname{ch}(gl)}$$

$$Z_{UL} = \frac{U(l) \operatorname{ch}(gl) + I(l) Z_0 g \operatorname{sh}(gl)}{I(l) g \operatorname{sh}(gl) + I(l) \operatorname{ch}(gl)}$$

$$Z_2 = Z_0 \rightarrow Z_{UL} = Z_0$$

prilagođenje