

(3) $u_1 = 8 \sin(\omega t) \rightarrow U_1 = \frac{8}{\sqrt{2}}$
 $u_2 = 6 \sin(\omega t + 90^\circ) \rightarrow U_2 = \frac{6}{\sqrt{2}} j$


$$|U| = |U_1 + U_2|$$

$$U = \sqrt{\frac{64}{2} + \frac{36}{2}} = \frac{10}{\sqrt{2}} = 7.07 \approx 7V$$

OE

METODA NAPONA ČVOROVA

①

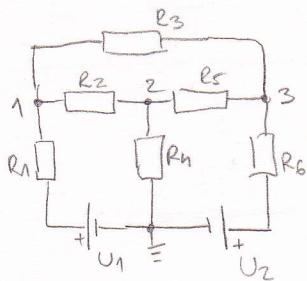


$$\begin{aligned}\varphi_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \varphi_2 \cdot \frac{1}{R_2} - \varphi_3 \cdot \frac{1}{R_3} &= \frac{U_1}{R_1} \\ -\varphi_1 \cdot \frac{1}{R_2} + \varphi_2 \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \varphi_3 \cdot \frac{1}{R_5} &= 0 \\ -\varphi_1 \cdot \frac{1}{R_3} - \varphi_2 \cdot \frac{1}{R_5} + \varphi_3 \cdot \left(\frac{1}{R_3} + \frac{1}{R_5} + \frac{1}{R_6} \right) &= \frac{U_2}{R_6}\end{aligned}$$

! Ako je + izvora obrnut prema čvoru 1 pišemo $+ \frac{U_1}{R_1}$.

Naponski izvor ima otpor 0 \rightarrow ima beskonačnu vodljivost
 strujni izvor ima beskonačan otpor \rightarrow 0 vodljivost


THEVENIN - onjet, osim kada je otpor beskonačan (R_{th}) pa onda koristimo Norton

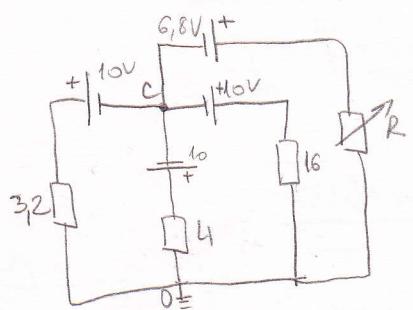② ugasiti izvore i izbaciti traženi otpor



MAX. SNAGA \rightarrow THEVENIN


\Rightarrow

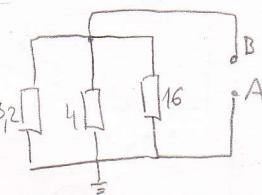


③ izračunati Theveninov otpor

$$\frac{1}{R_T} = \frac{1}{32} + \frac{1}{4} + \frac{1}{16} \Rightarrow R_T = 1.6 \Omega$$

④ vratići izvore i računati U_{ab}

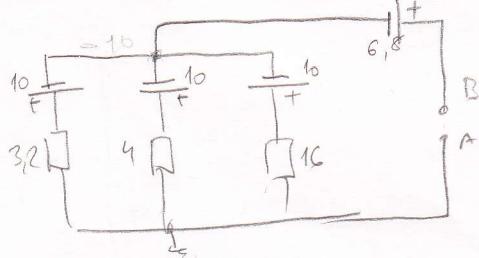

$$U_{ab} = U_T = 1.6V$$

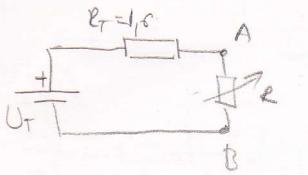

$$\text{MAX SNAGA : } R = R_f \\ R \geq 1.6 \Omega$$

MILMANOVOM METODOM DOBIJEMO U_{OC}

$$U_{OC} = \frac{\frac{10}{32} - \frac{10}{4} - \frac{10}{16}}{\frac{1}{32} + \frac{1}{4} + \frac{1}{16}} = -10V$$

$$U_I = -10 + 6,8 = -3,2V$$

$$I = \frac{U_T}{R+R_f}$$

$$P_{\text{MAX}} = I^2 \cdot R = 16W$$


NORTON

③ nadomjesna shema:



$$I_N = \frac{U_T}{R_f} = \frac{U_T}{R_f}$$

X.1-13

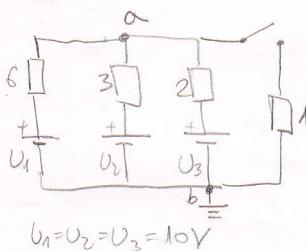

$$a) U_{ab} = \frac{10 \left(\frac{1}{6} + \frac{1}{3} + \frac{1}{2} \right)}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} = 10V \rightarrow \varphi_A = 10V$$

$$U_{ab} = \varphi_a - \varphi_b = \varphi_a$$


$$U_1 = U_2 = U_3 = 10V$$

$$\varphi_A = ?$$

b) skloplja zatvorena

$$U_{ab} = \frac{10 \left(\frac{1}{6} + \frac{1}{3} + \frac{1}{2} \right)}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} = 5V \rightarrow \varphi_A = 5V$$

X.1-7.

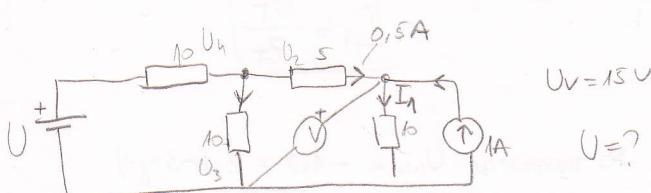

$$I_1 = \frac{15V}{6\Omega} = 1.5A$$

$$U_2 = 5 \cdot 0.5 = 2.5V$$

$$U_3 = 2.5 + 15 = 17.5V$$


$$I_3 = \frac{17.5}{10} = 1.75A$$

$$I_{in} = 1.75 + 0.5 = 2.25A$$

$$U_h = 22.5V$$

$$U = U_3 + U_4$$

$$U = 40V$$

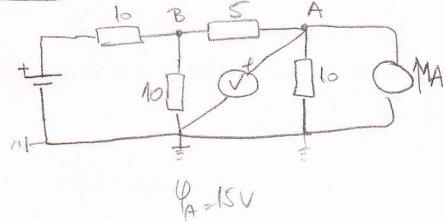2. nacin

$$\Psi_A \left(\frac{1}{6} + \frac{1}{5} \right) - \Psi_B \cdot \frac{1}{5} = 1$$

$$15 \cdot \frac{3}{10} - 1 = \frac{1}{5} \Psi_B$$


$$\frac{7}{2} = \frac{1}{5} \Psi_B$$

$$\underline{\Psi_B = 17,5V}$$

$$\Psi_B \left(\frac{1}{5} + \frac{1}{3} + \frac{1}{10} \right) - \Psi_A \cdot \frac{1}{5} = \frac{U}{10}$$

$$17,5 \cdot \frac{2}{5} - 15 \cdot \frac{1}{5} = \frac{6}{10}$$

$$\underline{\underline{U = 40V}}$$

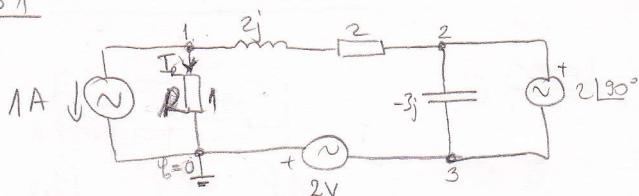ZAD 1

$$I_2 = \frac{U_R}{R} = \frac{\Psi_1 - \Psi_2}{1} = \frac{\Psi_1}{1}$$

$$\underline{\Psi_3 = -2V}$$

$$\Psi_1 \cdot \left(\frac{1}{1} + \frac{1}{2+j2} \right) - \Psi_2 \cdot \frac{1}{2+j2} = -1$$

$$\Psi_2 = -2V + 2jV = -2+j2$$



$$\Psi_1 \left(\frac{3+j2}{2+j2} \cdot \frac{2-j2}{2-j2} \right) - (-2+j2) \cdot \frac{1}{2+j2} \cdot \frac{2-j2}{2-j2} = -1$$

$$I_2 = ?$$

$$\Psi_1 \cdot \left(\frac{5}{4} - \frac{1}{4}j \right) - j = 1$$

$$\Psi_1 = \frac{1+j}{\frac{5}{4} - \frac{1}{4}j}$$

$$\underline{\Psi_1 = \frac{8}{13} + \frac{12}{13}j \quad i = 1,1 \angle 56^\circ}$$

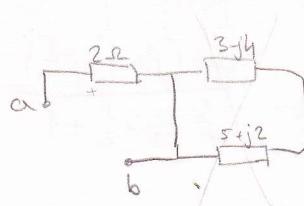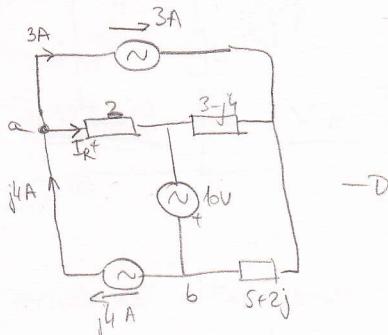ZAD 2

$$Z_N = Z_T = 2\Omega$$

$$I_N = \frac{U_T}{Z_T}$$

$$\text{PO THEVENINU } U_{ab} = -10 + 2 \cdot (-3+j4)$$

$$I_N, I_T = ?$$


$$j4 = I_T + 3$$

$$I_T = -3+j4 A$$

$$U_{ab} = -10 - 6 + j8$$

$$U_{ab} = -16 + j8 V$$
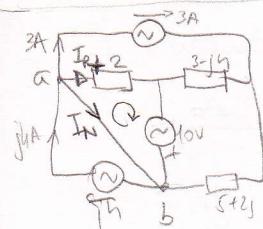
$$\underline{\underline{I_N = \frac{-16+j8}{2} = -8+j4 A}}$$




$$j4 = I_N + I_T + 3$$

$$I_T = 5A$$


$$I_N = j4 - 5 - 3$$

$$\underline{\underline{I_N = -8+j4 A}}$$


ZAD 3

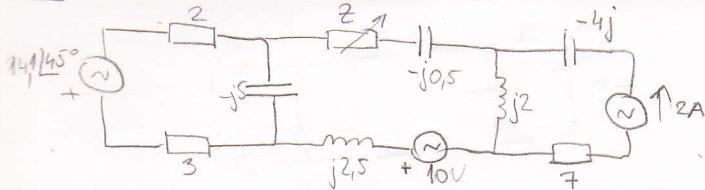

P_{\max} na \underline{Z}

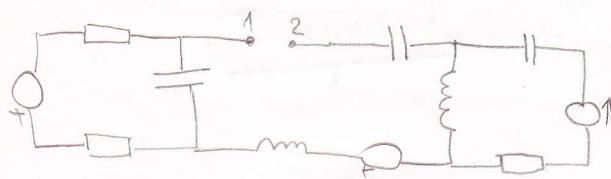


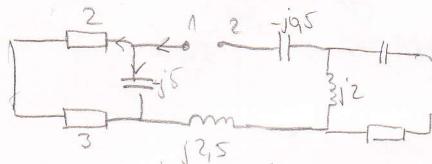2A MAX SNAGU:
 $\underline{Z} = \underline{Z}_T^*$



$$\underline{Z}_T = -j0,5 + j2 + j2,5 + \frac{5(j5)}{5-j5} = j4 + \frac{-j25}{5-j5} \cdot \frac{5(j5)}{5+j5} = \\ = j4 + \frac{75-j75}{50} = j4 + 2,5 - j2,5 = \underline{2,5 + j1,5 \Omega}$$
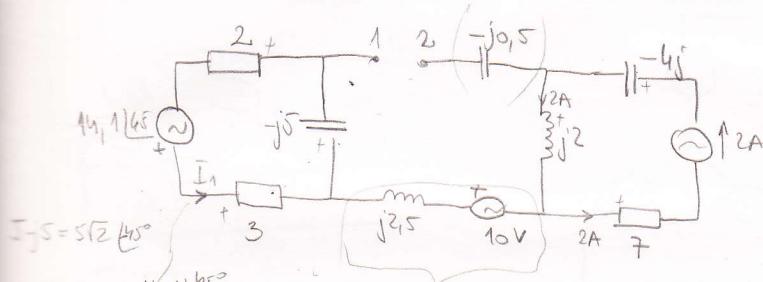
$$\underline{Z} = \underline{2,5 - j1,5 \Omega}$$



$$U_T = U_{12} = -j2 \cdot 2 + 10V - j2 \cdot (-j5)$$


$$\underline{U_T = U_{12}} = -j4 + 10 - 10 = \underline{-j4 V}$$

$$I_1 = \frac{14,145}{5\sqrt{2} \cdot 45^\circ}$$


$$\underline{I_1 = 2,190^\circ A}$$

$$\underline{I_1 = j2A}$$

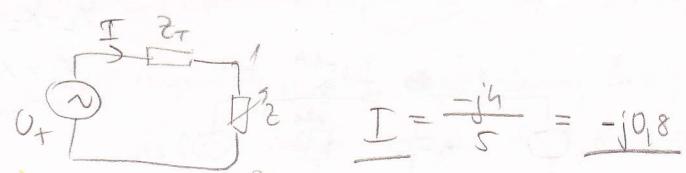tu ne teče struja
ne možemo napraviti krug, jer je gore "rupa"



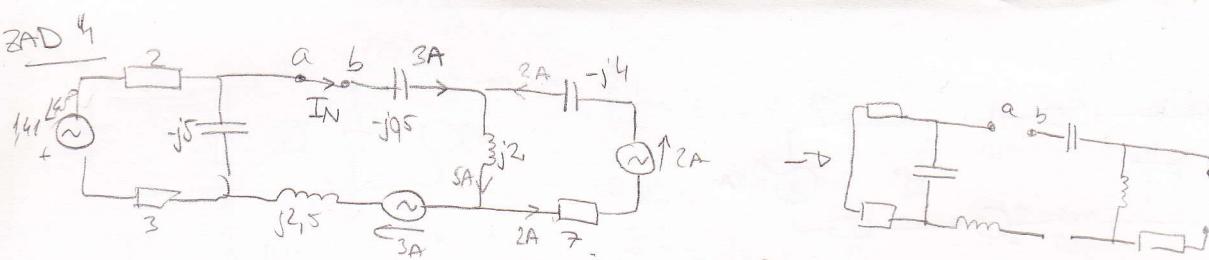
$$\underline{P = I^2 \cdot \operatorname{Re}\{\underline{Z}\}} = 0,64 \cdot 2,5 = \underline{1,6 W}$$



$$Z_N = \infty$$

Koristimo NORTON?

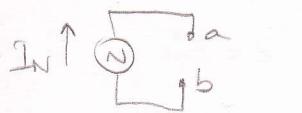


$$\underline{I_N = 3A}$$

što god
stavlji na ab
stojiće ostati
ista

$$Z_T = 0$$

THEVENIN


ZAD 5

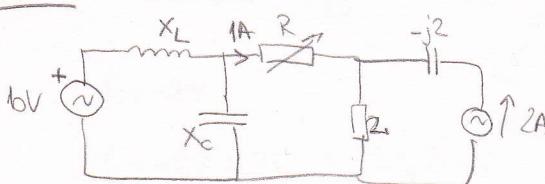

Odrediti struju kroz R koja će biti unjek ista (1A) bez obzira na R!

$$I_N = 1A$$


$$Z_N = \infty$$

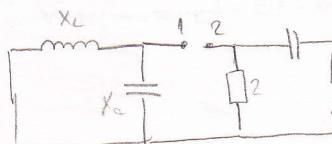

$$Z_N = \frac{jX_L \cdot (-jX_C)}{j(X_L - X_C)} + 2 = \infty$$

$$X_L - X_C = 0$$

$$X_L = X_C$$

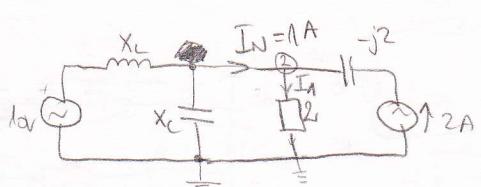

$$\varphi_2 \left(\frac{1}{jX_L} + \frac{1}{-jX_C} + \frac{1}{2} \right) = \frac{10}{X_L} + 2$$

$$I_N + 2 = I_1$$

$$I_1 = \frac{\varphi_2}{2}$$

$$\varphi_2 = \frac{20}{jX_L} + 4$$

$$\underline{I_N = I_1 - 2 = \frac{10}{jX_L} + 2 - 2 = \frac{10}{jX_L}}$$



$$|I_N| = 1 = \frac{b}{X_L}$$

$$\underline{X_L = 10 \Omega}$$


$$\underline{X_C = 10 \Omega}$$

MEDJUINDUKTIVITET

ZAD 1

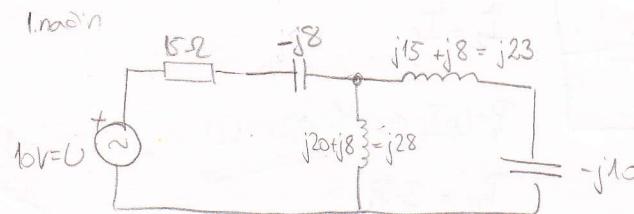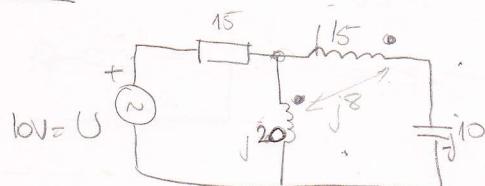

2. način



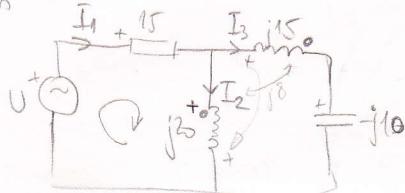


$$I_1 = I_2 + I_3 \quad \text{preslikavamo plus}$$

$$U = 15I_1 - j20I_2 + j8I_3 = 0$$

$$j20I_2 - j8I_3 - j15I_3 + j8I_2 - (-j10)I_3 = 0$$

TROFAZNI

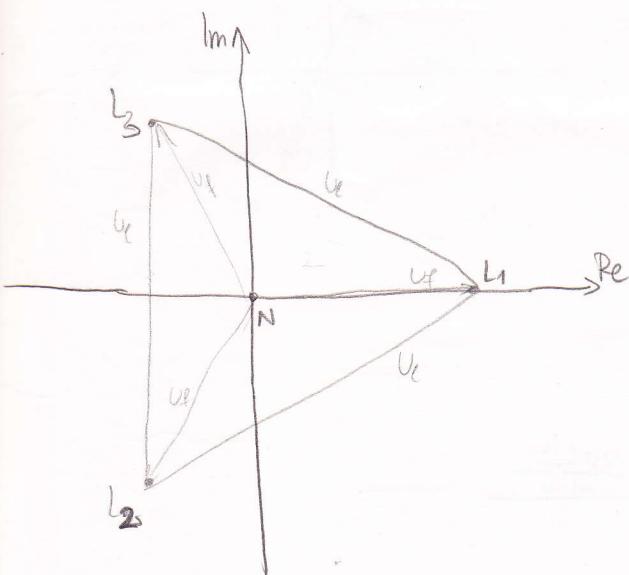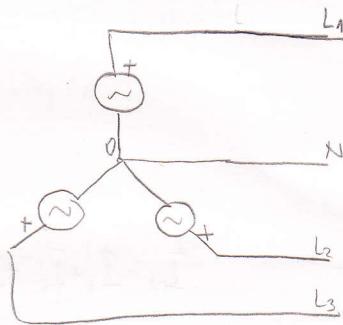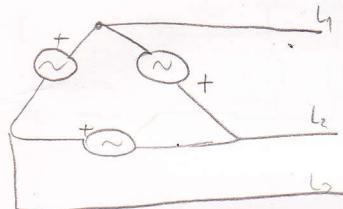


linijski napon \rightarrow napon između L_1, L_2, L_3

fazni napon \rightarrow napon u pojedinoj fazi;
napon između linije i nule

$U_f = 220 / 380 \text{ V}, 50 \text{ Hz} \rightarrow$ gradská mreža

$$U_f / U_L$$

$$U_L = \sqrt{3} U_f$$

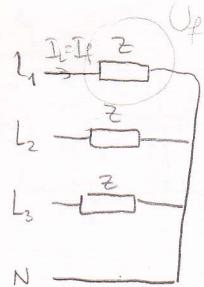

$$U_f = 220V$$


$$U_e = \sqrt{3} U_f$$

$$I_L = I_f$$

$$P_1 = U_f \cdot I_f \cdot \cos \varphi$$

$$P_{0,1} = 3 \cdot P_1$$

TROSILO SPJENO U ZVIJEZDU

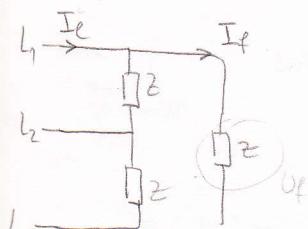

$$U_f = U_e = 380V$$

!!!

$$I_e = \sqrt{3} \cdot I_f$$


TROSILO SPJENO U TRIKUT

$$P_1 = U_f \cdot I_f \cdot \cos \varphi$$

$$P_{\Delta} = 3 P_1$$

ovaj U_f je 380V, a ne 220V

nesimetrično trosilo

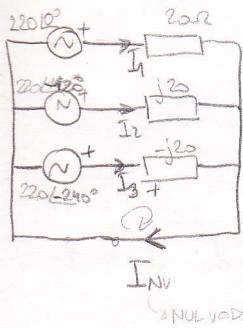

$$I_3 = \frac{220 \angle 120^\circ}{-j20} =$$


$$I_N = I_1 + I_2 + I_3$$

$$I_2 = \frac{220 \angle -120^\circ}{j20} =$$

$$I_N =$$

$$I_1 = \frac{220 \angle 0^\circ}{20} = 11$$

PREKID U NUL VODU

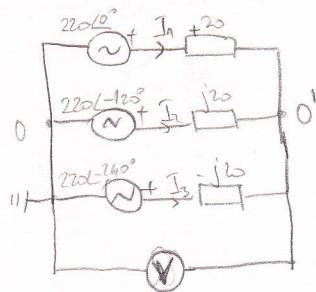


$$U_{00'} = \frac{\frac{220}{20} + \frac{220 \angle 120^\circ}{j20} + \frac{220 \angle 240^\circ}{-j20}}{\frac{1}{20} + \frac{1}{j20} + \frac{1}{-j20}}$$

$$U_V = |U_{00'}| = -161?$$


$$U_{00'} = I_n \cdot 20 - 220 \angle 0^\circ$$

$$I_n = 2,95$$


ZAD 1

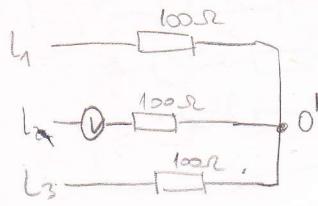

izvor linijskog napona $173V$

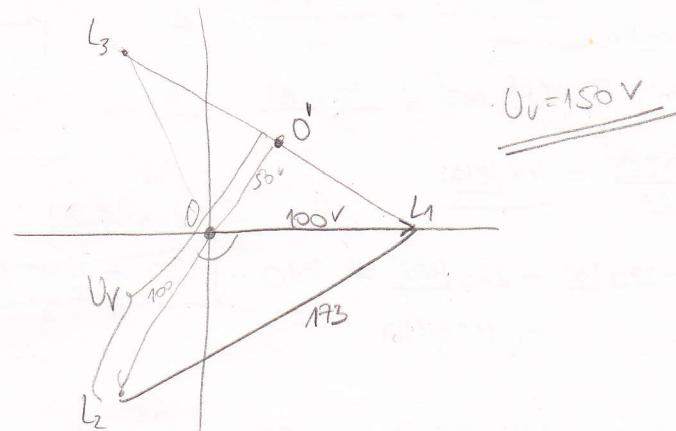


ZAD 2

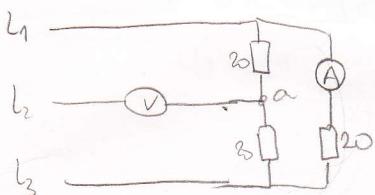

izvor linijskog napona $173V$

$$U_V, I_A = ?$$

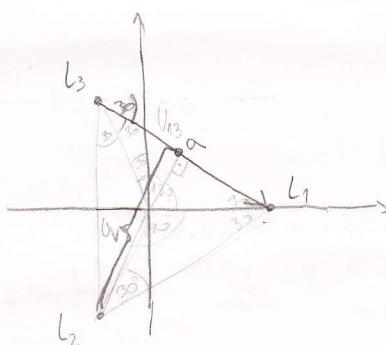


$$U_{13} = 173L-30$$

$$I_A = \frac{173L-30}{20} = 8,65L-30^{\circ} A$$

$$U_V = 150V$$

$$U_V = \sqrt{U_{13}^2 - \left(\frac{U_{13}}{2}\right)^2} = \sqrt{173^2 - \left(\frac{173}{2}\right)^2} = 150V$$

OE

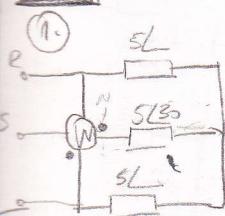

$$U_L = 380 \text{ V} \rightarrow U_f = 220 \text{ V}$$

\rightarrow simetrično trasišlo

$$\text{watmetar mjeri: } P_w = U \cdot I \cdot \cos \varphi$$

$$I = \frac{U_f}{S \cdot \cos \varphi} = \frac{220 / 240}{S \cdot \cos 60^\circ} = 44 / 210$$

$$U_w = U_f - U_T = 220 \angle 0^\circ - 220 \angle 120^\circ = 330 - j190 = 380 \angle 30^\circ \\ -(110 + j190)$$


$$210 + 3 = 240$$

$$\varphi = 120^\circ$$

$$P = 44 \cdot 380 \cdot \cos 120^\circ$$

$$\underline{\underline{P_w = -8,33 \text{ kW}}}$$

IPD

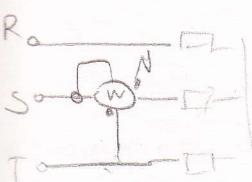

$$b) U = 220 \angle 240^\circ - 220 \angle 120^\circ = -j380 \text{ V} = 380 \angle 90^\circ$$


$$I = 44 \angle 210^\circ$$

$$P = 44 \cdot 380 \cos 60^\circ$$

$$\underline{\underline{P = 8,33 \text{ kW}}}$$

IPD

kondenzatori u zrakjadi

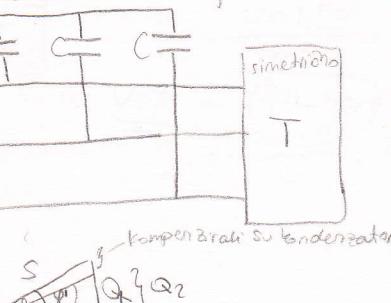

$$U_f = 380 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$P_1 = \frac{3800}{3} = 1166,6 \text{ kW}$$

$$\cos \varphi = 0,6 \rightarrow \varphi = 53,18^\circ$$

$$\cos \varphi' = 0,8 \rightarrow \varphi' = 38,39^\circ$$

Q₁ Q₂

$$\tan \varphi = \frac{Q_1}{P}$$

$$Q_1 = 1555 \text{ VAR}$$

$$Q_2 = P_1 \cdot \tan(38,39^\circ)$$


$$Q_2 = 924 \text{ VAR}$$

$$Q_c = Q_1 - Q_2 = 631$$

$$Q_c = \frac{U_f^2}{X_c} \Rightarrow X_c = \frac{U_f^2}{Q_c} = 76,7 \Omega$$

$$X_c = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{2\pi f X_c} = 4,5 \mu\text{F}$$

1-13

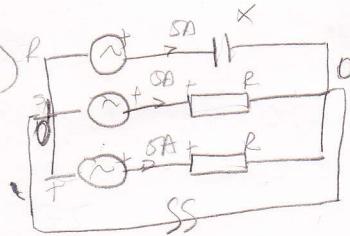

$$I_E = \frac{U_f 10^\circ}{-jX} = 5A \angle 90^\circ$$

$$I_S = \frac{U_f 1240^\circ}{R} = 5A \angle 1240^\circ$$

$$I_T = \frac{U_f 120^\circ}{R} = 5A \angle 120^\circ$$

→ jer su struje iste
kad je nultadaš
spojen (naponi
su isti)

$$U_{\infty'} = \frac{\frac{U_f 10^\circ}{-jX}}{\frac{1}{-jX} + \frac{1}{R} + \frac{1}{R}}$$

$$\frac{1}{-jX} = \frac{1}{R}$$

$$U_{\infty'} = \frac{5 10^\circ + 5 1240^\circ + 5 120^\circ}{\frac{1}{-jX} + \frac{1}{R} + \frac{1}{R}} = \frac{5 - 2,5 - 2,5}{\frac{2+j}{R}} = \frac{j 5 - 5}{2+j} \cdot R = (-1+j3) R$$

$$U_f - U_{T2} = U_{\infty'}$$


$$U_{T2} = U_f - U_{\infty'}$$

$$I = \frac{U_f - U_{\infty'}}{R}$$

$$U_2 = 5 10^\circ \cdot (-jR)$$

$$I = \frac{j 5 \cdot (-jR) - (-1+j3) \cdot R}{-jR} = \frac{-5+1-j^2}{-j} = \frac{6-j^2}{-j} = -3-6j$$

$$|I| = 2A$$

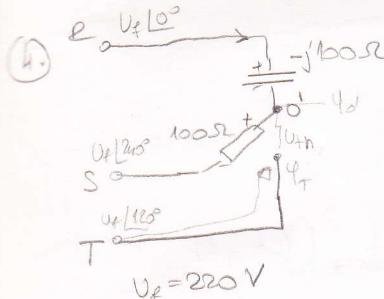

$$Z_T = 100 \parallel j 100 = 50 - j 50 \Omega$$

$$U_{ES} = U_f - U_s = 220 10^\circ - 220 1240^\circ = 330 + j 190$$

$$Z_{T2} = 100 - j 100$$

$$I = \frac{330 + j 190}{100 - j 100} = 97 + j 26$$



$$220 1240^\circ + I \cdot 100 = \varphi_o'$$

$$220 1240^\circ + 100(97 + j 26) = \varphi_o' \Rightarrow \varphi_o' = -40 + 70j$$

$$U_{TH} = U_f \angle 120^\circ - \varphi_o'$$

$$U_{TH} = -70 + j 120$$

$$|U_{TH}| = 130,92 V$$

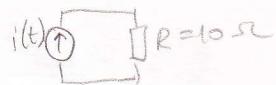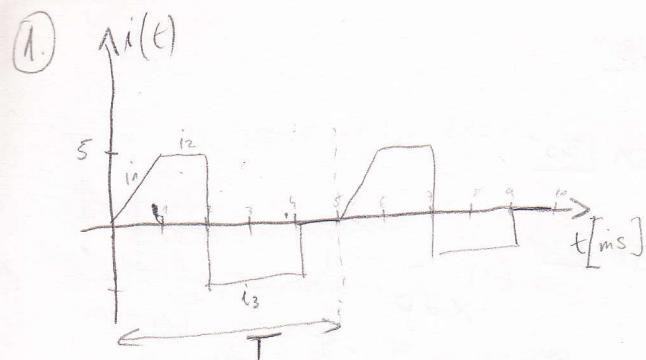

$$I_{SR} = \frac{1}{T} \int_T i(t) dt$$

$$I_{ref} = \sqrt{\frac{1}{T} \int_T (i(t))^2 dt}$$


$$I_{se} = I_{se0} \cdot \frac{T_1}{T}$$

↓
osnovni
oblik

$$I_{ref} = E_{ref} \sqrt{\frac{T_1}{T}}$$

$$I_{ref} = \sqrt{I_{ref}^2 + I_{ref}^2 + I_{ref}^2 + \dots}$$
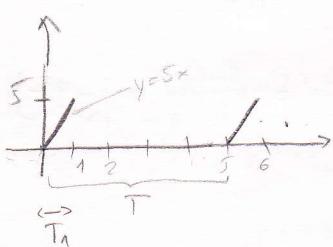
$$I_{se} = I_{se0} + I_{2se} + I_{3se} + \dots$$



$$I_{se0} = \frac{1}{5} \int_0^5 5t dt = \frac{1}{3} \cdot 5 \cdot \frac{t^2}{2} = \underline{\underline{\frac{1}{2} A}}$$

$$\underline{\underline{I_{se1} = I_{se0} \cdot \frac{T_1}{T}}} = \underline{\underline{\frac{Im}{2} \cdot \frac{1}{5} = \frac{1}{2}}}$$

$$\underline{\underline{I_{ref} = \sqrt{\frac{1}{5} \int_0^5 (5t)^2 dt} = \frac{\sqrt{15}}{3}}}$$

$$= \underline{\underline{\frac{Im}{\sqrt{2}} \cdot \sqrt{\frac{T_1}{T}}}} = \underline{\underline{\frac{5}{\sqrt{2}} \cdot \sqrt{\frac{1}{5}} = \frac{\sqrt{15}}{3}}}$$





$$I_{se} = \frac{1}{2} \int_0^2 10t dt = \frac{1}{2} \int_0^2 (10t - 10)$$

$$\underline{\underline{I_{2se} = \frac{1}{5} \int_0^5 5 dt = 1}} \\ = \underline{\underline{Im \cdot \frac{T_1}{T} = 5 \cdot \frac{1}{5} = 1}}$$

$$\underline{\underline{I_{ref} = \sqrt{\frac{1}{5} \int_0^5 5^2 dt} = \sqrt{15}}}$$
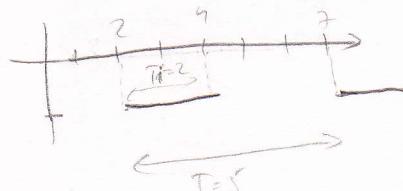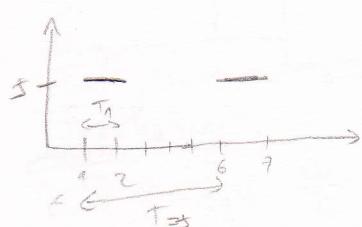
$$= \underline{\underline{Im \cdot \sqrt{\frac{T_1}{T}} = 5 \cdot \frac{1}{\sqrt{5}} = \sqrt{15}}}$$



$$\underline{\underline{I_{3se} = -5 \cdot \frac{2}{5} = -2}}$$

$$\underline{\underline{I_{ref} = 115 \cdot \sqrt{\frac{2}{5}} = 115 \cdot \frac{\sqrt{2}}{\sqrt{5}} = \sqrt{10}}}$$

$$\underline{\underline{I_{se} = \frac{1}{2} + 1 + (-2) = \frac{1}{2}}}$$

$$\underline{\underline{I_{ref} = \sqrt{\frac{15}{9} + 5 + 10} = \frac{5}{3}\sqrt{6}}}$$

↑ u SR ostavljano - /
↓ u EF je ujek +

$$\text{FAKTOR OBILJA}: \quad \xi = \frac{U_{\text{ef}}}{U_{\text{sr}}} > \frac{I_{\text{ef}}}{I_{\text{sr}}}$$

$$\text{TJEMENI FAKTOR}: \quad \alpha = \frac{U_m}{U_{\text{ef}}} = \frac{I_m}{I_{\text{ef}}}$$

ZI 2007

$$\textcircled{1} \quad I_{\text{ef}} = 0,1 \cdot \sqrt{0,1} \quad \xi = \frac{0,1 \cdot \sqrt{0,1}}{0,01} =$$

$$I_{\text{sr}} = 0,1 \cdot 0,1 = 0,01$$

$$\textcircled{2} \quad I_{\text{sr}} = \frac{6}{2} \cdot \frac{3}{5} = 1,8 \text{ A} \quad I_{\text{ef}} = \frac{6}{\sqrt{13}} \cdot \sqrt{\frac{3}{5}} = \frac{6\sqrt{5}}{5}$$


\rightarrow tječi kroz $R = 10 \Omega$

$$P_{\text{se}} = I^2 R = 1,8^2 \cdot 10 =$$

$$P_{\text{se}} = \underline{\underline{I_{\text{ef}}^2 \cdot R}} = \frac{36}{5} \cdot 10 = 72 \text{ W}$$

SREDNJA SNAGA = RADNA SNAGA

ZAD 1

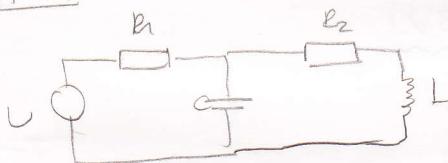

$$\begin{aligned} R_1 &= 10 \\ R_2 &= 10 \\ wL &= 10 \\ \frac{1}{wC} &= 20 \end{aligned}$$

$$I_{\text{ef}}(t) = ?$$


trezinao I_{ef} , pa ćemo sruđoje
trezini U_{ef} .

$$u(t) = 20 + 20 \sin(\omega t) + 707 \cdot \sin(2\omega t)$$

$$u(t) = U_0 + U_1 + U_2$$

$$U = U_0 = 20 \rightarrow \text{nulli harmonik}$$

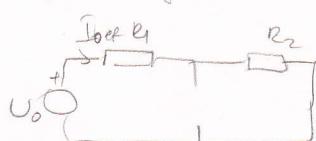\rightarrow 1st harmonika komponenta ($\omega = 0$) $\rightarrow X_L = \omega L = 0$



$$I_{\text{eff}} = \frac{20}{R_1 + R_2} = 1 \text{ A}$$


$$U = U_1 = 20\sqrt{2} \sin \omega t \rightarrow U_{\text{se}} = 0 \text{ V}$$

$$\omega = 2\pi f \rightarrow U_{\text{eff}} = 20$$

$$f_{\text{se}} = \frac{(R_2 + jX_L) \cdot (-jX_C)}{R_2 + jX_L - jX_C} + R_1$$

$$X_L = \omega L = 10$$

$$X_C = \frac{1}{\omega C} = 20$$

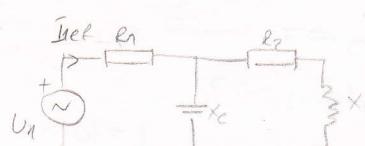

$$f_{\text{se}} = 30$$

$$I_{\text{eff}} = \frac{20}{30} = \frac{2}{3} \text{ A}$$

$$U = U_2 = 707 \sin 2\omega t \rightarrow U_{\text{se}} = 0$$

$$U_{\text{ef}} = 5 \text{ V}$$

$$X_L = 2\omega L = 20$$


$$X_C = \frac{1}{2\omega C} = 10$$

$$f_{\text{se}} = 15 - 15j = 15\sqrt{2} \angle -45^\circ$$

$$I_{\text{eff}} = \frac{5}{15\sqrt{2}} = \frac{\sqrt{2}}{6} \text{ A}$$


$$I_{\text{eff}} = \sqrt{I_{\text{b}}^2 + I_{\text{c}}^2} = \frac{\sqrt{15}}{2}$$

PRIČELZNE POJAVE

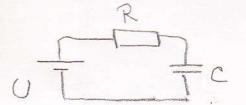

$$U_C(t) = U(1 - e^{-\frac{t}{RC}})$$

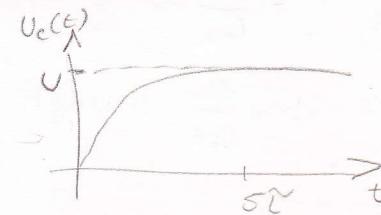
$$U_C(t) = U_C(0) + \Delta U(1 - e^{-\frac{t}{RC}})$$



sada se tender zato
napunio do kraja

$$\tau = R \cdot C$$

PR. 1

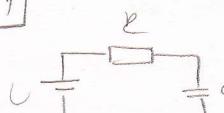

$$U = 12V$$

$$C = 1\mu F$$

$$R = 1000\Omega$$


$$Q(0) = 0C$$

$$C = \frac{Q}{U} \Rightarrow U_C(0) = \frac{Q(0)}{C} = 0V$$

$$U_R(t=20ms) = ?$$

$$\tau = R \cdot C = 10ms$$


$$t=0 \rightarrow R_C = 0$$

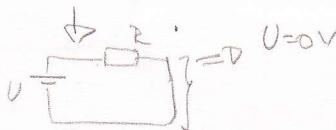

$$Q(t) = 0 + 12 \left(1 - e^{-\frac{t}{10^{-2}}} \right)$$


$$U_C(t) = 12 - 12e^{-\frac{20 \cdot 10^{-3}}{10^{-2}}} = 10,38V$$

$$t > 5\tau \rightarrow R_C = \infty$$

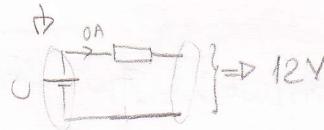

$$U_R(t_0) = 12 - 10,38 = 1,62V$$

PR. 2

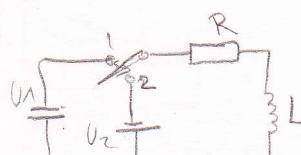

$$\tau = \frac{L}{R} = 10ms$$

$$i_L(t) = i_L(0) + \Delta I \left(1 - e^{-\frac{t}{\tau}} \right)$$

$$U_1 = 10V$$

$$U_2 = 30V$$

$$R = 10\Omega$$

$$L = 0,1H$$

$$\textcircled{S} \rightarrow t=0 \rightarrow 1 \\ t=10ms \rightarrow 2$$


$$t=10ms \Rightarrow S \Rightarrow 2$$



$$t=0 \Rightarrow S=1$$



$$t=0 \Rightarrow i_L = 0A$$

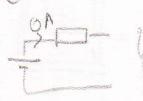

$$t = 5\tau \rightarrow R_C = 0$$

$$U_1 = \frac{U}{2} \Rightarrow I = \frac{U}{R} = 1A$$



$$i_L(t) = 0 + 1 \left(1 - e^{-\frac{t}{10^{-2}}} \right)$$

$$i_L(t=10ms) = 0,63A$$

$$t=10ms \Rightarrow S \rightarrow 2$$



$$t=0 \rightarrow R_L = \infty$$

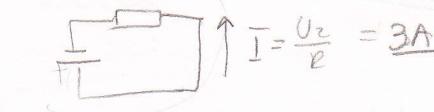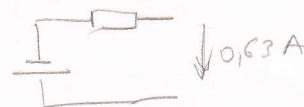

$$t=5s \rightarrow R_L = \infty$$

$$I_{L2}(t) = -0,63 + 3,63 \left(1 - e^{-\frac{t}{10^{-2}}}\right)$$

tačen nos
U_0 30s
a mimo
za mla vč
ložistli 10ms

$$I_{L2}(t=20) = -0,63 + 3,63 \left(1 - e^{-2}\right) = 2,5A$$

$$U_R(t) = I_R(t) \cdot R$$

$$U_R(t_0) = 25V$$

$$U_2(t) - U_R(t) - U_L(t) = 0$$


$$U_L(t) = U_2(t) - U_R(t)$$

$$\underline{U_L(t_0) = 30 - 25 = 5V}$$


zavojnica kroz nelo ujene
zadržava struju

a ~~zadržava~~ kondenzator zadržava napon

1.9.

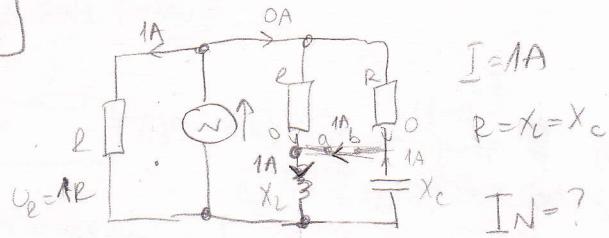

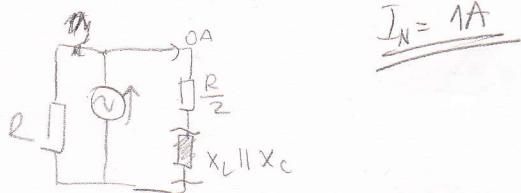
$$\begin{aligned} I_A &= 1A \\ R &= X_L = X_C \\ I_N &=? \end{aligned}$$



$$\underline{I_N = 1A}$$

1.17.

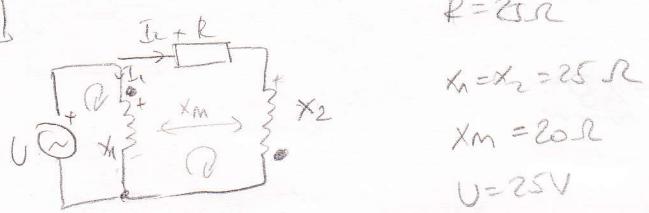

$$R = 25\Omega$$

$$X_1 = X_2 = 25\Omega$$

$$X_M = 20\Omega$$

$$U = 25V$$

$$\underline{P = ?}$$

$$U_1 - I_1 \cdot X_1 + I_2 \cdot X_M = 0$$

$$-I_2 \cdot R - I_2 \cdot X_2 + I_1 \cdot X_M + I_1 \cdot X_1 - I_2 \cdot X_M = 0$$

$$U = I_2 R + I_2 X_2 - I_1 X_M$$

$$I_1, I_2, \dots$$

$$\begin{aligned} P &= I^2 \cdot R = \\ &= \end{aligned}$$

(15)

$I_N = 0,1 \text{ A}$

$U = 120 \text{ V}$

$f = 50 \text{ Hz}$

$Z_N = \infty$

$\frac{1}{j\omega C} = j\omega L$

$X_L = X_C$

$Z_{eq} = X_L$

$0,1 = \frac{120}{X_L}$

$X_L = 1,28 \Omega$

$X_L = \omega L$

$L = \frac{120}{314} = 3,82 \text{ H}$

$\frac{1}{\omega C} = 1200$

$C = \frac{1}{\omega X_L} = 765 \mu\text{F}$

(3)

$Z_1 = 7 \Omega$

$Z_2 = 6 - j8 \Omega$

$P = 2000 \text{ W}$

$P = U \cdot I \cdot \cos \varphi = S \cdot \cos \varphi$

$Z_{eq} = |Z| e^{j\varphi}$

$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = 4,79 - j1,38 = 4,79 \angle -17^\circ$

$S = \frac{P}{\cos \varphi} = \sqrt{P^2 + Q^2}$

$Q = -600 \text{ Var}$

(6)



$U_1 = 100 \angle 0^\circ$

$U_2 = 100 \angle 60^\circ$

$I = \frac{U_{ab}}{Z} \Rightarrow Z = 3,645 \Omega$


$\frac{U_{ab}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{10 + \frac{10}{3}}{1 + \frac{1}{2} + \frac{1}{3}} = 3,27 \text{ V}$
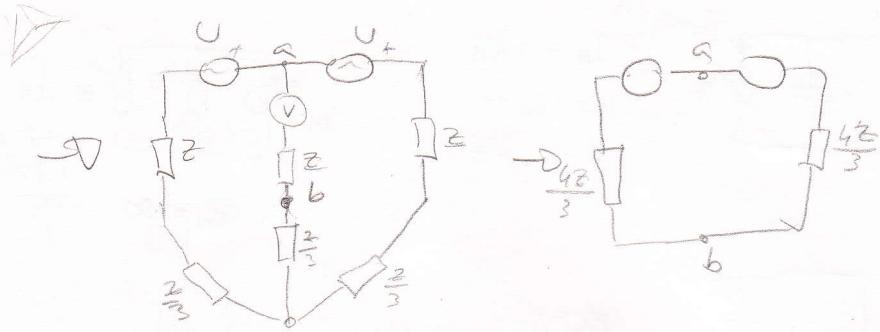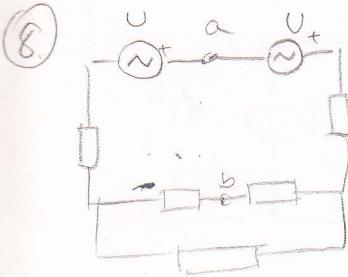
$$U_{ab} = \frac{-\frac{U_1}{Z} + \frac{U_2}{Z}}{\frac{1}{Z} + \frac{1}{Z} + \frac{1}{Z}} =$$





⑥


(21/Load)

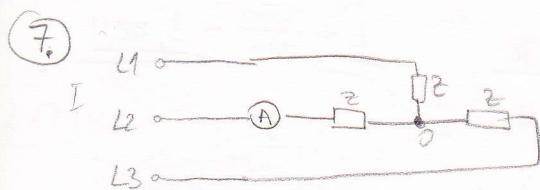

$$I_A = \frac{U_f}{Z}$$

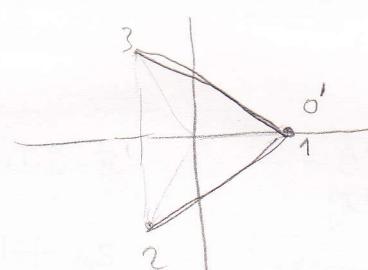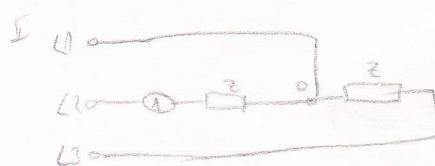
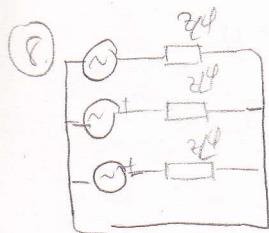
$$\tilde{I}_A^l = \frac{\sqrt{3} U_f}{Z} = \sqrt{3} \tilde{I}_A$$



$$P_l = 3 \cdot \frac{U_f^2}{Z} \cos \varphi$$


$$U' = 0,85 U_f$$


$$P' = 2 \cdot \frac{U_f^2}{Z} \cdot \cos \varphi + \frac{(0,85 U_f)^2}{Z} \cdot \cos \varphi$$

$$P' = 2,72 \cdot \frac{U_f^2}{Z} \cdot \cos \varphi$$

$$P_L = \frac{2,72}{3} P = \underline{0,9 P}$$

(21/2009)

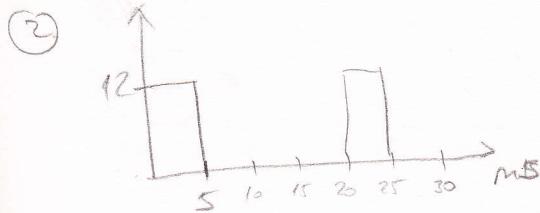

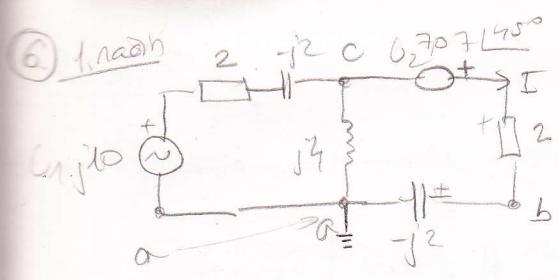

$$\begin{aligned} \varphi_A &= 0 \\ \varphi_b \left(\frac{1}{-j2} + \frac{1}{2} \right) - \varphi_c \left(\frac{1}{2} \right) &= \frac{7,07 \cancel{\text{V}}}{2} \\ -\varphi_B \frac{1}{2} + \varphi_c \left(\frac{1}{j4} + \frac{1}{2} + \frac{1}{2-j2} \right) &= -\frac{10}{2-j2} - \frac{7,07}{2} \end{aligned}$$

$$U_{ab} = \varphi_a - \varphi_b =$$

2. naeh

bez. auerla bz

$$U_{ac} = \frac{-\frac{U_1}{2-j2} + \frac{U_2}{2-j2}}{\frac{1}{2-j2} + \frac{1}{j4} + \frac{1}{2-j2}}$$

$$U_{ac} = U_2 - I \cdot 2 - I(-j2)$$

$$U_{ac} = U_2 - 2I + j2I$$

$$I = \dots$$

$$U_{ab} = -I \cdot (-j2)$$

$$U_{ab} =$$